

Common Errors Using Voltage and Current Injection

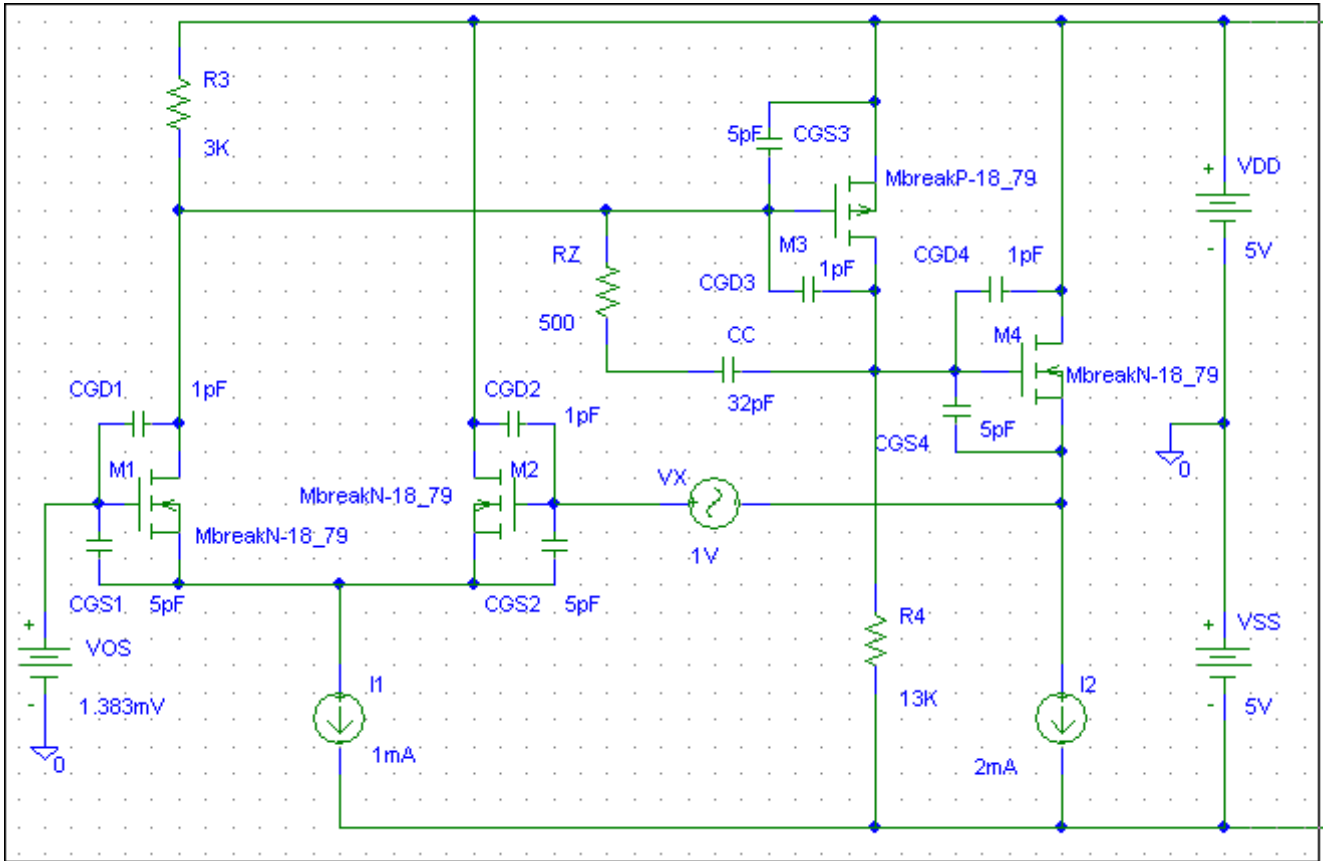


Figure 1 – Circuit schematic for Prob. 18.81 using voltage injection. Assume $T = T_v$. $T_v = (-V(M4:s)/V(M2:g))$ However, we observe strange behavior above 20 MHz. The curve of T_v crosses at 0 dB at two points!

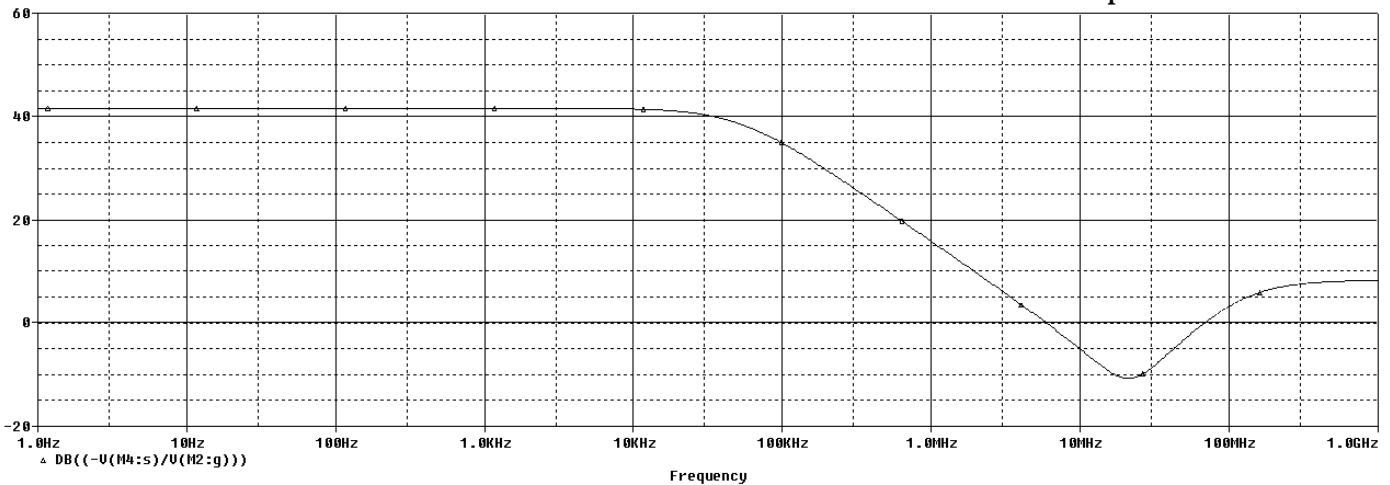


Figure 2 – Loop gain plot assuming that $T = T_v$.

The problem occurs because we are violating the assumption required for only using voltage injection. Figure 3 plots the current in V_x . The current in V_x is not zero at high frequencies. Thus the assumption that R_A is infinite is being violated at high frequencies! Therefore $T \neq T_v$.

Common Errors Using Voltage and Current Injection

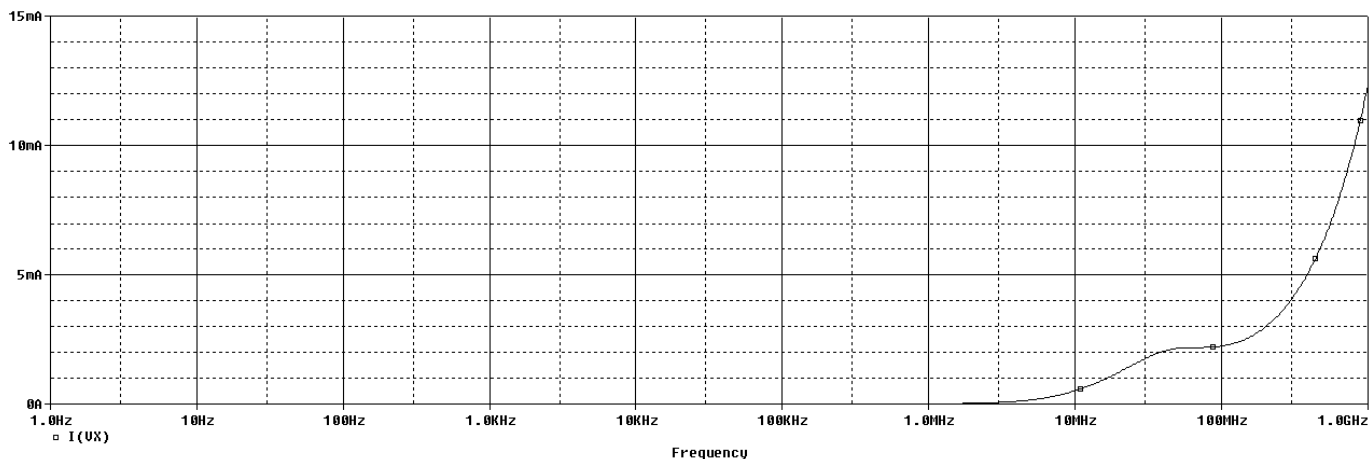


Figure 3 – Current in Vx is not zero at high frequencies.

However, we duplicate the circuit and calculate Tv, Ti and T at the same time.

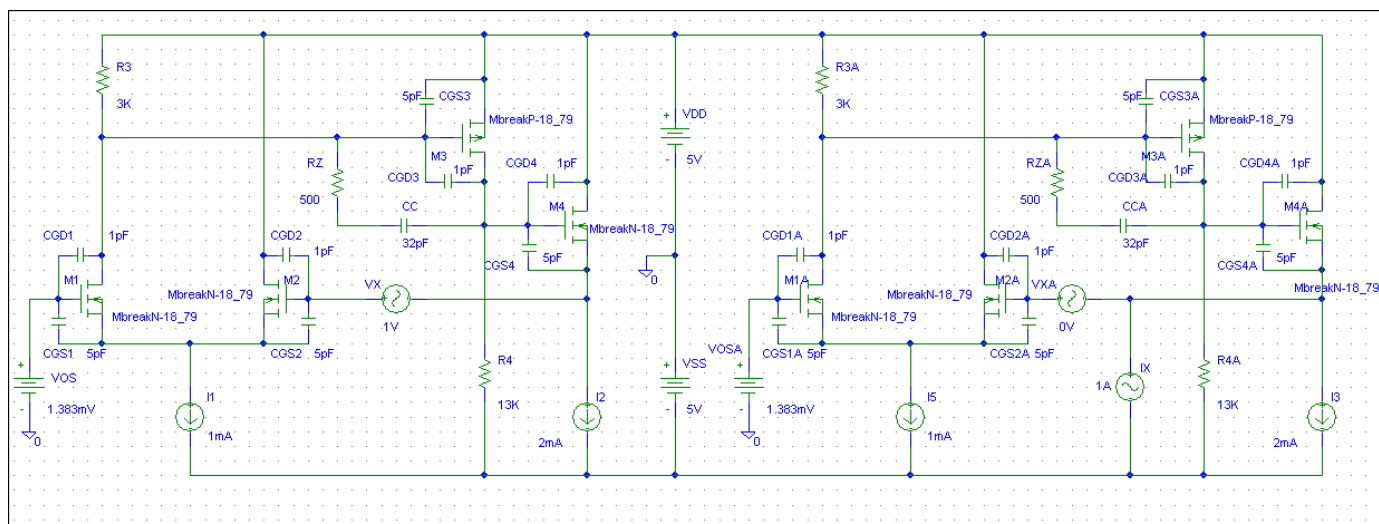


Figure 4 – Duplicated circuit allows simultaneous calculation of both Tv and Ti.

The formulae become more complicated now but can be created with a text editor and pasted into PSPICE.

$$T = (T_v * T_i - 1) / (2 + T_v + T_i)$$

$$T_v * T_i = ((-V(M4:s) / V(M2:g)) * (1 - I(VXA))) / I(VXA) - 1$$

$$2 + T_v + t_i = (2 + (-V(M4:s) / V(M2:g)) + (1 - I(VXA))) / I(VXA)$$

$$T = ((-V(M4:s) / V(M2:g)) * (1 - I(VXA))) / I(VXA) - 1 / (2 + (-V(M4:s) / V(M2:g)) + (1 - I(VXA))) / I(VXA)$$

Common Errors Using Voltage and Current Injection

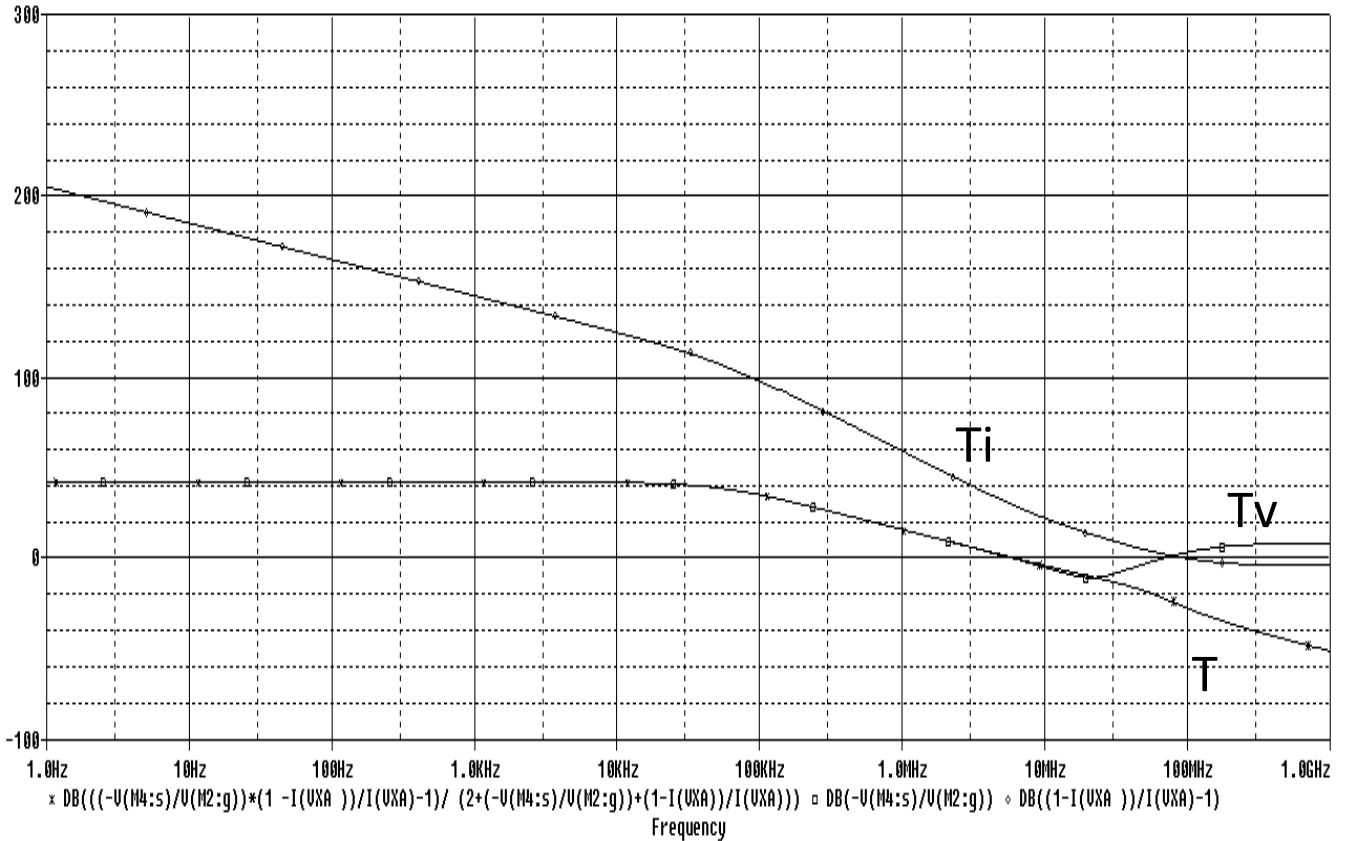


Figure 5 – Plots of T_v , T_i and T . Loop gain T now appears more reasonable with a continuous roll off at high frequencies

The general expression for loop gain is:
$$T = \frac{T_v T_i - 1}{2 + T_v + T_i}$$

As long as $T_i \gg 2 + T_v$, $T \cong T_v - \frac{1}{T_i} \cong T_v$

We see this in Fig. 5 in which $T \cong T_v$ for $f < 20\text{MHz}$.

Similarly, for $T_v \gg 2 + T_i$, $T \cong T_i - \frac{1}{T_v} \cong T_i$