

Microelectronic Circuit Design

Sixth Edition - Part I

Solutions to Exercises

CHAPTER 1

Page 1

$$V_{LSB} = \frac{5.12V}{2^{10} \text{ bits}} = \frac{5.12V}{1024 \text{ bits}} = 5.00 \text{ mV} \quad V_{MSB} = \frac{5.12V}{2} = 2.560V$$
$$1100010001_2 = 2^9 + 2^8 + 2^4 + 2^0 = 785_{10} \quad V_o = 785(5.00 \text{ mV}) = 3.925 \text{ V}$$

or $V_o = (2^{-1} + 2^{-2} + 2^{-6} + 2^{-10}) 5.12V = 3.925 \text{ V}$

Page 12

$$V_{LSB} = \frac{5.0V}{2^8 \text{ bits}} = \frac{5.00V}{256 \text{ bits}} = 19.53 \text{ mV} \quad N = \frac{1.2V}{5.00V} 256 \text{ bits} = 61.44 \text{ bits}$$
$$61 = 32 + 16 + 8 + 4 + 1 = 2^5 + 2^4 + 2^3 + 2^2 + 2^0 = 00111101_2$$
$$V_{LSB} = \frac{5.12V}{256 \text{ bits}} = 20.0 \text{ mV} \quad V_{LSB} = \frac{1.2V}{5.12V} 256 \text{ bits} = 60 \text{ bits}$$
$$60 = 32 + 16 + 8 + 4 = 2^5 + 2^4 + 2^3 + 2^2 = 00111100_2$$

Page 12

The dc component is $V_A = 4V$.

The signal consists of the remaining portion of v_A : $v_a = (5 \sin 2000\pi t + 3 \cos 1000 \pi t)$ Volts.

Page 23

$$v_o = -5 \cos(2000\pi t + 25^\circ) = -[-5 \sin(2000\pi t + 25^\circ - 90^\circ)] = 5 \sin(2000\pi t - 65^\circ)$$
$$V_o = 5\angle -65^\circ \quad V_i = 0.001\angle 0^\circ \quad A_v = \frac{5\angle -65^\circ}{0.001\angle 0^\circ} = 5000\angle -65^\circ$$

Page 25

$$A_v = -\frac{R_2}{R_1} \quad | \quad -5 = -\frac{10k\Omega}{R_1} \rightarrow R_1 = 20 \text{ k}\Omega$$

Page 26

$$v_s = [0.5 \sin(2000\pi t) + \sin(4000\pi t) + 1.5 \sin(6000\pi t)]$$

The three spectral component frequencies are $f_1 = 1000 \text{ Hz}$ $f_2 = 2000 \text{ Hz}$ $f_3 = 3000 \text{ Hz}$

(a) The gain of the band-pass filter is zero at both f_1 and f_3 . At f_2 , $V_o = 10(1V) = 10 \text{ V}$, and $v_o = 10.0 \sin(4000\pi t)$ volts.

(b) The gain of the low-pass filter is zero at both f_2 and f_3 . At f_1 , $V_o = 5(0.5V) = 2.5 \text{ V}$, and $v_o = 2.50 \sin(2000\pi t)$ volts.

Page 27

$$39k\Omega(1 - 0.1) \leq R \leq 39k\Omega(1 + 0.1) \quad \text{or} \quad 35.1 \text{ k}\Omega \leq R \leq 42.9 \text{ k}\Omega$$

$$3.6k\Omega(1 - 0.01) \leq R \leq 3.6k\Omega(1 + 0.01) \quad \text{or} \quad 3.56 \text{ k}\Omega \leq R \leq 3.64 \text{ k}\Omega$$

Page 29

$$P = \frac{V_I^2}{R_1 + R_2} \quad P^{nom} = \frac{15^2}{54k\Omega} = 4.17 \text{ mW}$$

$$P^{max} = \frac{(1.1 \times 15)^2}{0.95 \times 54k\Omega} = 5.31 \text{ mW} \quad P^{min} = \frac{(0.9 \times 15)^2}{1.05 \times 54k\Omega} = 3.21 \text{ mW}$$

Page 34

$$R = 10k\Omega \left[1 + \frac{2 \times 10^{-3}}{^\circ C} (-55 - 25) ^\circ C \right] = 8.40 \text{ k}\Omega \quad R = 10k\Omega \left[1 + \frac{2 \times 10^{-3}}{^\circ C} (-55 - 25) ^\circ C \right] = 11.2 \text{ k}\Omega$$

CHAPTER 2

Page 48

$$n_i = \sqrt{\left(2.31 \times 10^{30} \text{ K}^{-3} \text{ cm}^{-6}\right) (300 \text{ K})^3 \exp\left[\frac{-0.66 \text{ eV}}{(8.62 \times 10^{-5} \text{ eV/K})(300 \text{ K})}\right]} = 2.27 \times 10^{13} / \text{cm}^3$$

$$n_i = \sqrt{\left(1.08 \times 10^{31} \text{ K}^{-3} \text{ cm}^{-6}\right) (50 \text{ K})^3 \exp\left[\frac{-1.12 \text{ eV}}{(8.62 \times 10^{-5} \text{ eV/K})(50 \text{ K})}\right]} = 4.34 \times 10^{-39} / \text{cm}^3$$

$$n_i = \sqrt{\left(1.08 \times 10^{31} \text{ K}^{-3} \text{ cm}^{-6}\right) (325 \text{ K})^3 \exp\left[\frac{-1.12 \text{ eV}}{(8.62 \times 10^{-5} \text{ eV/K})(325 \text{ K})}\right]} = 4.01 \times 10^{10} / \text{cm}^3$$

$$L^3 = \frac{\text{cm}^3}{4.34 \times 10^{-39}} \left(10^{-2} \frac{\text{m}}{\text{cm}}\right)^3 \rightarrow L = 6.13 \times 10^{10} \text{ m}$$

Page 49

$$v_p = \mu_p E = 470 \frac{\text{cm}^2}{\text{V-s}} \left(10 \frac{\text{V}}{\text{cm}}\right) = 4.70 \times 10^3 \frac{\text{cm}}{\text{s}} \quad v_n = -\mu_n E = -1420 \frac{\text{cm}^2}{\text{V-s}} \left(1000 \frac{\text{V}}{\text{cm}}\right) = -1.42 \times 10^6 \frac{\text{cm}}{\text{s}}$$

$$E = \frac{V}{L} = \frac{1}{2 \times 10^{-4}} \frac{\text{V}}{\text{cm}} = 5.00 \times 10^3 \frac{\text{V}}{\text{cm}}$$

(a) From Fig. 2.5: The drift velocity for Ge saturates at $6 \times 10^6 \text{ cm/sec}$.

At low fields the slope is constant. Choose $E = 100 \text{ V/cm}$

$$\mu_n = \frac{v_n}{E} = \frac{4.3 \times 10^5 \text{ cm/s}}{100 \text{ V/cm}} = 4300 \frac{\text{cm}^2}{\text{s}} \quad \mu_p = \frac{v_p}{E} = \frac{2.1 \times 10^5 \text{ cm/s}}{100 \text{ V/cm}} = 2100 \frac{\text{cm}^2}{\text{s}}$$

(b) The velocity peaks at $2 \times 10^7 \text{ cm/sec}$

$$\mu_n = \frac{v_n}{E} = \frac{8.5 \times 10^5 \text{ cm/s}}{100 \text{ V/cm}} = 8500 \frac{\text{cm}^2}{\text{s}}$$

Page 51 See Table 2.1 page 44

$$n_i^2 = 1.08 \times 10^{31} (400)^3 \exp\left[\frac{-1.12}{8.62 \times 10^{-5} (400)}\right] = 5.40 \times 10^{24} / \text{cm}^6 \quad | \quad n_i = 2.32 \times 10^{12} / \text{cm}^3$$

$$\rho = \frac{1}{\sigma} = \frac{1}{1.60 \times 10^{-19} \left[(2.32 \times 10^{12})(1420) + (2.32 \times 10^{12})(470) \right]} = 1420 \, \Omega - \text{cm}$$

$$n_i^2 = 1.08 \times 10^{31} (50)^3 \exp\left[\frac{-1.12}{8.62 \times 10^{-5} (50)}\right] = 1.88 \times 10^{-77} / \text{cm}^6 \quad | \quad n_i = 4.34 \times 10^{-39} / \text{cm}^3$$

$$\rho = \frac{1}{\sigma} = \frac{1}{1.60 \times 10^{-19} \left[(4.34 \times 10^{-39})(6500) + (4.34 \times 10^{-39})(2000) \right]} = 1.69 \times 10^{53} \, \Omega - \text{cm}$$

Page 55

$$n_i^2 = 1.08 \times 10^{31} (400)^3 \exp\left[\frac{-1.12}{8.62 \times 10^{-5} (400)}\right] = 5.40 \times 10^{24} / \text{cm}^6$$

$$p = N_A - N_D = 10^{16} - 2 \times 10^{15} = 8 \times 10^{15} \frac{\text{holes}}{\text{cm}^3} \quad n = \frac{n_i^2}{p} = \frac{5.40 \times 10^{24}}{8 \times 10^{15}} = 6.75 \times 10^8 \frac{\text{electrons}}{\text{cm}^3}$$

Antimony (Sb) is a Column - V element, so it is a donor impurity. $n = N_D = 2 \times 10^{16} \frac{\text{electrons}}{\text{cm}^3}$

$$p = \frac{n_i^2}{n} = \frac{10^{20}}{2 \times 10^{16}} = 5.00 \times 10^3 \frac{\text{holes}}{\text{cm}^3} \quad n > p \rightarrow \text{n - type silicon}$$

Page 56

$$(a) \quad N_D = 10^{16} / \text{cm}^3 \quad | \quad N_A = 0 / \text{cm}^3 \quad | \quad N_T = 10^{16} / \text{cm}^3$$

$$\mu_n = 52.2 + \frac{1365}{1 + \left(\frac{1 \times 10^{16}}{9.68 \times 10^{16}} \right)^{0.68}} = 1180 \, \text{cm}^2 / \text{V} - \text{s} \quad | \quad \mu_p = 44.9 + \frac{426}{1 + \left(\frac{1 \times 10^{16}}{2.23 \times 10^{16}} \right)^{0.72}} = 318 \, \text{cm}^2 / \text{V} - \text{s}$$

$$N_D = 0 / \text{cm}^3 \quad | \quad N_A = 3 \times 10^{17} / \text{cm}^3 \quad | \quad N_T = 3 \times 10^{17} / \text{cm}^3 \quad |$$

$$\mu_n = 52.2 + \frac{1365}{1 + \left(\frac{3 \times 10^{17}}{9.68 \times 10^{16}} \right)^{0.68}} = 484 \, \text{cm}^2 / \text{V} - \text{s} \quad | \quad \mu_p = 44.9 + \frac{426}{1 + \left(\frac{3 \times 10^{17}}{2.23 \times 10^{16}} \right)^{0.72}} = 102 \, \text{cm}^2 / \text{V} - \text{s}$$

$$(b) \quad N_T = N_D + N_A = 4 \times 10^{16} / \text{cm}^3 + 6 \times 10^{16} / \text{cm}^3 = 1 \times 10^{17} / \text{cm}^3$$

$$\mu_n = 52.2 + \frac{1365}{1 + \left(\frac{1 \times 10^{17}}{9.68 \times 10^{16}} \right)^{0.68}} = 727 \, \text{cm}^2 / \text{V} - \text{s} \quad | \quad \mu_p = 44.9 + \frac{426}{1 + \left(\frac{1 \times 10^{17}}{2.23 \times 10^{16}} \right)^{0.72}} = 153 \, \text{cm}^2 / \text{V} - \text{s}$$

Page 58 Use the mobility expressions in Fig. 2.8 with a spread sheet or MATLAB

$$\sigma = 1000 = 1.60 \times 10^{-19} \mu_n n \rightarrow u_n n = 6.25 \times 10^{21} / \text{cm}^3 \cong (64.5)(9.68 \times 10^{19}) \quad | \quad \rho = \frac{1}{\sigma} = 0.001 \, \Omega\text{-cm}$$

$$(a) N_D = 2 \times 10^{16} / \text{cm}^3 \quad | \quad N_A = 0 / \text{cm}^3 \quad | \quad N_T = 2 \times 10^{16} / \text{cm}^3 \quad |$$

$$\mu_n = 52.2 + \frac{1365}{1 + \left(\frac{2 \times 10^{16}}{9.68 \times 10^{16}} \right)^{0.68}} = 1070 \, \text{cm}^2 / \text{V-s} \quad | \quad \mu_p = 44.9 + \frac{426}{1 + \left(\frac{2 \times 10^{16}}{2.23 \times 10^{16}} \right)^{0.72}} = 266 \, \text{cm}^2 / \text{V-s}$$

$$n = N_D = \frac{2 \times 10^{16}}{\text{cm}^3} \quad | \quad p = \frac{n_i^2}{n} = \frac{10^{20}}{2 \times 10^{16}} = \frac{5000}{\text{cm}^3} \quad | \quad \rho \cong \frac{1}{q u_n n} = \frac{1}{(1.60 \times 10^{-19})(1070)(2 \times 10^{16})} = 0.292 \, \Omega\text{-cm}$$

$$(b) N_T = N_D + N_A = 2 \times 10^{16} / \text{cm}^3 + 3 \times 10^{16} / \text{cm}^3 = 5 \times 10^{16} / \text{cm}^3$$

$$\mu_n = 52.2 + \frac{1365}{1 + \left(\frac{5 \times 10^{16}}{9.68 \times 10^{16}} \right)^{0.68}} = 886 \, \text{cm}^2 / \text{V-s} \quad | \quad \mu_p = 44.9 + \frac{426}{1 + \left(\frac{5 \times 10^{16}}{2.23 \times 10^{16}} \right)^{0.72}} = 198 \, \text{cm}^2 / \text{V-s}$$

$$p = N_A - N_D = \frac{1 \times 10^{16}}{\text{cm}^3} \quad | \quad n = \frac{n_i^2}{p} = \frac{10^{20}}{1 \times 10^{16}} = \frac{10000}{\text{cm}^3} \quad | \quad \rho \cong \frac{1}{q u_n n} = \frac{1}{(1.60 \times 10^{-19})(198)(1 \times 10^{16})} = 3.16 \, \Omega\text{-cm}$$

Page 59

Boron (B) is a Column-III element, so it is an acceptor impurity.

$$p = N_A - N_D = 4 \times 10^{18} \frac{\text{holes}}{\text{cm}^3} \quad | \quad n = \frac{n_i^2}{p} = \frac{10^{20}}{4 \times 10^{18}} = 25 \frac{\text{electrons}}{\text{cm}^3} \quad | \quad \text{p-type material}$$

$$N_T = \frac{4 \times 10^{18}}{\text{cm}^3} \quad \text{and mobilities from expressions in Fig. 2.8:}$$

$$\mu_n = 153 \frac{\text{cm}^2}{\text{V-s}} \quad | \quad \mu_p = 54.8 \frac{\text{cm}^2}{\text{V-s}} \quad | \quad \rho \cong \frac{1}{q \mu_p p} = \frac{1}{1.60 \times 10^{-19} (4 \times 10^{18}) (54.8)} = 0.0285 \, \Omega\text{-cm}$$

Indium (In) is a Column-III element, so it is an acceptor impurity.

$$p = N_A - N_D = 7 \times 10^{19} \frac{\text{holes}}{\text{cm}^3} \quad | \quad n = \frac{n_i^2}{p} = \frac{10^{20}}{7 \times 10^{19}} = 1.43 \frac{\text{electrons}}{\text{cm}^3} \quad | \quad \text{p-type material}$$

$$N_T = \frac{7 \times 10^{19}}{\text{cm}^3} \rightarrow \mu_n = 67.5 \frac{\text{cm}^2}{\text{V-s}} \quad | \quad \mu_p = 46.2 \frac{\text{cm}^2}{\text{V-s}}$$

$$\rho = \frac{1}{\sigma} = \frac{1}{1.60 \times 10^{-19} (7 \times 10^{19}) (46.2)} = 1.93 \, \text{m}\Omega\text{-cm}$$

Page 60

$$V_T = \frac{kT}{q} = \frac{1.38 \times 10^{-23} (50)}{1.602 \times 10^{-19}} = 4.31 \text{ mV} \quad | \quad V_T = \frac{1.38 \times 10^{-23} (77)}{1.602 \times 10^{-19}} = 6.63 \text{ mV}$$

$$V_T = \frac{1.38 \times 10^{-23} (300)}{1.602 \times 10^{-19}} = 25.8 \text{ mV} \quad | \quad V_T = \frac{1.38 \times 10^{-23} (400)}{1.602 \times 10^{-19}} = 34.5 \text{ mV}$$

$$D_n = \frac{kT}{q} \mu_n = 25.8 \text{ mV} (1365 + 52.2) \frac{\text{cm}^2}{\text{V} \cdot \text{s}} = 36.6 \frac{\text{cm}^2}{\text{s}}$$

$$D_p = \frac{kT}{q} \mu_p = 25.8 \text{ mV} (426 + 44.9) \frac{\text{cm}^2}{\text{V} \cdot \text{s}} = 12.1 \frac{\text{cm}^2}{\text{s}}$$

$$j_n = qD_n \frac{dn}{dx} = 1.60 \times 10^{-19} \text{ C} \left(20 \frac{\text{cm}^2}{\text{s}} \right) \left(\frac{10^{16}}{\text{cm}^3 - \mu\text{m}} \right) \left(\frac{10^4 \mu\text{m}}{\text{cm}} \right) = 320 \frac{\text{A}}{\text{cm}^2}$$

$$j_p = -qD_p \frac{dp}{dx} = -1.60 \times 10^{-19} \text{ C} \left(4 \frac{\text{cm}^2}{\text{s}} \right) \left(\frac{10^{16}}{\text{cm}^3 - \mu\text{m}} \right) \left(\frac{10^4 \mu\text{m}}{\text{cm}} \right) = -64 \frac{\text{A}}{\text{cm}^2}$$

CHAPTER 3

Page 78

$$\phi_j = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right) = 0.025V \ln\left(\frac{2 \times 10^{18} (10^{20})}{10^{20}}\right) = 1.05 V$$

$$w_{do} = \sqrt{\frac{2\epsilon_s}{q} \left(\frac{1}{N_A} + \frac{1}{N_D}\right) \phi_j} = \sqrt{\frac{2(11.7)(8.85 \times 10^{-14})}{1.60 \times 10^{-19}} \left(\frac{1}{2 \times 10^{18}} + \frac{1}{10^{20}}\right) (1.05)} = 2.63 \times 10^{-6} \text{ cm} = 0.0263 \mu\text{m}$$

Page 79

$$E_{\max} = \frac{1}{\epsilon_s} \int_{-x_p}^0 -qN_A dx = \frac{qN_A x_p}{\epsilon_s} \quad E_{\max} = -\frac{1}{\epsilon_s} \int_0^{x_n} qN_D dx = \frac{qN_D x_n}{\epsilon_s} \quad \text{For the values in Ex.3.2:}$$

$$E_{\max} = \frac{1.602 \times 10^{-19} \text{ C} (10^{17} / \text{cm}^3) (1.15 \times 10^{-5} \text{ cm})}{11.7 (8.854 \times 10^{-14} \text{ F/cm})} = 178 \frac{\text{kV}}{\text{cm}}$$

$$E_{\max} = \frac{2(1.05V)}{2.63 \times 10^{-6} \text{ cm}} = 798 \frac{\text{kV}}{\text{cm}}$$

$$x_p = 0.0263 \mu\text{m} \left(1 + \frac{2 \times 10^{18}}{10^{20}}\right)^{-1} = 0.0258 \mu\text{m} \quad x_n = 0.0263 \mu\text{m} \left(1 + \frac{10^{20}}{2 \times 10^{18}}\right)^{-1} = 5.16 \times 10^{-4} \mu\text{m}$$

Page 82

$$n \frac{kT}{q} = 1 \frac{1.381 \times 10^{-23} (300)}{1.602 \times 10^{-19}} = 0.0259 \quad | \quad T = \frac{300}{1.03} = 291 \text{ K} \quad |$$

$$\text{For } n = 1, \quad T = (1) \frac{1.602 \times 10^{-19} (0.025)}{1.381 \times 10^{-22}} = 290$$

Page 84 Using $V_T = 25.0 \text{ mV}$

$$i_D = 40 \times 10^{-15} \text{ A} \left[\exp\left(\frac{0.55}{0.025}\right) - 1 \right] = 143 \mu\text{A} \quad i_D = 40 \times 10^{-15} \text{ A} \left[\exp\left(\frac{0.70}{0.025}\right) - 1 \right] = 57.9 \text{ mA}$$

$$V_D = (0.025V) \ln\left(1 + \frac{6 \times 10^{-3} \text{ A}}{40 \times 10^{-15} \text{ A}}\right) = 0.643 V$$

$$i_D = 5 \times 10^{-15} \text{ A} \left[\exp\left(\frac{-0.04}{0.025}\right) - 1 \right] = -3.99 \text{ fA} \quad | \quad i_D = 5 \times 10^{-15} \text{ A} \left[\exp\left(\frac{-2.0}{0.025}\right) - 1 \right] = -5.00 \text{ fA}$$

Page 86

$$(a) V_{BE} = V_T \ln\left(1 + \frac{I_D}{I_S}\right) = 0.025V \ln\left(1 + \frac{40 \times 10^{-6} \text{ A}}{2 \times 10^{-15} \text{ A}}\right) = 0.593 \text{ V}$$

$$V_{BE} = V_T \ln\left(1 + \frac{I_D}{I_S}\right) = 0.025V \ln\left(1 + \frac{400 \times 10^{-6} \text{ A}}{2 \times 10^{-15} \text{ A}}\right) = 0.651 \text{ V} \quad \Delta V_{BE} = 57.6 \text{ mV}$$

$$(b) V_{BE} = V_T \ln\left(1 + \frac{I_D}{I_S}\right) = 0.0259V \ln\left(1 + \frac{40 \times 10^{-6} \text{ A}}{2 \times 10^{-15} \text{ A}}\right) = 0.614 \text{ V}$$

$$V_{BE} = V_T \ln\left(1 + \frac{I_D}{I_S}\right) = 0.0259V \ln\left(1 + \frac{400 \times 10^{-6} \text{ A}}{2 \times 10^{-15} \text{ A}}\right) = 0.674 \text{ V} \quad \Delta V_{BE} = 59.6 \text{ mV}$$

Page 87

$$\ln\left(\frac{i_D}{I_S}\right) = \ln(i_D) - \ln(I_S) \quad | \quad \text{Assume } i_D \text{ is constant, and } E_G = E_{GO}$$

$$\frac{dv_D}{dT} = \frac{k}{q} \ln\left(\frac{i_D}{I_S}\right) - \frac{kT}{q} \frac{1}{I_S} \frac{dI_S}{dT} = \frac{v_d}{T} - V_T \frac{1}{I_S} \frac{dI_S}{dT} \quad | \quad I_S = Kn_i^2 = KBT^3 \exp\left(-\frac{E_{GO}}{kT}\right)$$

$$\frac{dI_S}{dT} = 3KBT^2 \exp\left(-\frac{E_{GO}}{kT}\right) + KBT^3 \exp\left(-\frac{E_{GO}}{kT}\right) \left(\frac{E_{GO}}{kT^2}\right)$$

$$\frac{1}{I_S} \frac{dI_S}{dT} = \frac{3}{T} + \frac{E_{GO}}{kT^2} = \frac{3}{T} + \frac{qV_{GO}}{kT^2} = \frac{3}{T} + \frac{V_{GO}}{V_T T} \quad | \quad \frac{dv_D}{dT} = \frac{v_d}{T} - V_T \frac{1}{I_S} \frac{dI_S}{dT} = \frac{v_d - V_{GO} - 3V_T}{T}$$

$$V_D(275K) = 0.680V - 1.82 \times 10^{-3} \frac{V}{K} (300K - 275K) = 0.726 \text{ V}$$

$$V_D(350K) = 0.680V - 1.82 \times 10^{-3} \frac{V}{K} (350K - 300K) = 0.589 \text{ V}$$

Page 88

$$w_d = 0.113 \mu\text{m} \sqrt{1 + \frac{10V}{0.979V}} = 0.378 \mu\text{m} \quad | \quad E_{\text{max}} = \frac{2(V + \phi_j)}{w_d} = \frac{2(10.979V)}{0.378 \times 10^{-4} \text{ cm}} = 581 \frac{\text{kV}}{\text{cm}}$$

$$I_S = 10 \text{ fA} \sqrt{1 + \frac{10V}{0.8V}} = 36.7 \text{ fA}$$

Page 92

$$C_{j0} = \frac{11.7(8.854 \times 10^{-14} \text{ F/cm})}{0.113 \times 10^{-4} \text{ cm}} = 91.7 \frac{\text{nF}}{\text{cm}^2} \quad | \quad C_j(0\text{V}) = 91.7 \frac{\text{nF}}{\text{cm}^2} (10^{-2} \text{ cm})(1.25 \times 10^{-2} \text{ cm}) = 11.5 \text{ pF}$$

$$C_j(5\text{V}) = \frac{11.5 \text{ pF}}{\sqrt{1 + \frac{5\text{V}}{0.979\text{V}}}} = 4.64 \text{ pF}$$

Page 93

$$C_D = \frac{10^{-5} \text{ A}}{0.025\text{V}} 10^{-8} \text{ s} = 4.00 \text{ pF} \quad | \quad C_D = \frac{8 \times 10^{-4} \text{ A}}{0.025\text{V}} 10^{-8} \text{ s} = 320 \text{ pF} \quad | \quad C_D = \frac{5 \times 10^{-2} \text{ A}}{0.025\text{V}} 10^{-8} \text{ s} = 0.02 \text{ } \mu\text{F}$$

Page 98

Two points on the load line : $V_D = 0, I_D = \frac{5\text{V}}{5\text{k}\Omega} = 1 \text{ mA}; I_D = 0, V_D = 5\text{V}$

The intersection of the two curves occurs at the Q-pt : (0.88 mA, 0.6 V)

Page 100

$$10 = 10^4 I_D + V_D \quad | \quad V_D = V_T \ln\left(1 + \frac{I_D}{I_S}\right) \quad | \quad 10 = 10^4 I_D + 0.025 \ln\left(1 + \frac{I_D}{I_S}\right)$$

Page 101

```
id = fzero(@(id) (10-10000*id-0.025*log(1+id/1e-13)), 5e-4)
ans = 9.4258e-004
```

Page 102 Using MATLAB:

```
vd = fzero(@(vd) (10-10000*(1e-14)*(exp(40*vd)-1)-vd), 0.5)
vd = 0.6316 V
id = (1e-14)*(exp(40*vd)-1)
id = 9.3684e-04
---
id = fzero(@(id) (10-10000*id-log(1+id/1e-13)), .001)
id = 9.4258e-04
id = fzero(@(id) (10-10000*id-log(1+id/1e-15)), .001)
id = 9.3110e-04
```

Page 109

From the answer, the diodes are on,on,off.

$$I_1 = I_{D1} + I_{D2} \quad \frac{10V - V_B}{2.5k\Omega} = \frac{V_B - 0.6V - (-20V)}{10k\Omega} + \frac{V_B - 0.6V - (-10V)}{10k\Omega} = 0 \rightarrow V_B = 1.87 V$$

$$I_{D1} = \frac{1.87 - 0.6 - (-20V)}{10k\Omega} = 2.13 mA$$

$$I_{D2} = \frac{1.87 - 0.6 - (-10V)}{10k\Omega} = 1.13 mA \quad | \quad V_{D3} = -(1.87 - 0.6) = -1.27 V$$

$I_{D1} > 0, I_{D2} > 0, V_{D3} < 0$. These results are consistent with the assumptions.

Q-Pts: (2.13 mA, 0.60 V) (1.13 mA, 0.60 V) (0, -1.27 V)

Page 111

$$R_{\min} = \frac{5k\Omega}{\frac{20}{5} - 1} = 1.67 k\Omega$$

$$V_o = 20V \frac{1k\Omega}{5k\Omega + 1k\Omega} = 3.33 V \quad (V_Z \text{ is off}) \quad | \quad \text{For } R_L \geq 1.67 k\Omega,$$

$$V_o = 5 V \quad (V_Z \text{ is conducting})$$

Page 112

$$\frac{V_L - 20V}{1k\Omega} + \frac{V_L - 5V}{0.1k\Omega} + \frac{V_L}{5k\Omega} = 0 \rightarrow V_L = 6.25 V \quad | \quad I_Z = \frac{6.25V - 5V}{0.1k\Omega} = 12.5mA$$

$$P_Z = 5V(12.5mA) + 100\Omega(12.5mA)^2 = 78.1 mW$$

$$\text{Line Regulation} = \frac{0.1k\Omega}{0.1k\Omega + 5k\Omega} = 19.6 \frac{mV}{V} \quad \text{Load Regulation} = 0.1k\Omega || 5k\Omega = 98.0 \Omega$$

Page 118

$$V_{dc} = V_p - V_{on} = 6.3\sqrt{2} - 1 = 7.91 V \quad I_{dc} = \frac{7.91V}{0.5\Omega} = 15.8 A \quad V_r = \frac{I_{dc}}{C} T = \frac{15.8A}{0.5F} \frac{1}{60} s = 0.527 V$$

$$\Delta T = \frac{1}{\omega} \sqrt{2} \frac{V_r}{V_p} = \frac{1}{2\pi(60)} \sqrt{2} \left(\frac{0.527V}{8.91V} \right) = 0.912 ms \quad \theta_c = 120\pi(0.912ms) \frac{180^\circ}{\pi} = 19.7^\circ$$

$$V_{dc} = V_p - V_{on} = 10\sqrt{2} - 1 = 13.1 V \quad I_{dc} = \frac{13.1V}{2\Omega} = 6.57 A \quad C = \frac{I_{dc}}{V_r} T = \frac{6.57A}{0.1V} \frac{1}{60} s = 1.10 F$$

$$\Delta T = \frac{1}{\omega} \sqrt{2} \frac{V_r}{V_p} = \frac{1}{2\pi(60)} \sqrt{2} \left(\frac{0.1V}{14.1V} \right) = 0.316 ms \quad \theta_c = 120\pi(0.316ms) \frac{180^\circ}{\pi} = 6.82^\circ$$

Page 119

$$\text{At } 300\text{K}: V_D = \frac{kT}{q} \ln\left(1 + \frac{I_D}{I_S}\right) = \frac{1.38 \times 10^{-23} \text{ J/K}(300\text{K})}{1.60 \times 10^{-19} \text{ C}} \ln\left(1 + \frac{48.6 \text{ A}}{10^{-15} \text{ A}}\right) = 0.994 \text{ V}$$

$$\text{At } 50^\circ\text{C}: V_D = \frac{kT}{q} \ln\left(1 + \frac{I_D}{I_S}\right) = \frac{1.38 \times 10^{-23} \text{ J/K}(273\text{K} + 50\text{K})}{1.60 \times 10^{-19} \text{ C}} \ln\left(1 + \frac{48.6 \text{ A}}{10^{-15} \text{ A}}\right) = 1.07 \text{ V}$$

$$\text{Note: For } V_T = 0.025\text{V}, V_D = \frac{kT}{q} \ln\left(1 + \frac{I_D}{I_S}\right) = 0.025\text{V} \ln\left(1 + \frac{48.6 \text{ A}}{10^{-15} \text{ A}}\right) = 0.961 \text{ V}$$

Page 127

$$V_{rms} = \frac{V_{dc} + V_{on}}{\sqrt{2}} = \frac{15 + 1}{\sqrt{2}} = 11.3 \text{ V} \quad | \quad C = \frac{I_{dc} T}{V_r} = \frac{2 \text{ A}}{0.01(15\text{V})} \frac{1}{60} \text{ s} = 0.222 \text{ F} = 222,000 \text{ } \mu\text{F}$$

$$I_{SC} = \omega C V_p = 2\pi(60\text{Hz})(0.222\text{F})(16\text{V}) = 1340 \text{ A}$$

$$\Delta T = \frac{1}{\omega} \sqrt{2 \frac{V_r}{V_p}} = \frac{1}{2\pi(60)} \sqrt{2 \frac{(0.01)(15)}{16}} = 0.363 \text{ ms} \quad | \quad I_p = I_{dc} \frac{2T}{\Delta T} = 2 \text{ A} \frac{2\text{s}}{60(0.363\text{ms})} = 184 \text{ A}$$

CHAPTER 4

Page 152

$$(a) \beta_F = \frac{\alpha_F}{1 - \alpha_F} = \frac{0.970}{1 - 0.970} = 32.3 \quad | \quad \beta_F = \frac{0.993}{1 - 0.993} = 142 \quad | \quad \beta_F = \frac{0.250}{1 - .250} = 0.333$$

$$(b) \alpha_F = \frac{\beta_F}{\beta_F + 1} = \frac{40}{41} = 0.976 \quad | \quad \alpha_F = \frac{200}{201} = 0.995 \quad | \quad \alpha_F = \frac{3}{4} = 0.750$$

Page 154

$$i_C = 10^{-15} A \left[\exp\left(\frac{0.700}{0.0259}\right) - \exp\left(\frac{-9.30}{0.0259}\right) \right] - \frac{10^{-15} A}{0.5} \left[\exp\left(\frac{-9.30}{0.0259}\right) - 1 \right] = 0.547 \text{ mA}$$

$$i_E = 10^{-15} A \left[\exp\left(\frac{0.700}{0.0259}\right) - \exp\left(\frac{-9.30}{0.0259}\right) \right] + \frac{10^{-15} A}{100} \left[\exp\left(\frac{-9.30}{0.0259}\right) - 1 \right] = 0.552 \text{ mA}$$

$$i_B = \frac{10^{-15} A}{100} \left[\exp\left(\frac{0.700}{0.0259}\right) - \exp\left(\frac{-9.30}{0.0259}\right) \right] + \frac{10^{-15} A}{0.5} \left[\exp\left(\frac{-9.30}{0.0259}\right) - 1 \right] = 5.47 \mu A$$

Page 156

$$i_C = 10^{-16} A \left[\exp\left(\frac{0.75}{0.0259}\right) - \exp\left(\frac{0.70}{0.0259}\right) \right] - \frac{10^{-16} A}{0.4} \left[\exp\left(\frac{0.70}{0.0259}\right) - 1 \right] = 185 \mu A$$

$$i_E = 10^{-16} A \left[\exp\left(\frac{0.75}{0.0259}\right) - \exp\left(\frac{0.70}{0.0259}\right) \right] + \frac{10^{-16} A}{75} \left[\exp\left(\frac{0.75}{0.0259}\right) - 1 \right] = 327 \mu A$$

$$i_B = \frac{10^{-16} A}{75} \left[\exp\left(\frac{0.75}{0.0259}\right) - 1 \right] + \frac{10^{-16} A}{0.4} \left[\exp\left(\frac{0.70}{0.0259}\right) - 1 \right] = 142 \mu A$$

$$i_T = 10^{-15} A \left[\exp\left(\frac{0.75}{0.0259}\right) - \exp\left(\frac{-2.0}{0.0259}\right) \right] = 3.77 \text{ mA}$$

$$i_T = 10^{-15} A \left[\exp\left(\frac{0.75}{0.0259}\right) - \exp\left(\frac{-4.25}{0.0259}\right) \right] = 3.77 \text{ mA}$$

Page 157

$$v_{CE} \geq -0.0259 \ln(0.001) = 179 \text{ mV}$$

Page 159

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S} + 1\right) = 0.025V \ln\left(\frac{10^{-4} A}{10^{-16} A} + 1\right) = 0.691 V$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S} + 1\right) = 0.025V \ln\left(\frac{10^{-3} A}{10^{-16} A} + 1\right) = 0.748 V$$

For $V_T = 0.0259 V$: $V_{BE} = 0.716 V, 0.775$

Page 160

npn : $V_{BE} > 0, V_{BC} < 0 \rightarrow$ Forward – Active Region | pnp : $V_{EB} > 0, V_{CB} > 0 \rightarrow$ Saturation Region

Page 162

$$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = \frac{0.95}{0.05} = 19 \quad \beta_R = \frac{\alpha_R}{1 - \alpha_R} = \frac{0.25}{0.75} = \frac{1}{3}$$

$$V_{BE} = 0, V_{BC} \ll 0: I_C = I_S \left(1 + \frac{1}{\beta_R}\right) = 10^{-16} A \left(1 + \frac{1}{0.333}\right) = 0.400 fA$$

$$I_E = I_S = 0.100 fA \quad I_B = -\frac{I_S}{\beta_R} = -\frac{10^{-16} A}{0.333} = -0.300 fA$$

$$V_{BE} \ll 0, V_{BC} \ll 0: I_C = \frac{I_S}{\beta_R} = 3 \times 10^{-16} A = 0.300 fA$$

$$I_E = \frac{I_S}{\beta_F} = \frac{10^{-16} A}{19.0} = 5.26 aA \quad I_B = -\frac{I_S}{\beta_F} - \frac{I_S}{\beta_R} = -\frac{10^{-16} A}{19.0} - \frac{10^{-16} A}{1/3} = -0.305 fA$$

Page 164

(a) The currents do not depend upon V_{CC} as long as the collector - base junction is reverse biased by more than 0.1 V. (Later when Early voltage V_A is discussed, one should revisit this problem.)

$$(b) I_E = 100 \mu A \quad | \quad I_B = \frac{I_E}{\beta_F + 1} = \frac{100 \mu A}{51} = 1.96 \mu A \quad | \quad I_C = \beta_F I_B = 50 I_B = 98.0 \mu A$$

$$V_{BE} = V_T \ln(1 + I_C/I_S) = 0.0259V \ln(1 + 98 \mu A / 0.1 fA) = 0.715 V$$

Page 165

(a) The currents do not depend upon V_{CC} as long as the collector - base junction is reverse biased by more than 0.1 V. (Later when Early voltage V_A is discussed, one should revisit this problem.)

(b) Forward - active region : $I_B = 100 \mu A$ | $I_E = (\beta_F + 1)I_B = 5.10 mA$ | $I_C = \beta_F I_B = 5.00 mA$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S} + 1\right) = 0.025V \ln\left(\frac{5.00mA}{10^{-16}A} + 1\right) = 0.789 V \quad | \quad \text{Checking: } V_{BC} = -5 + 0.789 = -4.21$$

Forward - active region with $V_{CB} \geq 0$ requires $V_{CC} \geq V_{BE}$ or $V_{CC} \geq 0.792 V$

For $V_T = 25.9 mV$, $V_{BE} = 0.0259V \ln(5mA/0.1fA+1) = 0.817 V$ and $V_{CC} \geq 0.817 V$

Page 167

$$I_E = \frac{-0.7V - (-9V)}{5.6k\Omega} = 1.48 mA \quad | \quad I_B = \frac{I_E}{\beta_F + 1} = \frac{I_E}{51} = 29.1 \mu A \quad | \quad I_C = \beta_F I_B = 50I_B = 1.45 mA$$

$$V_{CE} = V_C - V_E = (9 - 4300I_C) - (-0.7) = 3.47 V \quad | \quad Q - Point = (1.45 mA, 3.47 V)$$

$$I_E = \frac{\beta_F + 1}{\beta_F} I_C = \frac{51}{50} 100 \mu A = 102 \mu A \quad | \quad R = \frac{-0.7V - (-9V)}{102 \mu A} = 81.4 k\Omega$$

The nearest 5% value is 82 k Ω .

Page 168

$$I_E = \frac{-0.7V - (-9V)}{5.6k\Omega} = 1.48 mA \quad | \quad I_B = \frac{I_E}{\beta_F + 1} = \frac{I_E}{51} = 29.1 \mu A \quad | \quad I_C = \beta_F I_B = 50I_B = 1.45 mA$$

$$I_E = \frac{\beta_F + 1}{\beta_F} I_C = \frac{51}{50} I_C = 102 I_C \quad | \quad V_{BE} = V_T \ln\left(\frac{I_C}{I_S} + 1\right) = 0.0259 \ln(2x10^{15} I_C + 1)$$

$$V_{BE} + 8200\Omega \left[1.02(5x10^{-16}A) \left[\exp\left(\frac{V_{BE}}{0.0259V}\right) - 1 \right] \right] = 9 V$$

Using a calculator solver, spreadsheet, MATLAB or WolframALPHA etc., $V_{BE} = 0.7333 V$.

$$I_C = 5x10^{-16} \exp\left(\frac{0.7333}{0.0259V}\right) A = 989 \mu A \quad | \quad V_{CE} = 9 - 4300I_C - (-0.7333) = 5.48 V$$

Page 169

$$I_{SD} = \frac{I_{SBJT}}{\alpha_F} = \frac{20fA}{0.95} = 21.1 fA$$

Page 171

$$-I_C = \frac{-0.7V - (-9V)}{5.6k\Omega} = 1.48 mA \quad | \quad I_B = \frac{-I_C}{\beta_R + 1} = \frac{-I_C}{2} = 0.741 mA \quad | \quad -I_E = \beta_R I_B = (1)I_B = 0.741 mA$$

Page 173

$$V_{CESAT} = (0.025V) \ln \left[\left(\frac{1}{0.5} \right) \frac{1 + \frac{1mA}{2(40\mu A)}}{1 - \frac{1mA}{50(40\mu A)}} \right] = 99.7 \text{ mV}$$

$$V_{BESAT} = (0.025V) \ln \left[\frac{0.1mA + (1-0.5)1mA}{10^{-15} A \left(\frac{1}{50} + 1 - 0.5 \right)} \right] = 0.694 \text{ mV}$$

$$V_{BCSAT} = (0.025V) \ln \left[\frac{0.1mA - \frac{1mA}{50}}{10^{-15} A \left(\frac{1}{0.5} \right) \left(\frac{1}{50} + 1 - 0.5 \right)} \right] = 0.627 \text{ mV}$$

Note: $V_{CESAT} = V_{BESAT} - V_{BCSAT} = 67.7 \text{ mV}$

For $V_T = 25.9 \text{ mV}$, scale the above results by $\frac{25.9}{25.0}$ yielding 103 mV, 0.719 V, 0.650 V.

Page 176

$$(a) D_n = \frac{kT}{q} \mu_n = 0.0259V(500 \text{ cm}^2/V - s) = 13.0 \text{ cm}^2/s$$

$$(b) I_S = \frac{qAD_n n_i^2}{N_{ABW}} = \frac{1.60 \times 10^{-19} C (50 \mu\text{m}^2) (10^{-4} \text{ cm}/\mu\text{m}) (13.0 \text{ cm}^2/s) (10^{20}/\text{cm}^6)}{(10^{18}/\text{cm}^3)(1 \mu\text{m})} = 1.04 \times 10^{-18} \text{ rounded to } 1 \text{ aA}$$

Page 179

$$V_T = \frac{(1.38 \times 10^{-23} \text{ J/K})(373 \text{ K})}{1.60 \times 10^{-19} \text{ C}} = 32.2 \text{ mV} \quad | \quad C_D = \frac{I_C}{V_T} \tau_F = \frac{10 \text{ A}}{0.0322 \text{ V}} (4 \times 10^{-9} \text{ s}) = 1.24 \mu\text{F}$$

$$f_\beta = \frac{f_T}{\beta_F} = \frac{300 \text{ MHz}}{125} = 2.40 \text{ MHz}$$

Page 180

$$I_C = 10^{-15} \left(\exp \frac{0.7}{0.0259V} \right) \left(1 + \frac{10}{50} \right) A = 0.656 \text{ mA} \quad | \quad \beta_F = 75 \left(1 + \frac{10}{50} \right) = 90 \quad | \quad I_B = \frac{0.656 \text{ mA}}{90} = 7.29 \mu\text{A}$$

$$I_C = 10^{-15} \left(\exp \frac{0.7}{0.0259V} \right) A = 0.547 \text{ mA} \quad | \quad I_B = \frac{0.547 \text{ mA}}{75} = 7.29 \mu\text{A}$$

Page 182

$$g_m = \frac{40}{V}(10^{-4} A) = 4.00 \text{ mS} \quad | \quad g_m = \frac{40}{V}(10^{-3} A) = 40.0 \text{ mS}$$

$$C_D = 4.00 \text{ mS}(25 \text{ ps}) = 0.100 \text{ pF} \quad | \quad C_D = 40.0 \text{ mS}(25 \text{ ps}) = 1.00 \text{ pF}$$

$$\frac{g_m}{I_D} = \frac{1}{V_T} = \frac{1}{0.02588 \text{ V}} = 38.6/\text{V}$$

Page 185

$$V_T = \frac{kT}{q} = \frac{1.38 \times 10^{-23}(300)}{1.60 \times 10^{-19}} = 25.9 \text{ mV} \quad | \quad I_S = \frac{I_C}{\exp\left(\frac{V_{BE}}{V_T}\right)} = \frac{350 \mu\text{A}}{\exp\left(\frac{0.68}{0.0259}\right)} = 1.39 \text{ fA}$$

$$BF = 80 \quad | \quad VAF = 70 \text{ V}$$

Page 189

$$V_{EQ} = \frac{18 \text{ k}\Omega}{18 \text{ k}\Omega + 36 \text{ k}\Omega} 12 \text{ V} = 4.00 \text{ V} \quad | \quad R_{EQ} = 18 \text{ k}\Omega \parallel 36 \text{ k}\Omega = 12 \text{ k}\Omega$$

$$I_B = \frac{4.00 - 0.7}{12 + (75 + 1)16 \text{ k}\Omega} \text{ V} = 2.687 \mu\text{A} \quad | \quad I_C = 75I_B = 202 \mu\text{A} \quad | \quad I_E = 76I_B = 204 \mu\text{A}$$

$$V_{CE} = 12 - 22000I_C - 16000I_E = 4.29 \text{ V} \quad | \quad Q\text{-point} : (202 \mu\text{A}, 4.29 \text{ V})$$

$$V_{EQ} = \frac{180 \text{ k}\Omega}{180 \text{ k}\Omega + 360 \text{ k}\Omega} 12 \text{ V} = 4.00 \text{ V} \quad | \quad R_{EQ} = 180 \text{ k}\Omega \parallel 360 \text{ k}\Omega = 120 \text{ k}\Omega$$

$$I_B = \frac{4.00 - 0.7}{120 + (75 + 1)16 \text{ k}\Omega} \text{ V} = 2.470 \mu\text{A} \quad | \quad I_C = 75I_B = 185 \mu\text{A} \quad | \quad I_E = 76I_B = 188 \mu\text{A}$$

$$V_{CE} = 12 - 22000I_C - 16000I_E = 4.29 \text{ V} \quad | \quad Q\text{-point} : (185 \mu\text{A}, 4.93 \text{ V})$$

Page 190

$$I_2 = \frac{I_C}{5} = \frac{50I_B}{5} = 10I_B$$

$$V_{EQ} = \frac{18k\Omega}{18k\Omega + 36k\Omega} 12V = 4.00 V \quad | \quad R_{EQ} = 18k\Omega || 36k\Omega = 12 k\Omega$$

$$I_B = \frac{4.00 - 0.7}{12 + (500 + 1)16 k\Omega} V = 0.4111 \mu A \quad | \quad I_C = 500I_B = 205.6 \mu A \quad | \quad I_E = 76I_B = 206.0 \mu A$$

$$V_{CE} = 12 - 22000I_C - 16000I_E = 4.18 V \quad | \quad \text{Q-point} : (206 \mu A, 4.18 V)$$

Page 192

The voltages all remain the same, and the currents are reduced by a factor of 10. Hence all the resistors are just scaled up by a factor of 10.

$$120 k\Omega \rightarrow 1.2 M\Omega \quad 82 k\Omega \rightarrow 820 k\Omega \quad 6.8 k\Omega \rightarrow 68 k\Omega$$

Page 193

$$I_B = \frac{9 - 0.7}{36 + (50 + 1)1 k\Omega} V = 95.4 \mu A \quad | \quad I_C = 50I_B = 4.77 mA \quad | \quad I_E = 51I_B = 4.87 mA$$

$$V_{CE} = 9 - 1000(I_C + I_B) = 4.13 V \quad | \quad \text{Q-point} : (4.77 mA, 4.13 V)$$

Page 194

IS	1.00E-15	VT	0.0259	BF	75
VBE	IC	V'BE			
7.0000E-01	2.0155E-04	6.7416E-01			
6.7416E-01	2.0313E-04	6.7436E-01			
6.7436E-01	2.0311E-04	6.7436E-01			
6.7436E-01	2.0311E-04	6.7436E-01			
6.7436E-01	2.0311E-04	6.7436E-01			
6.7436E-01	2.0311E-04	6.7436E-01			

CHAPTER 5

Page 220

$$K'_n = \mu_n \frac{\epsilon_{ox}}{T_{ox}} = 500 \frac{cm^2}{V-s} \frac{3.9(8.854 \times 10^{14} F/cm)}{25 \times 10^{-7} cm} = 69.1 \times 10^{-6} \frac{C}{V^2-s} = 69.1 \frac{\mu A}{V^2}$$

$$\text{Scaling: } K'_n = \frac{25 \times 10^{-7} cm}{5 \times 10^{-7} cm} \left(69.1 \frac{\mu A}{V^2} \right) = 345 \frac{\mu A}{V^2}$$

$$K_n = K'_n \frac{W}{L} = 50 \frac{\mu A}{V^2} \left(\frac{20 \mu m}{1 \mu m} \right) = 1000 \frac{\mu A}{V^2} \quad K_n = 50 \frac{\mu A}{V^2} \left(\frac{60 \mu m}{3 \mu m} \right) = 1000 \frac{\mu A}{V^2}$$

$$K_n = 50 \frac{\mu A}{V^2} \left(\frac{10 \mu m}{0.25 \mu m} \right) = 2000 \frac{\mu A}{V^2}$$

For $V_{GS} = 0 V$ and $1 V$, $V_{GS} < V_{TN}$ and the transistor is off. Therefore $I_D = 0$.

$V_{GS} - V_{TN} = 2 - 1.5 = 0.5 V$ and $V_{DS} = 0.1 V \rightarrow$ Triode region operation

$$I_D = K'_n \frac{W}{L} \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = 25 \frac{\mu A}{V^2} \left(\frac{10 \mu m}{1 \mu m} \right) \left(2 - 1.5 - \frac{0.1}{2} \right) 0.1 V^2 = 11.3 \mu A$$

$V_{GS} - V_{TN} = 3 - 1.5 = 1.5 V$ and $V_{DS} = 0.1 V \rightarrow$ Triode region operation

$$I_D = K'_n \frac{W}{L} \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = 25 \frac{\mu A}{V^2} \left(\frac{10 \mu m}{1 \mu m} \right) \left(3 - 1.5 - \frac{0.1}{2} \right) 0.1 V^2 = 36.3 \mu A$$

$$K'_n = 25 \frac{\mu A}{V^2} \left(\frac{100 \mu m}{1 \mu m} \right) = 250 \frac{\mu A}{V^2}$$

Page 221

$$R_{on} = \frac{1}{K'_n \frac{W}{L} (V_{GS} - V_{TN})} = \frac{1}{250 \frac{\mu A}{V^2} (2 - 1)} = 4.00 k\Omega \quad | \quad R_{on} = \frac{1}{250 \frac{\mu A}{V^2} (5 - 1)} = 1.00 k\Omega$$

$$V_{GS} = V_{TN} + \frac{1}{K_n R_{on}} = 1V + \frac{1}{250 \frac{\mu A}{V^2} (2000 \Omega)} = 3.00 V$$

Page 222

$V_{GS} - V_{TN} = 2.5 - 1 = 1.5 \text{ V}$ and $V_{DS} = 0.25 \text{ V} \rightarrow$ Triode region operation

$$I_D = K'_n \frac{W}{L} \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = 1000 \frac{\mu\text{A}}{\text{V}^2} \left(2.5 - 1 - \frac{0.25}{2} \right) 0.25 \text{ V}^2 = 344 \mu\text{A}$$

$$g_m = K'_n V_{DS} = 1000 \frac{\mu\text{A}}{\text{V}^2} (0.25 \text{ V}) = 250 \mu\text{S}$$

Page 224

$V_{GS} - V_{TN} = 5 - 1 = 4 \text{ V}$ and $V_{DS} = 10 \text{ V} \rightarrow$ Saturation region operation

$$I_D = \frac{K'_n}{2} (V_{GS} - V_{TN})^2 = \frac{1 \text{ mA}}{2 \text{ V}^2} (5 - 1)^2 \text{ V}^2 = 8.00 \text{ mA}$$

$$K'_n = K'_n \frac{W}{L} \rightarrow \frac{W}{L} = \frac{1 \text{ mA}}{40 \mu\text{A}} = \frac{25}{1} \quad W = 25L = 8.75 \mu\text{m}$$

Page 225

(a) $V_{GS} - V_{TN} = 2.5 - 1 = 1.5 \text{ V}$ and $V_{DS} = 0.28 \text{ V} \rightarrow$ Linear region operation

$$I_D = K'_n \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = 1 \frac{\text{mA}}{\text{V}^2} \left(2.5 - 1 - \frac{0.28}{2} \right) 0.28 \text{ V}^2 = 381 \mu\text{A}$$

$$g_m = K'_n V_{DS} = 1 \frac{\text{mA}}{\text{V}^2} 0.28 \text{ V} = 280 \mu\text{S}$$

(b) $V_{GS} - V_{TN} = 2.5 - 1 = 1.5 \text{ V}$ and $V_{DS} = 4 \text{ V} \rightarrow$ Saturation region operation

$$I_D = \frac{K'_n}{2} (V_{GS} - V_{TN})^2 = \frac{1 \text{ mA}}{2 \text{ V}^2} (2.5 - 1)^2 \text{ V}^2 = 1.13 \text{ mA}$$

$$g_m = K'_n (V_{GS} - V_{TN}) = 1 \frac{\text{mA}}{\text{V}^2} (1.5) = 1.50 \text{ mS}$$

Page 226

$V_{GS} - V_{TN} = 5 - 1 = 4 \text{ V}$ and $V_{DS} = 10 \text{ V} \rightarrow$ Saturation region operation

$$I_D = \frac{K'_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) = \frac{1 \text{ mA}}{2 \text{ V}^2} (5 - 1)^2 \text{ V}^2 [1 + 0.02(10)] = 9.60 \text{ mA}$$

$$I_D = \frac{K'_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) = \frac{1 \text{ mA}}{2 \text{ V}^2} (5 - 1)^2 \text{ V}^2 [1 + 0(10)] = 8.00 \text{ mA}$$

Page 227

$V_{GS} - V_{TN} = 4 - 1 = 3 \text{ V}$ and $V_{DS} = 5 \text{ V} \rightarrow$ Saturation region operation

$$I_D = \frac{K'_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) = \frac{25 \mu\text{A}}{2 \text{ V}^2} (4 - 1)^2 \text{ V}^2 [1 + 0.01(5)] = 118 \mu\text{A}$$

$$I_D = \frac{K'_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) = \frac{25 \mu\text{A}}{2 \text{ V}^2} (5 - 1)^2 \text{ V}^2 [1 + 0.01(10)] = 220 \mu\text{A}$$

Digitizing the graph with a digitizer App yields (5 V, 204 μA) and (10 V, 214 μA)

$$\lambda = \frac{1}{200 \mu\text{A}} \frac{(214 \mu\text{A} - 204 \mu\text{A})}{10 \text{ V} - 5 \text{ V}} = 0.010/\text{V}$$

Page 228

Assuming pinchoff region operation, $I_D = \frac{K_n}{2}(0 - V_{TN})^2 = \frac{50 \mu A}{2} (+2V)^2 = 100 \mu A$

$$V_{GS} = V_{TN} + \sqrt{\frac{2I_D}{K_n}} = 2V + \sqrt{\frac{2(100 \mu A)}{50 \mu A/V^2}} = 4.00 V$$

Assuming pinchoff region operation, $I_D = \frac{K_n}{2}(V_{GS} - V_{TN})^2 = \frac{50 \mu A}{2} [1 - (-2V)]^2 = 225 \mu A$

Page 230

$$V_{TN} = V_{TO} + \gamma(\sqrt{V_{SB} + 0.6V} - \sqrt{0.6V}) = 1 + 0.75(\sqrt{0 + 0.6} - \sqrt{0.6}) = 1 V$$

$$V_{TN} = 1 + 0.75(\sqrt{1.5 + 0.6} - \sqrt{0.6}) = 1.51 V \quad | \quad V_{TN} = 1 + 0.75(\sqrt{3 + 0.6} - \sqrt{0.6}) = 1.84 V$$

(a) V_{GS} is less than the threshold voltage, so the transistor is cut off and $I_D = 0$.

(b) $V_{GS} - V_{TN} = 2 - 1 = 1 V$ and $V_{DS} = 0.5 V \rightarrow$ Triode region operation

$$I_D = K_n \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = 1 \frac{mA}{V^2} \left(2 - 1 - \frac{0.5}{2} \right) 0.5V^2 = 375 \mu A$$

(c) $V_{GS} - V_{TN} = 2 - 1 = 1 V$ and $V_{DS} = 2 V \rightarrow$ Saturation region operation

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) = 0.5 \frac{mA}{V^2} (2 - 1)^2 V^2 [1 + 0.02(2)] = 520 \mu A$$

Page 232

(a) V_{GS} is greater than the threshold voltage, so the transistor is cut off and $I_D = 0$.

(b) $|V_{GS} - V_{TN}| = |-2 + 1| = 1 V$ and $|V_{DS}| = 0.5 V \rightarrow$ Triode region operation

$$I_D = K_n \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = 0.4 \frac{mA}{V^2} \left(-2 + 1 - \frac{-0.5}{2} \right) (-0.5)V^2 = 150 \mu A$$

(c) $|V_{GS} - V_{TN}| = |-2 + 1| = 1 V$ and $|V_{DS}| = 2 V \rightarrow$ Saturation region operation

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) = \frac{0.4 mA}{2 V^2} (-2 + 1)^2 V^2 [1 + 0.02(2)] = 208 \mu A$$

Page 235

$$(a) V_{DS} = 1.9V \mid V_{GS} - V_{TN} = 2.3V \mid I_D = K_n \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$I_D = 60\mu A \left(3 - 0.7 - \frac{1.9}{2} \right) 1.9 = 154 \mu A$$

$$(b) \text{ See Table S6.10 Fall time: } t_f = 3.7R_{on}C = 3.7 \frac{50fF}{60 \times 10^{-6}(3 - 0.7) \frac{1}{\Omega}} = 1.34 nS$$

(c) Oops! – See Sec. 5.10.7

$$I_D = K_n \left(V_{GS} - V_{TN} - \frac{V_{MIN}}{2} \right) V_{MIN} \mid V_{MIN} = \min(V_{GS} - V_{TN}, V_{DS}, V_{SAT}) = 1V$$

$$I_D = 60\mu A \left(3 - 0.7 - \frac{1}{2} \right) 1 = 108 \mu A$$

$$V_C = V_{BL} - V_{TN} \mid V_C = 3 - \left[0.7 + 0.5 \left(\sqrt{V_C + 0.6} - \sqrt{0.6} \right) \right] \rightarrow V_C = 1.89V \mid V_C = 3 - 0.7 = 2.3V$$

$$n = \frac{CV}{q} = \frac{25 \times 10^{-15} F (1.89V)}{1.60 \times 10^{-19} C} = 2.95 \times 10^5 \text{ electrons}$$

Page 237

$$(a) \Delta V = \frac{V_C - V_{BL}}{\frac{C_{BL}}{C_C} + 1} = \frac{1.9 - 0.95}{\frac{49C_C}{C_C} + 1} V = 19.0 mV \mid \Delta V = \frac{V_C - V_{BL}}{\frac{C_{BL}}{C_C} + 1} = \frac{0 - 0.95}{\frac{49C_C}{C_C} + 1} V = -19.0 mV$$

$$(b) \tau = R_{on} \frac{C_C}{\frac{C_C}{C_{BL}} + 1} = 5k\Omega \frac{25fF}{\frac{1}{49} + 1} = 0.123 ns \quad \text{or} \quad \tau \cong R_{on} C_C = 5k\Omega (25fF) = 0.125 ns$$

Page 240

$$(a) K_p = 40 \times 10^{-6} \left(\frac{20}{1} \right) = 800 \frac{\mu A}{V^2} \mid K_n = 100 \times 10^{-6} \left(\frac{20}{1} \right) = 2000 \frac{\mu A}{V^2} = 2.00 \frac{mA}{V^2}$$

$$(b) V_{TN} = 0.6 + 0.5 \left(\sqrt{2.5 + 0.6} - \sqrt{0.6} \right) = 1.09V$$

$$(c) V_{TP} = -0.6 - 0.75 \left(\sqrt{2.5 + 0.7} - \sqrt{0.7} \right) = -1.31V$$

Page 241

(a) For $v_I = 1\text{ V}$, $V_{G_{SN}} - V_{TN} = 1 - 0.6 = 0.4\text{ V}$ and $V_{G_{SP}} - V_{TP} = -1.5 + 0.6 = -0.9\text{ V}$

M_N is saturated for $v_O \geq 0.4\text{ V}$. M_P is in the triode region for $v_O \geq 1.6\text{ V}$. $\therefore 1.6\text{ V} \leq v_O \leq 2.5\text{ V}$

(b) M_P is saturated for $v_O \leq 1.6\text{ V}$. $\therefore 0.4\text{ V} \leq v_O \leq 1.6\text{ V}$

(c) M_N is in the triode region for $v_O \leq 0.4\text{ V}$. M_P is saturated for $v_O \leq 1.6\text{ V}$. $\therefore 0 \leq v_O \leq 0.4\text{ V}$

$$\left(\frac{W}{L}\right)_P = \frac{K_n}{K_p} \left(\frac{W}{L}\right)_N = 2.5 \left(\frac{10}{1}\right) = \frac{25}{1}$$

Page 242

Both transistors are saturated since $|V_{GS}| = |V_{DS}|$.

$$\frac{K_n}{2} (V_{G_{SN}} - V_{TN})^2 = \frac{K_p}{2} (V_{G_{SP}} - V_{TP})^2 \quad K_n = K_p \quad |V_{TN}| = |V_{TP}|$$

$$V_{G_{SN}} = -V_{G_{SP}} \rightarrow v_I = V_{DD} - v_I \rightarrow v_I = \frac{V_{DD}}{2}$$

$$\frac{10K_p}{2} (V_{G_{SN}} - V_{TN})^2 = \frac{K_p}{2} (V_{G_{SP}} - V_{TP})^2 \rightarrow \sqrt{10} (V_{G_{SN}} - V_{TN}) = -V_{G_{SP}} + V_{TP}$$

$$\sqrt{10} (v_I - 0.6) = 4 - v_I - 0.6 \rightarrow v_I = 1.273\text{ V}$$

$$\frac{K_p}{2} (V_{G_{SN}} - V_{TN})^2 = \frac{10K_p}{2} (V_{G_{SP}} - V_{TP})^2 \rightarrow (V_{G_{SN}} - V_{TN}) = \sqrt{10} (-V_{G_{SP}} + V_{TP})$$

$$v_I - 0.6 = \sqrt{10} (4 - v_I - 0.6) \rightarrow v_I = 2.727\text{ V}$$

Page 247

$$C_{GC} = \left(200 \frac{\mu\text{F}}{\text{m}^2}\right) (5 \times 10^{-6} \text{ m}) (0.5 \times 10^{-6} \text{ m}) = 0.500 \text{ fF}$$

$$\text{Triode region: } C_{GD} = C_{GS} = \frac{C_{GC}}{2} + C_{GSO} W = 0.25 \text{ fF} + \left(300 \frac{\text{pF}}{\text{m}}\right) (5 \times 10^{-6} \text{ m}) = 1.75 \text{ fF}$$

$$\text{Saturation region: } C_{GS} = \frac{2}{3} C_{GC} + C_{GSO} W = 0.333 \text{ fF} + \left(300 \frac{\text{pF}}{\text{m}}\right) (5 \times 10^{-6} \text{ m}) = 1.83 \text{ fF}$$

$$C_{GD} = C_{GSO} W = \left(300 \frac{\text{pF}}{\text{m}}\right) (5 \times 10^{-6} \text{ m}) = 1.50 \text{ fF}$$

Page 249

$$KP = K_n = 150U \quad | \quad LAMBDA = \lambda = 0.0133 \quad | \quad VTO = V_{TN} = 1 \quad | \quad PHI = 2\phi_F = 0.6$$

$$W = W = 1.5U \quad | \quad L = L = 0.25U$$

Page 251

$$\text{Circuits/cm}^2 \propto \alpha^2 = \left(\frac{0.18\mu\text{m}}{10\text{nm}}\right)^2 = \left(\frac{0.18\mu\text{m}}{0.010\mu\text{m}}\right)^2 = (18)^2 = 324$$

$$\text{Power - Delay Product} \propto \frac{1}{\alpha^3} = \frac{1}{18^3} = \frac{1}{5832}; \text{ Rounding} \rightarrow 5830 \text{ times improvement}$$

$$i_D^* = \mu_n \frac{\epsilon_{ox}}{T_{ox}} \frac{W}{\alpha} \frac{V_{GS} - V_{TN} - \frac{V_{DS}}{2}}{L/\alpha} v_{DS} = \alpha i_D \quad | \quad P^* = V_{DD} i_D^* = V_{DD} (\alpha i_D) = \alpha P$$

$$\frac{P^*}{A^*} = \frac{\alpha P}{(W/\alpha)(L/\alpha)} = \alpha^3 \frac{P}{A} \quad \rightarrow \quad i_D^* = \alpha i_D \quad | \quad P^* = \alpha P \quad | \quad \frac{P^*}{A^*} = \alpha^3 \frac{P}{A}$$

Page 252

$$(a) f_T = \frac{1}{2\pi} \frac{500\text{cm}^2 / V - s}{(0.25 \times 10^{-4} \text{cm})^2} (1V) = 127 \text{ GHz}$$

$$(b) f_T = \frac{1}{2\pi} \frac{500\text{cm}^2 / V - s}{(40\text{nm})^2} (1V) = \frac{1}{2\pi} \frac{500\text{cm}^2 / V - s}{\left[(40 \times 10^{-9} \text{m}) \left(100 \frac{\text{cm}}{\text{m}}\right)\right]^2} (1V) = 4.97 \text{ THz}$$

Page 253

$$\frac{V}{L} \geq 10^5 \frac{V}{\text{cm}} \rightarrow V = \left(10^5 \frac{V}{\text{cm}}\right) (10^{-4} \text{cm}) = 10 \text{ V}$$

$$V = \left(10^5 \frac{V}{\text{cm}}\right) (10^{-5} \text{cm}) = 1 \text{ V} \quad | \quad L = \left(10^5 \frac{V}{\text{cm}}\right) (15 \times 10^{-7} \text{cm}) = 0.15 \text{ V}$$

$$V_{MIN} = \min[(V_{GS} - V_{TN}), V_{DS}, V_{SAT}] = \min[3.5, 4, 2.5] = 2.5 \text{ V}$$

$$I_D = K_n \left(V_{GS} - V_{TN} - \frac{V_{MIN}}{2}\right) V_{MIN} (1 + \lambda V_{DS}) = 10^{-4} \left(4 - 0.5 - \frac{2.5}{2}\right) (2.5) [1 + 0.02(4)] = 607.5 \mu\text{A}$$

$$V_{MIN} = \min[(V_{GS} - V_{TN}), V_{DS}, V_{SAT}] = \min[3.5, 4, 20] = 3.5 \text{ V}$$

$$I_D = K_n \left(V_{GS} - V_{TN} - \frac{V_{MIN}}{2}\right) V_{MIN} (1 + \lambda V_{DS}) = 10^{-4} \left(3.5 - \frac{3.5}{2}\right) (3.5) [1 + 0.02(4)] = 661.5 \mu\text{A}$$

Page 258

(a) From the graph for $V_{GS} = 0.25 \text{ V}$, $I_D \cong 10^{-18} \text{ A}$ |

(b) From the graph for $V_{GS} = V_{TN} - 0.5 \text{ V}$, $I_D \cong 3 \times 10^{-15} \text{ A}$

(c) $I = (10^9 \text{ transistors})(3 \times 10^{-15} \text{ A/transistors}) = 3 \mu\text{A}$

From the graph in the exponential region:

$$(V_{GS}, I_D) = (0.45\text{V}, 10^{-10}\text{A}), (0.70\text{V}, 10^{-8}\text{A}) \text{ and } I_D = I_{D0} \exp\left(\frac{V_{GS} - V_{TN}}{nV_T}\right)$$

$$\frac{10^{-8}}{10^{-10}} = \frac{I_{D0} \exp\left(\frac{0.70 - V_{TN}}{nV_T}\right)}{I_{D0} \exp\left(\frac{0.45 - V_{TN}}{nV_T}\right)} \rightarrow 100 = \exp\left(\frac{0.25}{nV_T}\right) \rightarrow n = \frac{0.25}{(0.0259)\ln(100)} = 2.096 \rightarrow 2.10$$

$$I_{D0} = \frac{10^{-8}}{\exp\left(\frac{0.2}{0.054287}\right)} = 0.251 \times 10^{-9} \text{ A} \text{ and } I_{D0} = \frac{10^{-10}}{\exp\left(\frac{-0.05}{0.054287}\right)} = 0.251 \times 10^{-9} \text{ | } I_{D0} = 0.251 \text{ nA}$$

Using the previous values: $nV_T = 2.086(0.02590) = 54.286 \text{ mV} \rightarrow 54.3 \text{ mV/decade}$

$$I_D = I_{D0} \exp\left(\frac{V_{GS} - V_{TN}}{nV_T}\right) \quad | \quad g_m = \frac{I_D}{nV_T} \quad | \quad \frac{g_m}{I_D} = \frac{1}{nV_T} = \frac{1}{0.054287} = 18.4$$

$$(a) V_{GS} = V_{TN}: \left[\ln\left(1 + \exp\left(\frac{0 - nV_{DS}}{2nV_T}\right)\right) \right]^2 = (0.05) \left[\ln\left(1 + \exp\left(\frac{0}{2nV_T}\right)\right) \right]^2$$

$$\left[\ln\left(1 + \exp\left(\frac{-V_{DS}}{2V_T}\right)\right) \right] = (\sqrt{0.05})\ln(2) \quad | \quad 1 + \exp\left(\frac{-V_{DS}}{2V_T}\right) = 1.1676$$

$$| V_{DS} = -2(0.0259)\ln(0.16765) \quad | \quad V_{DS} = 92.509 \text{ mV}$$

$$I_D = 100 \mu\text{A} \left(\left[\ln(2) \right]^2 - \left[\ln\left(1 + \exp\left(-\frac{92.509 \text{ mV}}{2(25.9 \text{ mV})}\right)\right) \right]^2 \right) = 45.643 \mu\text{A}$$

$$\text{Check: } I_D = 100 \mu\text{A}(0.95)[\ln(2)]^2 = 45.643 \mu\text{A}$$

$$(b) V_{GS} - V_{TN} = -0.2 \text{ V}: \left[\ln\left(1 + \exp\left(-\frac{0.2 + 1.5V_{DS}}{3V_T}\right)\right) \right]^2 = (0.05) \left[\ln\left(1 + \exp\left(-\frac{0.2}{3V_T}\right)\right) \right]^2$$

$$\left[\ln\left(1 + \exp\left(-\frac{0.2 + 1.5V_{DS}}{3V_T}\right)\right) \right] = (\sqrt{0.05})\ln\left(1 + \exp\left(-\frac{0.2}{3V_T}\right)\right) = 0.016427$$

$$\left(\exp\left(-\frac{0.2 + 1.5V_{DS}}{3V_T}\right) \right) = -1 + \exp(0.016427) = 0.016563$$

$$0.2 + 1.5V_{DS} = -3V_T \ln(0.016563) \rightarrow V_{DS} = 79.077 \text{ mV}$$

$$I_D = 100 \mu\text{A}(0.95) \left[\ln\left(1 + \exp\left(-\frac{0.2}{3V_T}\right)\right) \right]^2 = 0.51271 \mu\text{A}$$

Page 261

(a)

$$L = 2\Lambda = 0.250 \mu m \quad | \quad W = 10\Lambda = 1.25 \mu m$$

$$\text{Active area} = 10\Lambda(12\Lambda) = 120\Lambda^2 = 120(0.125\mu m)^2 = 1.88 \mu m^2$$

$$\text{Gate area} = 2\Lambda(10\Lambda) = 20\Lambda^2 = 20(0.125\mu m)^2 = 0.313 \mu m^2$$

$$\text{Transistor area} = (10\Lambda + 2\Lambda + 2\Lambda)(12\Lambda + 2\Lambda + 2\Lambda) = 224\Lambda^2 = 224(0.125\mu m)^2 = 3.50 \mu m^2$$

$$N = \frac{(10^4 \mu m)^2}{3.50 \mu m^2} = 28.6 \times 10^6 \text{ transistors}$$

(b)

$$L = 2\Lambda = 40 \text{ nm} \quad | \quad W = 10\Lambda = 200 \text{ nm}$$

$$\text{Active area} = 200\text{nm}(240\text{nm}) = 4.8 \times 10^4 \text{ nm}^2 = 0.048 \times 10^{-2} \mu m^2$$

$$\text{Gate area} = 40\text{nm}(200\text{nm}) = 8 \times 10^3 \text{ nm}^2 = 0.008 \times 10^{-2} \mu m^2$$

$$\text{Transistor area} = 280\text{nm}(320\text{nm}) = 8.96 \times 10^4 \text{ nm}^2 = 8.96 \times 10^{-2} \mu m^2$$

$$N = \frac{(10^4 \mu m)^2}{8.96 \times 10^{-2} \mu m^2} = 1.12 \times 10^9 \text{ transistors}$$

Page 270 Upper group

$$V_{GS}^2 + V_{GS} \left(\frac{2}{K_n R_S} - 2V_{TN} \right) + V_{TN}^2 - \frac{2V_{EQ}}{K_n R_S} = 0 \quad | \quad V_{GS} = - \left(\frac{1}{K_n R_S} - V_{TN} \right) \pm \sqrt{\left(\frac{1}{K_n R_S} - V_{TN} \right)^2 - V_{TN}^2 + \frac{2V_{EQ}}{K_n R_S}}$$

$$V_{GS} = V_{TN} - \frac{1}{K_n R_S} \pm \sqrt{\left(\frac{1}{K_n R_S} \right)^2 - \frac{2V_{TN}}{K_n R_S} + V_{TN}^2 - V_{TN}^2 + \frac{2V_{EQ}}{K_n R_S}} = V_{TN} + \frac{1}{K_n R_S} \left(\sqrt{1 + 2K_n R_S (V_{EQ} - V_{TN})} - 1 \right)$$

Assume saturation region operation.

$$I_D = \frac{1}{2K_n R_S^2} \left(\sqrt{1 + 2K_n R_S (V_{EQ} - V_{TN})} - 1 \right)^2$$

$$I_D = \frac{1}{2(30\mu A)(39k\Omega)^2} \left(\sqrt{1 + 2(30\mu A)(39k\Omega)(4 - 1)} - 1 \right)^2 = 36.8 \mu A$$

$$V_{DS} = 10 - 114k\Omega(36.8\mu A) = 5.81 V \quad | \quad \text{Saturation region is correct.} \quad | \quad \text{Q-Point: } (36.8 \mu A, 5.81 V)$$

Assume saturation region operation.

$$I_D = \frac{1}{2(25\mu A)(39k\Omega)^2} \left(\sqrt{1 + 2(25\mu A)(39k\Omega)(4 - 1.5)} - 1 \right)^2 = 26.7 \mu A$$

$$V_{DS} = 10 - 114k\Omega(26.7\mu A) = 6.96 V \quad | \quad \text{Saturation region is correct.} \quad | \quad \text{Q-Point: } (26.7 \mu A, 6.96 V)$$

Assume saturation region operation.

$$I_D = \frac{1}{2(25\mu A)(62k\Omega)^2} \left(\sqrt{1 + 2(25\mu A)(62k\Omega)(4 - 1)} - 1 \right)^2 = 25.4 \mu A$$

$$V_{DS} = 10 - 137k\Omega(25.4\mu A) = 6.52 V \quad | \quad \text{Saturation region is correct.} \quad | \quad \text{Q-Point: } (25.4 \mu A, 6.52 V)$$

Page 271 Second group

$$V_{EQ} = \frac{R_1}{R_1 + R_2} V_{DD} = \frac{1M\Omega}{1M\Omega + 1.5M\Omega} 10V = 4V \quad | \text{ Assume saturation region operation.}$$

$$I_D = \frac{1}{2K_n R_S^2} \left(\sqrt{1 + 2K_n R_S (V_{EQ} - V_{TN})} - 1 \right)^2$$

$$I_D = \frac{1}{2(25\mu A)(1.8k\Omega)^2} \left(\sqrt{1 + 2(25\mu A)(1.8k\Omega)(4 - 1)} - 1 \right)^2 = 99.5 \mu A$$

$$V_{DS} = 10 - 40.8k\Omega(99.5\mu A) = 5.94V \quad | \text{ Saturation region is correct. } | \text{ Q-Point: } (99.5 \mu A, 5.94V)$$

$$V_{EQ} = \frac{R_1}{R_1 + R_2} V_{DD} = \frac{1.5M\Omega}{1.5M\Omega + 1M\Omega} 10V = 6V \quad | \text{ Assume saturation region operation.}$$

$$I_D = \frac{1}{2(25\mu A)(22k\Omega)^2} \left(\sqrt{1 + 2(25\mu A)(22k\Omega)(6 - 1)} - 1 \right)^2 = 99.2 \mu A$$

$$V_{DS} = 10 - 40k\Omega(99.2\mu A) = 6.03V \quad | \text{ Saturation region is correct. } | \text{ Q-Point: } (99.2 \mu A, 6.03V)$$

$$I_{Bias} = \frac{V_{DD}}{R_1 + R_2} \rightarrow R_1 + R_2 = \frac{V_{DD}}{I_{Bias}} = \frac{10V}{2\mu A} = 5M\Omega$$

$$V_{EQ} = \frac{R_1}{R_1 + R_2} V_{DD} \rightarrow R_1 = (R_1 + R_2) \frac{V_{EQ}}{V_{DD}} = 5M\Omega \frac{4V}{10V} = 2M\Omega$$

$$R_2 = 5M\Omega - R_1 = 3M\Omega \quad | \quad R_{EQ} = R_1 \parallel R_2 = 1.2M\Omega$$

Page 274 Should refer to Fig. 5.46

$$V_{GS} = 4 - 39000I_D \quad V_{SB} = 39000I_D \quad V_{TN} = 1 + 0.75(\sqrt{V_{SB} + 0.6} - \sqrt{0.6}) \quad I_D = \frac{25\mu A}{2}(V_{GS} - V_{TN})^2$$

Spreadsheet iteration yields $I_D = 28.2 \mu A$.

Page 276

$$I_G = 0 \rightarrow V_{GS} = V_{DS} = V_{DD} - I_D R_D$$

$$\text{Eqn. 5.87: } K_n R_D = (50 \times 10^{-6})(75 \times 10^3) = 3.75V$$

$$V_{FS} = \left(1 - \frac{1}{3.75} \pm \sqrt{\left(1 - \frac{1}{3.75} \right)^2 + \frac{2(10)}{3.75} - 1^2} \right) V = 2.940V$$


$$I_D = \frac{50\mu A}{2} (2.940 - 1)^2 = 94.13 \mu A$$

Page 279 - Use equation set on page 229
Assume saturation region operation.

$$10 - 6 = \frac{25 \times 10^{-6} (62 \times 10^4)}{2} (V_{GS} + 1)^2 - V_{GS} \rightarrow V_{GS}^2 + 0.710 V_{GS} - 4.161 = 0 \rightarrow V_{GS} = -2.426V, +1.716V$$

$$I_D = \frac{25 \times 10^{-6}}{2} (-2.426 + 1)^2 = 25.4 \mu A \quad | \quad V_{DS} = -[10 - 137k\Omega(25.4\mu A)] = -6.52 V$$

Saturation region is correct. | Q-Point : (25.4 μA , -6.52 V)

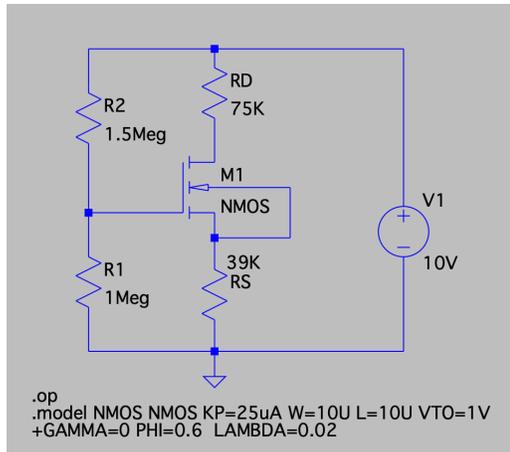

```

EX-P279.log
Circuit: * /Users/microman/Documents/LTspice/P5-171.asc
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- MOSFET Transistors ---
Name:      m1
Model:     nmos
Id:        3.59e-05
Vgs:       2.60e+00
Vds:       5.91e+00
Vbs:       0.00e+00
Vth:       1.00e+00
Vdsat:     1.60e+00
Gm:        4.48e-05
Gds:       6.41e-07
Gmb:       0.00e+00
Cbd:       0.00e+00
Cbs:       0.00e+00
Cgs0v:    0.00e+00
Cgd0v:    0.00e+00
Cgs0vov:  0.00e+00
Cgd0vov:  0.00e+00
Cgs:       0.00e+00
Cgd:       0.00e+00
Cgb:       0.00e+00

Operating Bias Point Solution:
V(n002)    7.31879  voltage
V(n004)    4        voltage
V(n003)    1.39839  voltage
V(n001)    10       voltage
Id(M1)    3.58561e-05 device_current
Ig(M1)    0         device_current
Ib(M1)    -5.9224e-12 device_current
Is(M1)    -3.58561e-05 device_current
I(R1)     3.58561e-05 device_current
I(R2)     4e-06     device_current
I(Rs)     3.58561e-05 device_current
I(V1)     -3.98561e-05 device_current

```

Page 280

$$K_R = 1: V_{GSN} = \frac{2.5 + \sqrt{1(0.6) - 0.6}}{1 + \sqrt{1}} = 1.25 V \quad | \quad I_D = \frac{50}{2} (1.25 - 0.6)^2 = 10.6 \mu A$$

$$K_R = 5: V_{GSN} = \frac{2.5 + \sqrt{5(0.6) - 0.6}}{1 + \sqrt{5}} = 1.00 V \quad | \quad I_D = \frac{50}{2} (1.00 - 0.6)^2 = 4.00 \mu A$$

$$K_R = 5: V_{GSN} = \frac{2.5 + \sqrt{0.2(0.6) - 0.6}}{1 + \sqrt{0.2}} = 1.50 V \quad | \quad I_D = \frac{50}{2} (1.50 - 0.6)^2 = 20.3 \mu A$$

Page 286

(a) $V_{DS} = 3\text{ V}$, $V_{GS} - V_P = -2 - (-3.5) = +1.5\text{ V}$. The transistor is pinched off.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 1\text{mA} \left[1 - \left(\frac{-2\text{V}}{-3.5\text{V}}\right)\right]^2 = 184\ \mu\text{A} \quad | \quad \text{Pinchoff requires } V_{DS} \geq V_{GS} - V_P = +1.5\text{ V}$$

(b) $V_{DS} = 6\text{ V}$, $V_{GS} - V_P = -1 - (-3.5) = +2.5\text{ V}$. The transistor is pinched off.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 1\text{mA} \left[1 - \left(\frac{-1\text{V}}{-3.5\text{V}}\right)\right]^2 = 510\ \mu\text{A} \quad | \quad \text{Pinchoff requires } V_{DS} \geq V_{GS} - V_P = +2.5\text{ V}$$

(c) $V_{DS} = 0.5\text{ V}$, $V_{GS} - V_P = -2 - (-3.5) = +1.5\text{ V}$. The transistor is in the triode region.

$$I_D = \frac{2I_{DSS}}{V_P^2} \left(V_{GS} - V_P - \frac{V_{DS}}{2}\right) V_{DS} = \frac{2(1\text{mA})}{(-3.5)^2} \left(-2 + 3.5 - \frac{0.5}{2}\right) 0.5 = 51.0\ \mu\text{A}$$

Pinchoff requires $V_{DS} \geq V_{GS} - V_P = +1.5\text{ V}$

(a) $V_{DS} = 0.5\text{ V}$, $V_{GS} - V_P = -2 - (-4) = +2\text{ V}$. The transistor is in the triode region.

$$I_D = \frac{2I_{DSS}}{V_P^2} \left(V_{GS} - V_P - \frac{V_{DS}}{2}\right) V_{DS} = \frac{2(0.2\text{mA})}{(-4)^2} \left(-2 + 4 - \frac{0.5}{2}\right) 0.5 = 21.9\ \mu\text{A}$$

(b) $V_{DS} = 6\text{ V}$, $V_{GS} - V_P = -1 - (-4) = +3\text{ V}$. The transistor is pinched off.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 0.2\text{mA} \left[1 - \left(\frac{-1\text{V}}{-4\text{V}}\right)\right]^2 = 113\ \mu\text{A}$$

Page 288

(a) $V_{DS} = -3\text{ V}$, $V_{GS} - V_P = 3 - 4 = -1\text{ V}$. The transistor is pinched off.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 2.5\text{mA} \left[1 - \frac{3\text{V}}{4\text{V}}\right]^2 = 156\ \mu\text{A} \quad | \quad \text{Pinchoff requires } V_{DS} \leq V_{GS} - V_P = -1\text{ V}$$

(b) $V_{DS} = -6\text{ V}$, $V_{GS} - V_P = 1 - (4) = -3\text{ V}$. The transistor is pinched off.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 2.5\text{mA} \left[1 - \frac{1\text{V}}{4\text{V}}\right]^2 = 1.41\text{ mA} \quad | \quad \text{Pinchoff requires } V_{DS} \leq V_{GS} - V_P = -3\text{ V}$$

(c) $V_{DS} = -0.5\text{ V}$, $V_{GS} - V_P = 2 - (4) = -2\text{ V}$. The transistor is in the triode region.

$$I_D = \frac{2I_{DSS}}{V_P^2} \left(V_{GS} - V_P - \frac{V_{DS}}{2}\right) V_{DS} = \frac{2(2.5\text{mA})}{4^2} \left(2 - 4 - \frac{-0.5}{2}\right) (-0.5) = 273\ \mu\text{A}$$

Pinchoff requires $V_{DS} \leq V_{GS} - V_P = -2\text{ V}$

Page 289

$$\text{BETA} = \frac{I_{DSS}}{V_P^2} = \frac{2.5 \text{ mA}}{(-2)^2} = 0.625 \text{ mA} \quad | \quad \text{VTO} = V_P = -2 \text{ V} \quad | \quad \text{LAMBDA} = \lambda = 0.025 \text{ V}^{-1}$$

$$\text{BETA} = \frac{I_{DSS}}{V_P^2} = \frac{5 \text{ mA}}{2^2} = 1.25 \text{ mA} \quad | \quad \text{VTO} = V_P = 2 \text{ V} \quad | \quad \text{LAMBDA} = \lambda = 0.02 \text{ V}^{-1}$$

Page 290

$$\text{VTO} = V_P = -5 \text{ V} \quad | \quad \text{BETA} = \frac{I_{DSS}}{V_P^2} = \frac{5 \text{ mA}}{(-5)^2} = 0.2 \text{ mA} \quad | \quad \text{LAMBDA} = \lambda = 0.02 \text{ V}^{-1}$$

Page 291

$$V_{GS} = V_G - V_S = -I_G R_G - I_S R_S = 0 - I_D R_S = -I_D R_S$$

$$V_{GS} = -\frac{K_n}{2} (V_{GS} - V_{TN})^2 R_S = -\frac{K_n}{2} V_{TN}^2 R_S \left(\frac{V_{GS}}{V_{TN}} - 1 \right)^2 = -I_{DSS} R_S \left(1 - \frac{V_{GS}}{V_P} \right)^2 \quad \text{for } I_{DSS} = \frac{K_n}{2} V_{TN}^2 \quad \text{and } V_P = V_{TN}$$

$$V_{GS} = -\frac{0.4 \text{ mA}}{2} (-5)^2 (1 \text{ k}\Omega) \left(1 - \frac{V_{GS}}{-5} \right)^2 = 5 \left(1 + \frac{V_{GS}}{5} \right)^2 \rightarrow V_{GS}^2 - 15V_{GS} + 25 = 0 \quad \text{and the rest is identical.}$$

Assuming pinchoff, $I_D = 1.91 \text{ mA}$ and $V_{DS} = 9 - 1.91 \text{ mA}(2 \text{ k}\Omega + 1 \text{ k}\Omega) = 3.27 \text{ V}$.

$V_{GS} - V_P = 3.09 \text{ V}$, $V_{DS} > V_{GS} - V_P$, and pinchoff is correct.

$$\text{Assuming pinchoff, } V_{GS} = -I_{DSS} R_S \left(1 - \frac{V_{GS}}{V_P} \right)^2 = -(5 \times 10^{-3})(2 \times 10^3) \left(1 + \frac{V_{GS}}{5} \right)^2 \rightarrow V_{GS}^2 + 12.5V_{GS} + 25 = 0$$

$$V_{GS} = -2.5 \text{ V} \quad | \quad I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 5 \text{ mA} \left(1 - \frac{-2.5}{-5} \right)^2 = 1.25 \text{ mA}$$

$$V_{DS} = 12 - 1.25 \text{ mA}(2 \text{ k}\Omega + 2 \text{ k}\Omega) = 7.00 \text{ V}$$

$V_{GS} - V_P = -2.5 - (-5) = +2.5 \text{ V}$, $V_{DS} > V_{GS} - V_P$, and pinchoff is correct. Q-Point: (1.25 mA, 7.00 V)

$$(a) \quad V_G = -I_G R_G = -10 \text{ nA}(680 \text{ k}\Omega) = -6.80 \text{ mV}$$

$$V_{GS} = V_G - V_S = -I_G R_G - I_{DSS} R_S \left(1 - \frac{V_{GS}}{V_P} \right)^2 = -0.00680 - (5 \times 10^{-3})(10^3) \left(1 + \frac{V_{GS}}{5} \right)^2 \rightarrow V_{GS}^2 - 15V_{GS} + 25 = 0$$

The value of V_G is insignificant with respect to the constant term of 25. So the answers are the same to 3 significant digits.

(b) $V_G = -I_G R_G = -1 \mu\text{A}(680 \text{ k}\Omega) = 0.680 \text{ V}$ and now cannot be neglected.

$$V_{GS} = V_G - V_S = -I_G R_G - I_{DSS} R_S \left(1 - \frac{V_{GS}}{V_P} \right)^2 = -0.680 - (5 \times 10^{-3})(10^3) \left(1 + \frac{V_{GS}}{5} \right)^2 \rightarrow V_{GS}^2 - 15V_{GS} + 28.4 = 0$$

$$V_{GS} = -2.226 \text{ V} \quad | \quad I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 5 \text{ mA} \left(1 - \frac{-2.226}{-5} \right)^2 = 1.54 \text{ mA}$$

$$V_{DS} = 12 - 1.54 \text{ mA}(2 \text{ k}\Omega + 1 \text{ k}\Omega) = 7.38 \text{ V} \quad | \quad \text{Q-Point:}(1.54 \text{ mA}, 7.38 \text{ V})$$