

Microelectronic Circuit Design

Sixth Edition - Part II

Solutions to Exercises

CHAPTER 6

Page 317

$$(a) A_p = |A_v||A_i| = 4 \times 10^4 (2.75 \times 10^8) = 1.10 \times 10^{13}$$

$$(b) V_o = \sqrt{2P_o R_L} = \sqrt{2(20W)(16\Omega)} = 25.3 \text{ V} \quad | \quad A_v = \frac{V_o}{V_i} = \frac{25.3V}{0.005V} = 5.06 \times 10^3$$

$$I_o = \frac{V_o}{R_L} = \frac{25.3V}{16\Omega} = 1.58 \text{ A} \quad | \quad I_i = \frac{V_i}{R_s + R_m} = \frac{0.005V}{10k\Omega + 20k\Omega} = 0.167 \mu\text{A} \quad | \quad A_i = \frac{I_o}{I_i} = \frac{1.58A}{0.167\mu\text{A}} = 9.48 \times 10^6$$

$$A_p = \frac{P_o}{P_s} = \frac{25.3V(1.58A)}{0.005V(0.167\mu\text{A})} = 4.79 \times 10^{10} \quad | \quad \text{Checking: } A_p = (5.06 \times 10^3)(9.48 \times 10^6) = 4.80 \times 10^{10}$$

Page 318

$$A_{vdB} = 20\log(5060) = 74.1 \text{ dB} \quad | \quad A_{idB} = 20\log(9.48 \times 10^6) = 140 \text{ dB} \quad | \quad A_{pdB} = 20\log(4.79 \times 10^{10}) = 107 \text{ dB}$$

$$A_{vdB} = 20\log(1210) = 61.7 \text{ dB} \quad | \quad A_{idB} = 20\log(2.51 \times 10^6) = 128 \text{ dB} \quad | \quad A_{pdB} = 20\log(3.03 \times 10^9) = 94.8 \text{ dB}$$

$$A_{vdB} = 20\log(1210) = 61.7 \text{ dB}$$

Page 325

$$G_{in} = g_{11} = \frac{1}{20k\Omega + 76(50k\Omega)} = 0.262 \mu\text{S} \quad | \quad A = g_{21} = 0.262\mu\text{S}(76)(50k\Omega) = 0.995$$

$$R_{out} = g_{22} = \left[\frac{1}{50k\Omega} + \frac{1}{20k\Omega} + \frac{75}{20k\Omega} \right]^{-1} = 262 \Omega \quad | \quad g_{12} = -\frac{g_{22}}{(20k\Omega)} = -\frac{262\Omega}{(20k\Omega)} = -0.0131$$

$$R_{in} = \frac{1}{g_{11}} = 3.82 M\Omega \quad | \quad A = g_{21} = 0.995 \quad | \quad R_{out} = \frac{1}{g_{22}} = 262 \Omega$$

Page 326

$$R_{in} = \infty \rightarrow I_1 = 0 \quad | \quad I_o \neq 0 \rightarrow A_i = \infty$$

$$A_p = A_v A_i = A_v \left(A_v \frac{R_I + R_{in}}{R_L} \right) = A_v^2 \left(\frac{R_I + R_{in}}{R_L} \right)$$

$$V_o = \sqrt{2PR_L} = \sqrt{2(100W)(8\Omega)} = 40 \text{ V} \quad | \quad V_o = AV_i \left(\frac{R_{in}}{R_I + R_{in}} \right) \left(\frac{R_L}{R_{out} + R_L} \right)$$

$$A = \frac{V_o}{V_i} \left(\frac{R_I + R_{in}}{R_{in}} \right) \left(\frac{R_{out} + R_L}{R_L} \right) = \frac{40V}{0.001V} \left(\frac{5k\Omega + 50k\Omega}{50k\Omega} \right) \left(\frac{0.5\Omega + 8\Omega}{8\Omega} \right) = 4.68 \times 10^4$$

$$A_{db} = 20 \log(4.68 \times 10^4) = 93.4 \text{ dB} \quad | \quad P = \frac{I_o^2}{2} R_{out} = \left(\frac{40V}{8\Omega} \right)^2 \frac{0.5\Omega}{2} = 6.25 \text{ W}$$

$$A_i = \frac{I_o}{I_i} = \frac{I_o}{V_i} (R_I + R_{in}) = \frac{5V}{0.001V} (5k\Omega + 50k\Omega) = 2.75 \times 10^8$$

$$A_{db} = 20 \log(2.75 \times 10^8) = 169 \text{ dB}$$

$$A = \frac{40V}{0.001V} \left(\frac{5k\Omega + 50k\Omega}{5k\Omega} \right) \left(\frac{8\Omega + 8\Omega}{8\Omega} \right) = 1.6 \times 10^5 \quad | \quad A_{db} = 20 \log(1.6 \times 10^5) = 104 \text{ dB}$$

$$P = \frac{I_o^2}{2} R_{out} = \left(\frac{40V}{8\Omega} \right)^2 \frac{8\Omega}{2} = 100 \text{ W!} \quad | \quad A_i = \frac{5V}{0.001V} (5k\Omega + 50k\Omega) = 5 \times 10^7 \quad (154 \text{ dB})$$

Page 331

(a) The constant slope region spanning a maximum input range is between $-0.5 \text{ V} \leq v_{ID} \leq 1.5 \text{ V}$,

and the bias voltage V_{ID} should be centered in this range: $V_{ID} = \frac{1.5 + (-0.5)}{2} V = +0.5 \text{ V}$.

$$v_{ID} = V_{ID} + v_{id} \quad | \quad -0.5V \leq 0.5V + v_{id} \rightarrow v_{id} \geq -1 \text{ V} \quad \text{and} \quad 0.5V + v_{id} \leq 1.5 \rightarrow v_{id} \leq +1 \text{ V}$$

$$\therefore -1 \text{ V} \leq v_{id} \leq +1 \text{ V} \quad \text{or} \quad |v_{id}| \leq 1 \text{ V} \quad \text{and} \quad |v_o| \leq 10 \text{ V}$$

(b) For $V_{ID} = -1 \text{ V}$, the slope of the voltage transfer characteristics is zero, so $A = 0$.

$$v_o = 10(v_{ID} - 0.5V) = 10(-0.5 + 0.25 + 0.75 \sin 1000\pi t) = (-2.5 + 7.5 \sin 1000\pi t) \text{ V} \quad | \quad V_o = -2.5 \text{ V}$$

Page 336

$$A_v(s) = -\frac{2\pi \times 10^6}{s + 5000\pi} = \frac{-400}{1 + \frac{s}{5000\pi}} \rightarrow A_{mid} = -400 \quad | \quad f_H = \frac{5000\pi}{2\pi} = 2.50 \text{ kHz}$$

$$BW = f_H - f_L = 2.50 \text{ kHz} - 0 = 2.50 \text{ kHz} \quad | \quad GBW = (400)(2.50 \text{ kHz}) = 1.00 \text{ MHz}$$

Page 338

$$f_H = \frac{1}{2\pi} \frac{1}{(1k\Omega \parallel 100k\Omega)(200pF)} = 804 \text{ kHz}$$

Page 339

$$A_v(s) = \frac{250}{1 + \frac{250\pi}{s}} \quad | \quad A_o = 250 \quad | \quad f_L = \frac{250\pi}{2\pi} = 125 \text{ Hz} \quad | \quad f_H = \infty \quad | \quad BW = \infty - 125 = \infty$$

Page 341

$$f_L = \frac{1}{2\pi} \frac{1}{(1k\Omega \parallel 100k\Omega)(0.1\mu F)} = 15.8 \text{ Hz}$$

Page 343

$$A_v(j1) = 50 \frac{-1+4}{-1+2+j2} = \frac{150}{1+j2} \quad | \quad |A_v(j1)| = \frac{150}{\sqrt{(1)^2 + (2)^2}} = 67.08$$

$$A_{\text{v dB}} = 20 \log(67.08) = 36.5 \text{ dB} \quad | \quad \angle A_v(j1) = \angle(50) + \angle(3) - \tan^{-1}\left[\frac{2}{1}\right] = 0 + 0 - 63.4^\circ = -63.4^\circ$$

$$A_v(j5) = 50 \frac{-25+4}{-25+2+j10} = \frac{1050}{23-j10} \quad | \quad |A_v(j5)| = \frac{1050}{\sqrt{(-23)^2 + (10)^2}} = 41.87$$

$$A_{\text{v dB}} = 20 \log(41.87) = 32.4 \text{ dB} \quad | \quad \angle A_v(j5) = \angle(1050) + -\tan^{-1}\left[\frac{10}{-23}\right] = 0 - (-23.5^\circ) = +23.5^\circ$$

$$A_v(j\omega) = \frac{20}{1+j\frac{0.1\omega}{1-\omega^2}} \quad | \quad |A_v(j0.95)| = \frac{20}{\sqrt{1^2 + \frac{(0.1)^2(0.95^2)}{(1-0.95^2)^2}}} = 14.3$$

$$\angle A_v(j0.95) = \angle 20 - \tan^{-1}\left[\frac{0.1(0.95)}{1-0.95^2}\right] = 0 - (44.3^\circ) = -44.3^\circ$$

$$|A_v(j1)| = \frac{20}{\sqrt{1^2 + \frac{(0.1)^2(1^2)}{(1-1^2)^2}}} = 0 \quad | \quad \angle A_v(j1) = \angle 20 - \tan^{-1}\left[\frac{0.1(1)}{1-1^2}\right] = 0 - (90^\circ) = -90.0^\circ$$

$$|A_v(j1.1)| = \frac{20}{\sqrt{1^2 + \frac{(0.1)^2(1.1^2)}{(1-1.1^2)^2}}} = 17.7 \quad | \quad \angle A_v(j1.1) = \angle 20 - \tan^{-1}\left[\frac{0.1(1.1)}{1-1.1^2}\right] = 0 - (-27.6^\circ) = +27.6^\circ$$

$$(i) \quad A_v(s) = \frac{-400}{\left(1+\frac{100}{s}\right)\left(1+\frac{s}{50000}\right)} \quad | \quad A_o = 400 \text{ or } 52 \text{ dB}$$

$$f_L = \frac{100}{2\pi} = 15.9 \text{ Hz} \quad | \quad f_H = \frac{50000}{2\pi} = 7.96 \text{ kHz} \quad | \quad BW = 7960 - 15.9 = 7.94 \text{ kHz}$$

CHAPTER 7

Page 355

$$(a) \text{At the Q-point: } \beta_F = \frac{I_C}{I_B} = \frac{1.5mA}{15\mu A} = 100$$

$$(b) I_S = \frac{I_C}{\exp\left(\frac{V_{BE}}{V_T}\right)} = \frac{1.5mA}{\exp\left(\frac{0.700V}{0.0259V}\right)} = 2.74 fA$$

$$(c) R_m = \frac{v_{be}}{i_b} = \frac{8mV}{5\mu A} = 1.6 k\Omega \quad (d) \text{Yes. With the given applied signal, the smallest value of } v_{CE} \text{ is}$$

$$v_{CE}^{\min} = 5V - 0.5mA(3.3k\Omega) = 3.35 V \text{ which exceeds } v_{BE} = 0.708 V. \quad (e) A_{vdB} = 20 \log| -206 | = 46.3 dB$$

Page 356

(a) No: $v_{DS}^{\min} \cong 2.7V$ with $v_{GS} - V_{TN} = 4 - 1 = 3V$, so the transistor has entered the triode region.

(b) Choose two points on the i-v characteristics. For example,

$$1.56mA = \frac{K_n}{2}(3.5 - V_{TN})^2 \quad \text{and} \quad 1.0mA = \frac{K_n}{2}(3.0 - V_{TN})^2.$$

Solving for K_n and V_{TN} yields $500 \frac{\mu A}{V^2}$ and 1 V respectively.

$$(c) A_{vdB} = 20 \log| -4.13 | = 12.3 dB$$

Page 357

$$V_{EQ} = \frac{10k\Omega}{10k\Omega + 30k\Omega} 12V = 3.00 V \quad | \quad R_{EQ} = 10k\Omega \parallel 30k\Omega = 7.5 k\Omega$$

$$I_C = \beta_F I_B = \beta_F \frac{V_{EQ} - V_{BE}}{R_{EQ} + (\beta_F + 1)R_4} = 100 \frac{3.0V - 0.7V}{7.5k\Omega + (101)(1.5k\Omega)} = 1.45 mA$$

$$V_{CE} = 12 - 4300I_C - 1500I_E = 12 - 4300(1.45mA) - 1500\left(\frac{101}{100}\right)(1.45mA) = 3.57 V$$

$$V_B = V_{EQ} - I_B R_{EQ} = 3.00 - \frac{1.45mA}{100}(7.5k\Omega) = 2.89 V$$

Page 358

$$v_C(t) = V_C + v_C = (5.8 - 1.1 \sin 2000\pi t) V \quad | \quad v_E(t) = V_E + 0 = 1.45mA \left(\frac{101}{100} \right) (1.5k\Omega) = 2.20 V$$

$$|i_c| = \frac{1.1V}{4.3k\Omega} = 0.256mA \quad | \quad \angle i_c = 180^\circ \quad | \quad i_c(t) = -0.26 \sin 2000\pi t mA \quad | \quad v_B(t) = V_B + v_b(t)$$

$$V_B = V_{EQ} - I_B R_{EQ} = 3.00 - \frac{1.45mA}{100} (7.5k\Omega) = 2.89 V \quad | \quad v_B(t) = (2.89 + 0.005 \sin 2000\pi t) V$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2000\pi(500\mu F)} = 0.318 \Omega \quad | \quad X_C \ll R_{in}$$

Page 361

$$R_B = 20k\Omega \parallel 62k\Omega = 15.1 k\Omega \quad | \quad R_L = 8.2k\Omega \parallel 100k\Omega = 7.58 k\Omega$$

Page 365

$$r_d = \frac{V_T}{I_D + I_S} \quad | \quad r_d = \frac{0.025V}{1fA} = 25.0 T\Omega \quad | \quad r_d = \frac{0.025V}{50\mu A} = 500 \Omega$$

$$r_d = \frac{0.025V}{2mA} = 12.5 \Omega \quad | \quad r_d = \frac{0.025V}{3A} = 8.33 m\Omega$$

$$r_d = \frac{0.025V}{1.5mA} = 16.7 \Omega \quad | \quad \frac{kT}{q} = \left(8.62 \times 10^{-5} \frac{V}{K} \right) (373K) = 0.0322 V \quad | \quad r_d = \frac{0.0322V}{1.5mA} = 21.4 \Omega$$

Page 370

$$g_m = 40I_C = 40(50\mu A) = 2.00 \text{ mS} \quad | \quad r_\pi = \frac{\beta_o}{g_m} = \frac{75}{2 \text{ mS}} = 37.5 \text{ k}\Omega$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{60V + 5V}{50\mu A} = 1.30 \text{ M}\Omega \quad | \quad \mu_f = g_m r_o = 2 \text{ mS}(1.30 \text{ M}\Omega) = 2600$$

$$g_m = 40I_C = 40(250\mu A) = 10.0 \text{ mS} \quad | \quad r_\pi = \frac{\beta_o}{g_m} = \frac{50}{10 \text{ mS}} = 5.00 \text{ k}\Omega$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{75V + 15V}{250\mu A} = 360 \text{ k}\Omega \quad | \quad \mu_f = g_m r_o = 10 \text{ mS}(360 \text{ k}\Omega) = 3600$$

The slope of the output characteristics is zero, so $V_A = \infty$ and $r_o = \infty$.

$$\beta_{FO} = \frac{\beta_F}{1 + \frac{V_{CE}}{V_A}} = \beta_F = \frac{I_C}{I_B} = \frac{1.5mA}{15\mu A} = 100 \quad | \quad g_m = \frac{\Delta i_C}{\Delta v_{BE}} = \frac{0.5mA}{8mV} = 62.5 \text{ mS}$$

$$\beta_o = \frac{\Delta i_C}{\Delta i_B} = \frac{500\mu A}{5\mu A} = 100 \quad | \quad r_\pi = \frac{\beta_o}{g_m} = \frac{100}{62.5 \text{ mS}} = 1.60 \text{ k}\Omega \quad | \quad r_\pi = \frac{\Delta v_{BE}}{\Delta i_B} = \frac{8mV}{0.5mA/100} = 1.60 \text{ k}\Omega$$

$$r_\mu = \beta_o r_o = 100r_o \quad | \quad \text{Multiply each entry by 100.}$$

Page 380

$A_{vt} = -g_m R_L = -9.80 mS (18 k\Omega) = -176$ | Ten percent of the input signal is being lost by voltage division between source resistance R_i and the amplifier input resistance.

Assume the Q-point remains constant.

$$(a) R_{ib} = r_\pi = \frac{125}{9.80 mS} = 12.8 k\Omega \quad | \quad A_v = -9.80 mS (18 k\Omega) \left(\frac{104 k\Omega \| 12.8 k\Omega}{1 k\Omega + 104 k\Omega \| 12.8 k\Omega} \right) = -162$$

$$(b) R_L^{\max} = 1.1 (18 k\Omega) = 19.8 k\Omega \quad | \quad R_L^{\min} = 0.9 (18 k\Omega) = 16.2 k\Omega$$

$$A_v^{\min} = -9.80 mS (16.2 k\Omega) \left(\frac{104 k\Omega \| 10.2 k\Omega}{1 k\Omega + 104 k\Omega \| 10.2 k\Omega} \right) = -143$$

$$A_v^{\max} = A_v^{\min} \left(\frac{19.8 k\Omega}{16.2 k\Omega} \right) = -143 \left(\frac{19.8 k\Omega}{16.2 k\Omega} \right) = -175$$

$$\text{Checking: } A_v^{\min} = A_v^{\text{nom}} \left(\frac{16.2 k\Omega}{18 k\Omega} \right) = -159 (0.9) = -143 \quad | \quad A_v^{\max} = A_v^{\text{nom}} \left(\frac{19.8 k\Omega}{18 k\Omega} \right) = -159 (1.1) = -175$$

$$(c) V_{CE} = 12V - 22 k\Omega I_C - 13 k\Omega I_E = 12V - 0.275 mA \left(22 k\Omega + \frac{101}{100} 13 k\Omega \right) = 2.34 V$$

$$g_m = 40 (0.275 mA) = 11.0 mS \quad | \quad R_{ib} = r_\pi = \frac{100}{11.0 mS} = 9.09 k\Omega$$

$$A_v = -11.0 mS (18 k\Omega) \left(\frac{104 k\Omega \| 9.09 k\Omega}{1 k\Omega + 104 k\Omega \| 9.09 k\Omega} \right) = -177$$

$$A_v^{CE} \cong -10 V_{CC} = -10 (20) = -200 \quad | \quad g_m = 40 I_C = 40 (100 \mu A) = 4.00 mS \quad | \quad R_{ib} = r_\pi = \frac{\beta_o}{g_m} = \frac{100}{4 mS} = 25 k\Omega$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{50V + 10V}{100 \mu A} = 600 k\Omega \quad | \quad \mu_f = g_m r_o = 4 mS (600 k\Omega) = 2400$$

$$A_v = -g_m (R_C \| r_o) \frac{R_B \| R_{ib}}{R_I + R_B \| R_{ib}} = -4.00 mS (100 k\Omega \| 600 k\Omega) \left(\frac{150 k\Omega \| 25 k\Omega}{5 k\Omega + 150 k\Omega \| 25 k\Omega} \right) = -278$$

Page 381

$$V_{EQ} = \frac{160k\Omega}{160k\Omega + 300k\Omega} 12V = 4.17 V \quad | \quad R_{EQ} = 160k\Omega \parallel 300k\Omega = 104 k\Omega$$

$$I_C = \beta_F I_B = \beta_F \frac{V_{EQ} - V_{BE}}{R_{EQ} + (\beta_F + 1)R_E} = 100 \frac{4.17V - 0.7V}{104k\Omega + (101)(13k\Omega)} = 0.245 mA$$

$$V_{CE} = 12 - 22000I_C - 13000I_E = 12 - 22000(0.245mA) - 13000\left(\frac{101}{100}\right)(0.245mA) = 3.39 V$$

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CB}}{V_A}\right) \quad | \quad V_T = \frac{kT}{q} = \frac{1.38 \times 10^{-23}(300)}{1.6 \times 10^{-19}} = .025875 V$$

$$I_S = \frac{0.245mA}{\exp\left(\frac{0.7}{0.025875}\right)\left(1 + \frac{3.39 - 0.7}{75}\right)} = 422 fA$$

There is a units error in the previous equation: $I_S = 0.422 fA$!

Page 384

$$(a) g_m = \sqrt{2K_n I_D (1 + \lambda V_{DS})} = \sqrt{2(1mA/V^2)(0.25mA)[1 + 0.02(5)]} = 0.742 mS$$

$$r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} = \frac{50V + 5V}{250\mu A} = 220 k\Omega \quad | \quad \mu_f = g_m r_o = 0.742 mS (220k\Omega) = 163$$

$$g_m = \sqrt{2K_n I_D (1 + \lambda V_{DS})} = \sqrt{2(1mA/V^2)(5mA)[1 + 0.02(10)]} = 3.46 mS$$

$$r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} = \frac{50V + 10V}{5mA} = 12 k\Omega \quad | \quad \mu_f = g_m r_o = 3.46 mS (12k\Omega) = 41.5$$

(b) The slope of the output characteristics is zero, so $\lambda = 0$ and $r_o = \infty$.

$$\text{For the positive change in } v_{gs}, g_m = \frac{\Delta i_D}{\Delta v_{GS}} \cong \frac{2.1V}{0.5V} = 1.3 mS$$

Page 385

$$|v_{gs}| \leq 0.2(V_{GS} - V_{TN}) = 0.2 \sqrt{\frac{2I_D}{K_n}} = 0.2 \sqrt{\frac{2(25mA)}{2.0mA/V^2}} = 1.00 V \quad | \quad |v_{be}| \leq 0.005 V$$

Page 386

$$\eta = \frac{\gamma}{2\sqrt{V_{SB} + 2\phi_F}} = \frac{0.75}{2\sqrt{0 + 0.6}} = 0.48 \quad | \quad \eta = \frac{0.75}{2\sqrt{3 + 0.6}} = 0.20$$

Page 387

$$I_D = I_{DO} \exp\left(\frac{V_{GS} - V_{TN}}{nV_T}\right) \quad | \quad g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{I_D}{nV_T} \quad | \quad \frac{g_m}{I_D} = \frac{1}{nV_T} = \frac{1}{1.5V_T} = 25.8/V$$

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \quad | \quad g_m = \frac{\partial I_D}{\partial V_{BE}} = \frac{I_C}{V_T} \quad | \quad \frac{g_m}{I_D} = \frac{1}{V_T} = \frac{1}{V_T} = 38.8/V$$

$$S = nV_T \ln(10) = 1.5(0.0258mV) \ln(10) = 89.1 \text{ mV/dec}$$

Page 388

$$g_m = 2 \frac{\sqrt{I_{DSS} I_D (1 + \lambda V_{DS})}}{|V_P|} = 2 \frac{\sqrt{5mA (2mA) [1 + 0.02(5)]}}{|-2|} = 3.32 \text{ mS}$$

$$r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} = \frac{50V + 5V}{2mA} = 27.5 \text{ k}\Omega \quad | \quad \mu_f = g_m r_o = 3.32 \text{ mS} (27.5 \text{ k}\Omega) = 91.3$$

$$V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right) = -2V \left(1 - \sqrt{\frac{2mA}{5mA}} \right) = -0.735 \text{ V}$$

$$|V_{GS}| \leq 0.2(V_{GS} - V_P) = 0.2(-0.735 + 2) = 0.253 \text{ V}$$

Page 396

$$V_{EQ} = \frac{1.5M\Omega}{1.5M\Omega + 2.2M\Omega} 12V = 4.87 \text{ V} \quad | \quad R_{EQ} = 1.5M\Omega \parallel 2.2M\Omega = 892 \text{ k}\Omega$$

Neglect λ in hand calculations of the Q-point.

$$4.87 = V_{GS} + 12000I_D \quad | \quad 4.87 = V_{GS} + 12000 \left(\frac{5 \times 10^{-4}}{2} \right) (V_{GS} - 1)^2$$

$$3V_{GS}^2 - 5V_{GS} - 1.87 = 0 \rightarrow V_{GS} = 1.981 \text{ V} \quad | \quad I_D = 241 \mu A$$

$$V_{DS} = 12 - 22000I_D - 12000I_D = 3.81 \text{ V} \quad | \quad \text{Q-point: } (241 \mu A, 3.81 \text{ V})$$

The small-signal model appears in Fig. 7.27(c).

$$V_{GS} - V_{TN} \cong \sqrt{\frac{2(241\mu A)}{2 \times 10^{-3}}} = 0.491 \text{ V} \quad | \quad A_v^{CS} \cong -\frac{12V}{0.491V} = -24.4 \quad | \quad M = \frac{K_{n2}}{K_{n1}} = \frac{2 \times 10^{-3}}{5 \times 10^{-4}} = 4$$

$$V_{EQ} = \frac{1.5M\Omega}{1.5M\Omega + 2.2M\Omega} 12V = 4.87 V \quad | \quad R_{EQ} = 1.5M\Omega \| 2.2M\Omega = 892 k\Omega$$

Neglect λ in hand calculations of the Q-point.

$$4.87 = V_{GS} + 12000I_D \quad | \quad 4.87 = V_{GS} + 12000 \left(\frac{5 \times 10^{-4}}{2} \right) (V_{GS} - 1)^2$$

$$3V_{GS}^2 - 5V_{GS} - 1.87 = 0 \rightarrow V_{GS} = 1.981 V \quad | \quad I_D = 241 \mu A$$

$$V_{DS} = 12 - 22000I_D - 12000I_D = 3.81 V \quad | \quad \text{Q-point: } (241 \mu A, 3.81 V)$$

The small-signal model appears in Fig. 13.27(c).

$$V_{GS} - V_{TN} \cong \sqrt{\frac{2(241\mu A)}{2 \times 10^{-3}}} = 0.491 V \quad | \quad A_v^{CS} \cong -\frac{12V}{0.491V} = -24.4 \quad | \quad M = \frac{K_{n2}}{K_{n1}} = \frac{2 \times 10^{-3}}{5 \times 10^{-4}} = 4$$

Page 398

$$r_\pi = \frac{\beta_o V_T}{I_C} = \frac{100(0.025V)}{0.725mA} = 3.45 k\Omega \quad | \quad R_{in}^{CE} = R_B \| r_\pi = 104k\Omega \| 3.45k\Omega = 3.34 k\Omega$$

$$R_{in}^{CS} = 680k\Omega \| 1.0M\Omega = 405 k\Omega \quad | \quad V_{EQnew} = \frac{680k\Omega}{680k\Omega + 1M\Omega} V_{DD} = 0.405V_{DD}$$

$$V_{EQold} = \frac{1.5M\Omega}{1.5Mk\Omega + 2.2M\Omega} V_{DD} = 0.405V_{DD} \quad | \quad \text{No change. The gate voltages are the same.}$$

Page 404

From Ex. 13.6, $\mu_f = 230$ and $A_v = -20.3$. $|A_v| \ll \mu_f$

$$V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right) = -1V \left(1 - \sqrt{\frac{0.25mA}{1mA}} \right) = -0.500 V$$

$$|v_{gs}| \leq 0.2(V_{GS} - V_P) = 0.2(-0.5 + 1) = 0.100 V \quad | \quad |v_o| \leq 20.3(0.1) = 2.03 V$$

SPICE Results:

$$\lambda = 0 : \text{Q-point} = (250 \mu A, 4.75 V) \quad | \quad \lambda = 0.02 V^{-1} : \text{Q-point} = (257 \mu A, 4.54 V)$$

Page 406

$$I_C = 245 \mu A \quad | \quad V_{CE} = 3.39 V \quad | \quad I_E = 245 \mu A \left(\frac{66}{65} \right) = 249 \mu A$$

$$P_D = I_C V_{CE} + I_B V_{BE} = 245 \mu A (3.39 V) + \frac{245 \mu A}{65} (0.7 V) = 0.833 mW$$

$$P_S = V_{CC} (I_C + I_2) \quad | \quad I_2 = \frac{V_{CC} - V_B}{R_2} = \frac{V_{CC} - (V_{BE} + I_E R_E)}{R_2} = \frac{12 - 0.7 - 0.249 mA (13 k\Omega)}{300 k\Omega} = 26.9 \mu A$$

$$P_S = 12V (245 \mu A + 26.9 \mu A) = 3.26 mW$$

Page 407

$$P_D = I_D V_{DS} = 241 \mu A (3.81 V) = 0.918 mW \quad | \quad P_S = V_{DD} (I_D + I_2)$$

$$I_2 = \frac{V_{DD}}{R_1 + R_2} = \frac{12V}{1.5 M\Omega + 2.2 M\Omega} = 3.24 \mu A \quad | \quad P_S = 12V (241 \mu A + 3.24 \mu A) = 2.93 mW$$

Page 408

$$(a) V_M \leq \min [I_C R_C, (V_{CE} - V_{BE})] = \min [245 \mu A (22 k\Omega), (3.39 - 0.7) V] = 2.69 V$$

V_M is limited by the value of V_{CE} .

$$(b) V_M \leq \min [I_D R_D, (V_{DS} - V_{DSSAT})] = \min [241 \mu A (22 k\Omega), (3.81 - 0.982) V] = 2.83 V$$

Limited by the value of V_{DS} .

CHAPTER 8

Page 427

$$V_{EQ} = \frac{160k\Omega}{160k\Omega + 300k\Omega} 12V = 4.17 V \quad | \quad R_{EQ} = 160k\Omega \parallel 300k\Omega = 104 k\Omega$$

$$I_C = \beta_F I_B = \beta_F \frac{V_{EQ} - V_{BE}}{R_{EQ} + (\beta_F + 1)R_E} = 100 \frac{4.17V - 0.7V}{104k\Omega + (101)(13k\Omega)} = 0.245 mA$$

$$V_{CE} = 12 - 22000I_C - 13000I_E = 12 - 22000(0.245mA) - 13000\left(\frac{101}{100}\right)(0.245mA) = 3.39 V$$

$$g_m = 40I_C = 40(0.245mA) = 9.80 mS \quad | \quad r_\pi = \frac{\beta_o}{g_m} = \frac{100}{9.80mS} = 10.2 k\Omega$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{53.4V}{0.245mA} = 218 k\Omega \quad | \quad \mu_f = g_m r_o = 2140$$

$$V_{EQ} = \frac{1.5M\Omega}{1.5M\Omega + 2.2M\Omega} 12V = 4.87 V \quad | \quad R_{EQ} = 1.5M\Omega \parallel 2.2M\Omega = 892 k\Omega$$

Neglect λ in hand calculations of the Q-point.


$$4.87 = V_{GS} + 12000I_D \quad | \quad 4.87 = V_{GS} + 12000\left(\frac{5 \times 10^{-4}}{2}\right)(V_{GS} - 1)^2$$

$$3V_{GS}^2 - 5V_{GS} - 1.87 = 0 \rightarrow V_{GS} = 1.981 V \quad | \quad I_D = 241 \mu A$$

$$V_{DS} = 12 - 22000I_D - 12000I_D = 3.81 V \quad | \quad \text{Q-point: } (241 \mu A, 3.81 V)$$

$$g_m = \sqrt{2K_n I_D} = \sqrt{2\left(5 \times 10^{-4}\right)\left(2.41 \times 10^{-4}\right)} = 0.491 mS \quad | \quad r_o = \frac{\lambda^{-1} + V_{CE}}{I_C} = \frac{53.8V}{0.241mA} = 223 k\Omega$$

$$\mu_f = g_m r_o = 110$$

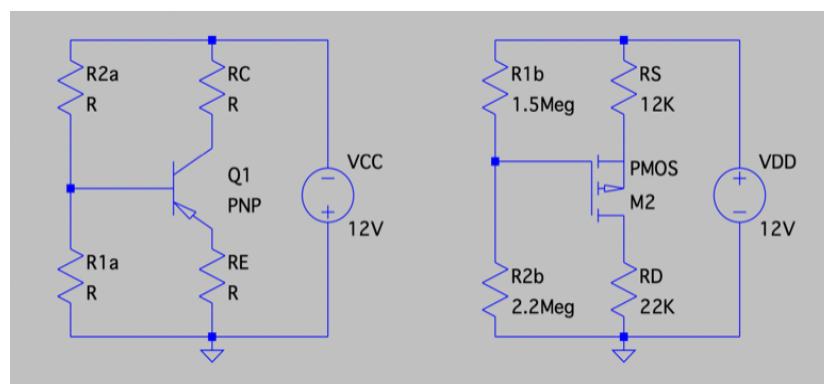

LTSpice Circuit

Page 428

$$R_B = 160k\Omega \parallel 300k\Omega = 104 \text{ } k\Omega \quad | \quad R_E = 3.00 \text{ } k\Omega \quad | \quad R_L = 22k\Omega \parallel 100k\Omega = 18.0 \text{ } k\Omega$$

$$R_G = 1.5M\Omega \parallel 2.2M\Omega = 892 \text{ } k\Omega \quad | \quad R_S = 2.00 \text{ } k\Omega \quad | \quad R_L = 22k\Omega \parallel 100k\Omega = 18.0 \text{ } k\Omega$$

$$R_B = 160k\Omega \parallel 300k\Omega = 104 \text{ } k\Omega \quad | \quad R_L = 13k\Omega \parallel 100k\Omega = 11.5 \text{ } k\Omega$$

$$R_G = 1.5M\Omega \parallel 2.2M\Omega = 892 \text{ } k\Omega \quad | \quad R_L = 12k\Omega \parallel 100k\Omega = 10.7 \text{ } k\Omega$$

Page 431

$$R_I = 2 \text{ } k\Omega \quad | \quad R_6 = 13 \text{ } k\Omega \quad | \quad R_L = 22k\Omega \parallel 100k\Omega = 18.0 \text{ } k\Omega$$

$$R_I = 2 \text{ } k\Omega \quad | \quad R_6 = 12 \text{ } k\Omega \quad | \quad R_L = 22k\Omega \parallel 100k\Omega = 18.0 \text{ } k\Omega$$

Page 442

$$(a) I_C \cong \frac{V_{EQ} - V_{BE}}{R_E + R_4} \quad \text{or} \quad I_C \propto \frac{1}{R_E + R_4} \quad | \quad I_C = 0.245mA \frac{13k\Omega}{R_E + R_4}$$

$$\text{For large } g_m R_E, \quad A_{vt}^{CE} = -\frac{g_m R_L}{1 + g_m R_E} \cong -\frac{R_L}{R_E} = -\frac{R_C \| R_3}{R_E}$$

$$\text{For } A_{vt}^{CE \max} \text{ make } R_C \text{ and } R_3 \text{ large and } R_E \text{ small.} \quad R_L = 1.1(22k\Omega) \| 1.1(100k\Omega) = 19.8 k\Omega$$

$$R_E = 0.9(3k\Omega) = 2.7 k\Omega \quad | \quad I_C = 0.245mA \frac{13k\Omega}{12.7k\Omega} = 0.251 mA \quad | \quad g_m = 40(0.251 mA) = 10.0 mS$$

$$r_\pi = \frac{\beta_o}{g_m} = \frac{100}{10.0mS} = 10.0 k\Omega \quad | \quad R_{iB} = 10.0k\Omega + 101(2.7k\Omega) = 283 k\Omega$$

$$A_v^{CE \max} = -\frac{10.0mS(19.8k\Omega)}{1 + 10.0mS(2.7k\Omega)} \left(\frac{104k\Omega \| 283k\Omega}{1k\Omega + 104k\Omega \| 283k\Omega} \right) = -6.98$$

$$\text{For } A_{vt}^{CE \min} \text{ make } R_C \text{ and } R_3 \text{ small and } R_E \text{ large.} \quad R_L = 0.9(22k\Omega) \| 0.9(100k\Omega) = 16.2 k\Omega$$

$$R_E = 1.1(3k\Omega) = 3.3 k\Omega \quad | \quad I_C = 0.245mA \frac{13k\Omega}{13.3k\Omega} = 0.239 mA \quad | \quad g_m = 40(0.239 mA) = 9.56 mS$$

$$r_\pi = \frac{\beta_o}{g_m} = \frac{100}{9.56mS} = 10.5 k\Omega \quad | \quad R_{iB} = 10.5k\Omega + 101(3.3k\Omega) = 344 k\Omega$$

$$A_v^{CE \ min} = -\frac{9.56mS(16.2k\Omega)}{1 + 9.56mS(3.3k\Omega)} \left(\frac{104k\Omega \| 344k\Omega}{1k\Omega + 104k\Omega \| 344k\Omega} \right) = -4.70$$

(b) Assume the collector current does not change.

$$r_\pi = \frac{\beta_o}{g_m} = \frac{125}{9.8mS} = 12.8 k\Omega \quad | \quad R_{iB} = 12.8k\Omega + 126(3.0k\Omega) = 391 k\Omega$$

$$A_v^{CE} = -\frac{9.80mS(18k\Omega)}{1 + 9.80mS(3k\Omega)} \left(\frac{104k\Omega \| 391k\Omega}{1k\Omega + 104k\Omega \| 391k\Omega} \right) = -5.73 \quad \text{The gain is essentially unchanged.}$$

$$(c) V_{CE} = V_{CC} - I_C R_C - I_E(R_E + R_4) = 12V - 0.275mA \left(22k\Omega + \frac{101}{100} 13k\Omega \right) = 2.34 V$$

2.34 V > 0.7 V Therefore the transistor is still in the active region.

$$g_m = 40(0.275mA) = 11.0 mS \quad | \quad r_\pi = \frac{\beta_o}{g_m} = \frac{100}{11mS} = 9.09 k\Omega \quad | \quad R_{iB} = 9.09k\Omega + 101(3.0k\Omega) = 312 k\Omega$$

$$A_v^{CE} = -\frac{11.0mS(18k\Omega)}{1 + 11.0mS(3k\Omega)} \left(\frac{104k\Omega \| 312k\Omega}{1k\Omega + 104k\Omega \| 312k\Omega} \right) = -5.75 \quad \text{The gain is essentially unchanged.}$$

Continued on the next page

Page 442 cont.

$$R_{iC} = 320k\Omega \left[1 + \frac{100(2k\Omega)}{(1k\Omega||104k\Omega) + 10.2k\Omega + 2k\Omega} \right] = 5.17 M\Omega \quad | \quad \mu_f R_E = 3140(2k\Omega) = 6.28 M\Omega$$

$$R_{iC} < \mu_f R_E \quad | \quad R_{out} = 5.17 M\Omega || 22k\Omega = 21.9 k\Omega \quad | \quad R_{out} \ll \mu_f R_E$$

$$\lim_{R_E \rightarrow \infty} R_{iC} = \lim_{R_E \rightarrow \infty} r_o \left(1 + \frac{\beta_o R_E}{R_{th} + r_\pi + R_E} \right) = r_o \left(1 + \frac{\beta_o R_E}{R_E} \right) = (\beta_o + 1)r_o$$

Page 445

$$R_{iB} = 10.2k\Omega + 101(1k\Omega) = 111k\Omega$$

$$A_v = -\frac{9.80mS(18k\Omega)}{1 + 9.80mS(1k\Omega)} \left(\frac{104k\Omega||111k\Omega}{1k\Omega + 104k\Omega||111k\Omega} \right) = -16.0 \quad | \quad R_4 = 13k\Omega - 1k\Omega = 12k\Omega.$$

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CB}}{V_A} \right) \quad | \quad V_T = \frac{kT}{q} = \frac{1.38 \times 10^{-23}(300)}{1.60 \times 10^{-19}} = .025875 V$$

$$I_S = \frac{0.245mA}{\exp\left(\frac{0.7}{0.025875}\right) \left(1 + \frac{3.39 - 0.7}{100} \right)} = 425fA$$

The answer above should be 0.425 fA.

$$A_v^{CE} \cong -10V_{CC} = -10(20) = -200 \quad | \quad g_m = 40I_C = 40(100\mu A) = 4.00 mS \quad | \quad R_{iB} = r_\pi = \frac{\beta_o}{g_m} = \frac{100}{4mS} = 25 k\Omega$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{50V + 10V}{100\mu A} = 600 k\Omega \quad | \quad \mu_f = g_m r_o = 4mS(600k\Omega) = 2400$$

$$A_v^{CE} = -g_m (R_C || r_o) \frac{R_B || R_{iB}}{R_I + R_B || R_{iB}} = -4.00mS(100k\Omega || 600k\Omega) \left(\frac{150k\Omega || 25k\Omega}{5k\Omega + 150k\Omega || 25k\Omega} \right) = -278$$

Page 451

$$V_{EQ} = \frac{1.5M\Omega}{1.5M\Omega + 2.2M\Omega} 12V = 4.87 V \quad | \quad R_{EQ} = 1.5M\Omega || 2.2M\Omega = 892 k\Omega$$

Neglect λ in hand calculations of the Q-point.

$$4.87 = V_{GS} + 12000I_D \quad | \quad 4.87 = V_{GS} + 12000 \left(\frac{5 \times 10^{-4}}{2} \right) (V_{GS} - 1)^2$$

$$3V_{GS}^2 - 5V_{GS} - 1.87 = 0 \rightarrow V_{GS} = 1.981 V \quad | \quad I_D = 241 \mu A$$

$$V_{DS} = 12 - 22000I_D - 12000I_D = 3.81 V \quad | \quad \text{Q-point: } (241 \mu A, 3.81 V)$$

$$A_{vdB}^{CS} = 20 \log |-4.50| = -13.1 dB$$

Page 452

$$R_{ib} = 10.2k\Omega + 101(1k\Omega) = 111k\Omega$$

$$A_v^{CE} = -\frac{9.80mS(18k\Omega)}{1+9.80mS(1k\Omega)} \left(\frac{104k\Omega \| 111k\Omega}{1k\Omega + 104k\Omega \| 111k\Omega} \right) = -16.0 \quad | \quad R_4 = 13k\Omega - 1k\Omega = 12k\Omega$$

$$A_v^{CS} = -\frac{0.503mS(18k\Omega)}{1+0.503mS(1k\Omega)} \left(\frac{892k\Omega}{1k\Omega + 892k\Omega} \right) = -6.02 \quad | \quad R_4 = 12k\Omega - 1k\Omega = 11k\Omega$$

$$(iii) \quad R_{ib} = 10.2k\Omega + 101(13k\Omega) = 1.32M\Omega$$

$$A_v^{CE} = -\frac{9.80mS(18k\Omega)}{1+9.80mS(13k\Omega)} \left(\frac{104k\Omega \| 1.32M\Omega}{1k\Omega + 104k\Omega \| 1.32M\Omega} \right) = -1.36 \quad | \quad A_v^{CE} \cong -\frac{R_L}{R_E + R_4} = -\frac{18k\Omega}{13k\Omega} = -1.38$$

$$A_v^{CS} = -\frac{0.503mS(18k\Omega)}{1+0.503mS(12k\Omega)} \left(\frac{892k\Omega}{1k\Omega + 892k\Omega} \right) = -1.29 \quad | \quad A_v^{CS} \cong -\frac{R_L}{R_S + R_4} = -\frac{18k\Omega}{12k\Omega} = -1.50$$

$$V_T = \left(\frac{1.381 \times 10^{-23}}{1.602 \times 10^{-19}} \frac{V}{K} \right) (273K + 27K) = 25.861mV \quad | \quad I_S = \frac{I_C}{\exp\left(\frac{V_{BE}}{V_T}\right)} = \frac{245\mu A}{\exp\left(\frac{0.700V}{0.025861V}\right)} = 0.430fA$$

$$g_m R_L = -9.80mS(18k\Omega) = -176 \quad | \quad A_v^{CE} \cong -\frac{18k\Omega}{3k\Omega} = -6.00 \quad | \quad 5.72 < 6.00$$

$$g_m R_L = -0.503mS(18k\Omega) = -9.05 \quad | \quad A_v^{CS} \cong -\frac{18k\Omega}{2k\Omega} = -9.00 \quad | \quad 4.50 < 9.00$$

Page 458

$$R_B = 160k\Omega \| 300k\Omega = 104k\Omega \quad | \quad R_{ib} \cong r_\pi(1 + g_m R_L) = \frac{2.5V}{0.25mA} [1 + 10mS(11.5k\Omega)] = 1.16M\Omega$$

$$v_i \leq 0.005V(1 + g_m R_L) \frac{R_I + R_B \| R_{ib}}{R_B \| R_{ib}} = 0.005V[1 + 10mS(11.5k\Omega)] \frac{2k\Omega + 95.4k\Omega}{95.4k\Omega} = 0.592V$$

$$v_i \leq 0.2(V_{GS} - V_{TN})(1 + g_m R_L) \frac{R_I + R_G}{R_G} = 0.2(1V)[1 + 0.5mS(10.7k\Omega)] \frac{2k\Omega + 892k\Omega}{892k\Omega} = 1.27V$$

Page 459

Add r_o either in parallel the dependent current source or in parallel with v_x .

$$i_x = \frac{v_x}{r_o} + \frac{v_x}{r_\pi + R_{TH}} - \beta_o i_x = \frac{v_x}{r_o} + \frac{v_x}{r_\pi + R_{TH}} - \beta_o \left(-\frac{v_x}{r_\pi + R_{TH}} \right)$$

$$\frac{i_x}{v_x} = \frac{1}{r_o} + \frac{\beta_o + 1}{r_\pi + R_{TH}} \quad | \quad R_{IE} = \frac{v_x}{i_x} = r_o \parallel \frac{r_\pi + R_{TH}}{\beta_o + 1} \cong r_o \parallel \left(\frac{1}{g_m} + \frac{R_{TH}}{\beta_o} \right) \cong \frac{1}{g_m}$$

Page 460

Replace v_x in Fig. 8.17 with a current source i_x . (r_o is also included but not in Eq. 8.68)

$$i_x = \frac{v_x}{r_o} \pm i_B - \beta_o i_B = \frac{v_x}{r_o} - (\beta_o + 1)i_B \quad | \quad v_x = -i_B(r_\pi + R_{TH})$$

$$i_x = v_x i_x = v_x \left(\frac{v_x}{r_o} + \frac{\beta_o + 1}{r_\pi + R_{TH}} \right) \quad | \quad R_{IE} = \frac{v_x}{i_x} = r_o \parallel \frac{r_\pi + R_{TH}}{\beta_o + 1} \cong r_o \parallel \left(\frac{1}{g_m} + \frac{R_{TH}}{\beta_o} \right) \cong \frac{1}{g_m}$$

Page 464

$$A_{vi} = \frac{2k\Omega + 892k\Omega}{892k\Omega} 0.971 = 0.973 \quad | \quad \frac{(0.491ms)R_L}{1 + (0.491ms)R_L} = 0.973 \rightarrow R_L = 73.4k\Omega$$

$R_6 \parallel 100k\Omega = 73.4k\Omega \rightarrow R_6 = 276 k\Omega$ | Note, however, that the 12 kΩ resistor can't simply be replaced with a 276 kΩ resistor because of Q-point problems.

$$R_{ib} = 10.2k\Omega + 10(13k\Omega) = 1.32M\Omega \quad | \quad R_{in}^{CC} = 104k\Omega \parallel 1.32M\Omega = 96.4k\Omega$$

$$A_v^{CE} = -\frac{9.80mS(13k\Omega)}{1 + 9.80mS(13k\Omega)} \left(\frac{96.4k\Omega}{2k\Omega + 96.4k\Omega} \right) = +0.972$$

$$A_v^{CS} = -\frac{0.491mS(12k\Omega)}{1 + 0.491mS(12k\Omega)} \left(\frac{892k\Omega}{2k\Omega + 892k\Omega} \right) = +0.853$$

$$\text{BJT: } g_m R_L = 9.80mS(11.5k\Omega) = 113 \quad | \quad \text{FET: } g_m R_L = 0.491mS(10.7k\Omega) = 5.25$$

Page 468

$$\text{BJT: } v_i \leq 0.005V(1 + g_m R_I) \frac{R_I + R_6}{R_6} = 0.005V[1 + 9.8mS(2k\Omega)] \left[\frac{2k\Omega + 13k\Omega}{13k\Omega} \right] = 119 \text{ mV}$$

$$\text{Neglecting } R_6, \quad v_i \leq 0.005V(1 + g_m R_I) = 0.005V[1 + 9.8mS(2k\Omega)] = 103 \text{ mV}$$

$$\text{FET: } v_i \leq 0.2(V_{GS} - V_{TN})(1 + g_m R_I) \frac{R_I + R_6}{R_6} = 0.2(0.982)[1 + 0.491mS(2k\Omega)] \frac{2k\Omega + 12k\Omega}{12k\Omega} = 454 \text{ mV}$$

$$\text{Neglecting } R_6, \quad v_i \leq 0.2(V_{GS} - V_{TN})(1 + g_m R_I) = 0.2(0.982)[1 + 0.491mS(2k\Omega)] = 389 \text{ mV}$$

Page 469

$$R_{iC} = r_o \left[1 + \frac{\beta_o R_{th}}{R_{th} + r_\pi} \right] = 219k\Omega \left[1 + \frac{100(1.73k\Omega)}{1.73k\Omega + 10.2k\Omega} \right] = 3.40 M\Omega$$

Or more approximately, $R_{iC} = r_o [1 + g_m R_{th}] = 219k\Omega [1 + 9.8mS(1.73k\Omega)] = 3.93 M\Omega$

$$R_{iD} = r_o [1 + g_m R_{th}] = 223k\Omega [1 + 0.491(1.71k\Omega)] = 410 k\Omega$$

Page 473

$$A_v^{CB} = g_m R_L \frac{\frac{R_6 \left(\frac{1}{g_m} \right)}{R_6 + \frac{1}{g_m}}}{R_I + \frac{R_6 \left(\frac{1}{g_m} \right)}{R_6 + \frac{1}{g_m}}} = g_m R_L \frac{\frac{R_6}{R_6 + \frac{1}{g_m}}}{g_m R_I + \frac{R_6}{R_6 + \frac{1}{g_m}}} = g_m R_L \frac{R_6}{R_6 (1 + g_m R_I) + R_I}$$

$$A_v^{CB} = g_m R_L \frac{R_6}{R_6 + R_I} \frac{1}{1 + \frac{g_m R_I R_6}{R_6 + R_I}} = \frac{g_m R_L}{1 + g_m R_{th}} \left(\frac{R_6}{R_6 + R_I} \right)$$

The voltage gains are proportional to the load resistance

$$A_v^{CE} = +8.48 \left(\frac{22k\Omega}{18k\Omega} \right) = +10.4 \quad | \quad A_v^{CG} = +4.12 \left(\frac{22k\Omega}{18k\Omega} \right) = +5.02$$

$$\text{CB: } A_v^{CB} \leq g_m R_L = 176 \quad | \quad A_v^{CB} \cong \frac{R_L}{R_{th} \| R_6} = \frac{R_L}{R_I \| R_6} = \frac{18k\Omega}{1.73k\Omega} = 10.4 \quad | \quad 8.48 < 10.4 << 176$$

$$\text{CG: } A_v^{CG} \leq g_m R_L = 8.84 \quad | \quad A_v^{CG} \cong \frac{R_L}{R_{th}} = \frac{R_L}{R_I \| R_6} = \frac{18k\Omega}{1.71k\Omega} = 10.5 \quad | \quad 4.11 < 8.84 < 10.5$$

$$R_{iE} \cong \frac{1}{g_m} = \frac{1}{40I_C} \quad | \quad R_{iS} = \frac{1}{g_m} = \frac{V_{GS} - V_{TN}}{2I_D} \quad | \quad \frac{R_{iE}}{R_{iS}} = \frac{1}{40I_C} \left(\frac{2I_D}{V_{GS} - V_{TN}} \right) = \frac{2}{40(1)} = \frac{1}{20}$$

Page 481

$$A_v^{CS} = \frac{1}{1 + \eta} \sqrt{\frac{(W/L)_1}{(W/L)_2}} \quad | \quad 10^{\frac{26}{20}} = \frac{1}{1 + 0.2} \sqrt{\frac{(W/L)_1}{4}} = \frac{2290}{1}$$

Page 482

$\eta = 0 \quad | \quad I_{D2} = I_{D1} \quad | \quad$ Both transistors are in the active region since $V_{DS} = V_{GS}$.

$$\text{Neglecting } \lambda: \frac{10^{-4}}{2} \left(\frac{2}{1} \right) (5 - V_o - 1)^2 = \frac{10^{-4}}{2} \left(\frac{8}{1} \right) (V_o - 1)^2 \rightarrow V_o = 2.00 \text{ V}$$

$$\text{Keeping } \lambda: \frac{10^{-4}}{2} \left(\frac{2}{1} \right) (5 - V_o - 1)^2 [1 + 0.02(5 - V_o)] = \frac{10^{-4}}{2} \left(\frac{8}{1} \right) (V_o - 1)^2 (1 + 0.02V_o) \rightarrow$$

$$V_o = 2.0064 \text{ V}, \quad I_D = 421.39 \mu\text{A} \rightarrow \text{Q-point: } (2.01 \text{ V}, 421 \mu\text{A})$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TN}} \quad | \quad g_{m1} = \frac{2(421\mu\text{A})}{2 - 1} = 8.42 \times 10^{-4} \text{ A/V} \quad | \quad g_{m2} = \frac{2(421\mu\text{A})}{3 - 1} = 4.21 \times 10^{-4} \text{ A/V}$$

$$r_o = \frac{1/\lambda + V_{DS}}{I_D} \quad | \quad r_{01} = \frac{50V + 2V}{421\mu\text{A}} = 123.5 \text{ k}\Omega \quad | \quad r_{02} = \frac{50V + 3V}{421\mu\text{A}} = 125.9 \text{ k}\Omega$$

$$A_v = -g_{m1} \left(\frac{1}{g_{m2}} || r_{01} || r_{02} || R_F \right) = -8.42 \times 10^{-4} / V(2.375\text{k}\Omega || 123.5\text{k}\Omega || 125.9\text{k}\Omega || 1\text{M}\Omega) = -1.92$$

$$\text{Note Eq. 8.100: For } \eta = 0, A_v \cong \frac{g_{m1}}{g_{m2}} = \frac{8.42}{4.21} = 2.00 \quad \text{or} \quad A_v \cong \sqrt{\frac{W/L_1}{W/L_2}} = \sqrt{\frac{8/1}{2/1}} = 2.00$$

Page 483

$I_{D2} = I_{D1} \quad | \quad$ Both transistors are in the active region since $V_{DS} = V_{GS}$.

$$K_n = 10^{-4} \left(\frac{20}{1} \right) = 2 \times 10^{-3} \frac{A}{V^2} \quad | \quad K_p = 4 \times 10^{-5} \left(\frac{50}{1} \right) = 2 \times 10^{-3} \frac{A}{V^2} \quad | \quad \text{The transistors are symmetrical.}$$

$$\therefore V_o = \frac{V_{DD}}{2} = \frac{3.3V}{2} = 1.65 \text{ V} \quad | \quad I_D = \frac{10^{-4}}{2} \left(\frac{20}{1} \right) (1.65 - 0.7)^2 [1 + 0.02(1.65)] = 932 \mu\text{A}$$

$$\text{Q-point: } (1.65 \text{ V}, 932 \mu\text{A})$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TN}} \quad | \quad g_{m1} = \frac{2(932\mu\text{A})}{1.65 - 0.7} = 1.97 \times 10^{-3} \text{ A/V} \quad | \quad g_{m2} = \frac{2(932\mu\text{A})}{3.3 - 1.65 - 1} = 1.97 \times 10^{-3} \text{ A/V}$$

$$r_o = \frac{1/\lambda + V_{DS}}{I_D} \quad | \quad r_{01} = r_{02} = \frac{50V + 1.65V}{932\mu\text{A}} = 55.4 \text{ k}\Omega \quad | \quad A_v = -(g_{m2} + g_{m1})(r_{01} || r_{02} || R_F)$$

$$A_v = -3.94 \times 10^{-3} / V(55.4\text{k}\Omega || 55.4\text{k}\Omega || 560\text{k}\Omega) = -3.94(26.4) = -104$$

(Compare this to the gain of the circuit in Fig. 8.30 on page 480!!)

Page 485

Since we need high gain, the emitter should be bypassed, and $R_{in}^{CE} = R_B || r_\pi = 250\text{k}\Omega$.

$$\text{If we choose } R_B \cong r_\pi, \quad I_C = \frac{\beta_o}{40r_\pi} \cong \frac{100}{40(500\text{k}\Omega)} = 5 \mu\text{A}$$

$$R_{in}^{CG} \cong \frac{1}{g_m} \quad | \quad I_C \cong \frac{1}{40(2\text{k}\Omega)} = 12.5 \mu\text{A}$$

Page 489

Common – Emitter :

$$C_1 \gg \frac{1}{2\pi(250Hz)(1k\Omega + 77.9k\Omega)} = 8.07nF \quad | \quad \text{Choose } C_1 = 82 \text{ nF} = 0.082 \mu F$$

$$C_2 \gg \frac{1}{2\pi(250Hz)(21.9k\Omega + 82k\Omega)} = 6.13nF \quad | \quad \text{Choose } C_2 = 68 \text{ nF} = 0.068 \mu F$$

$$C_3 \gg \frac{1}{2\pi(250Hz)\left[10k\Omega \left(3k\Omega + \frac{1}{9.80mS}\right)\right]} = 0.269\mu F \quad | \quad \text{Choose } C_3 = 2.7 \mu F$$

Common – Source :

$$C_1 \gg \frac{1}{2\pi(250Hz)(1k\Omega + 892k\Omega)} = 713pF \quad | \quad \text{Choose } C_1 = 8200 pF$$

$$C_2 \gg \frac{1}{2\pi(250Hz)(21.5k\Omega + 82k\Omega)} = 6.15nF \quad | \quad \text{Choose } C_2 = 68 \text{ nF} = 0.068 \mu F$$

$$C_3 \gg \frac{1}{2\pi(250Hz)\left[10k\Omega \left(2k\Omega + \frac{1}{0.491mS}\right)\right]} = 0.221\mu F \quad | \quad \text{Choose } C_3 = 2.2 \mu F$$

Page 491

Common – Collector :

$$C_1 \gg \frac{1}{2\pi(250Hz)(1k\Omega + 95.5k\Omega)} = 6.60nF \quad | \quad \text{Choose } C_1 = 68 \text{ nF} = 0.068 \mu F$$

$$C_2 \gg \frac{1}{2\pi(250Hz)(120\Omega + 82k\Omega)} = 7.75nF \quad | \quad \text{Choose } C_2 = 82 \text{ nF} = 0.082 \mu F$$

Common – Drain :

$$C_1 \gg \frac{1}{2\pi(250Hz)(1k\Omega + 892k\Omega)} = 713pF \quad | \quad \text{Choose } C_1 = 8200 pF$$

$$C_2 \gg \frac{1}{2\pi(250Hz)(1.74k\Omega + 82k\Omega)} = 7.60nF \quad | \quad \text{Choose } C_2 = 82 \text{ nF} = 0.082 \mu F$$

Page 495

Common – Base:

$$C_1 \gg \frac{1}{2\pi(250Hz)(1k\Omega + 0.1k\Omega)} = 0.579 \mu F \quad | \quad \text{Choose } C_1 = 6.8 \mu F$$

$$C_2 \gg \frac{1}{2\pi(250Hz)(21.9k\Omega + 82k\Omega)} = 6.13nF \quad | \quad \text{Choose } C_2 = 0.068 \mu F$$

$$C_3 \gg \frac{1}{2\pi(250Hz)\left(160k\Omega \parallel 300k\Omega \parallel [10.2k\Omega + 101(13k\Omega \parallel 1k\Omega)]\right)} = 12.2nF \quad | \quad \text{Choose } C_3 = 0.12 \mu F$$

Common – Gate:

$$C_1 \gg \frac{1}{2\pi(250Hz)(1k\Omega + 1.74k\Omega)} = 0.232 \mu F \quad | \quad \text{Choose } C_1 = 2.2 \mu F$$

$$C_2 \gg \frac{1}{2\pi(250Hz)(20.9k\Omega + 82k\Omega)} = 6.19nF \quad | \quad \text{Choose } C_2 = 0.068 \mu F$$

$$C_3 \gg \frac{1}{2\pi(250Hz)(1.5M\Omega \parallel 2.2M\Omega)} = 714pF \quad | \quad \text{Choose } C_3 = 8200 pF$$

Page 496

(a) Common – Source :

$$C_3 = \frac{1}{2\pi(1000Hz)\left[10k\Omega \parallel \left(2k\Omega + \frac{1}{0.491mS}\right)\right]} = 55.3nF \quad | \quad \text{Choose } C_3 = 0.056 \mu F$$

(b) Common – Collector :

$$C_2 \gg \frac{1}{2\pi(2000Hz)(120\Omega + 100k\Omega)} = 795pF \quad | \quad \text{Choose } C_2 = 820 pF$$

(c) Common – Gate :

$$C_1 \gg \frac{1}{2\pi(1000Hz)(2k\Omega + 1.74k\Omega)} = 42.6nF \quad | \quad \text{Choose } C_1 = 0.042 \mu F$$

Page 500

$$20V = V_{GS} + 3600I_D \quad | \quad 20 = V_{GS} + 3600 \frac{0.020}{2} (V_{GS} - 1.5)^2 \rightarrow V_{GS} = 2.203 \text{ V} \quad | \quad I_D = 4.94 \text{ mA}$$

$$V_{DS} = 5 - (-V_{GS}) = 7.20 \text{ V} \quad | \quad \text{Q-point: } (4.94 \text{ mA}, 7.20 \text{ V}) \quad | \quad R_{in} = R_G = 22 \text{ M}\Omega$$

$$A_v^{CD} = \frac{g_m R_L}{1 + g_m R_L} \quad | \quad g_m = \frac{2(4.94 \text{ mA})}{(2.20 - 1.50)V} = 14.2 \text{ mS} \quad | \quad R_L = 3600\Omega \parallel 3000\Omega = 1630 \text{ }\Omega \quad | \quad A_v^{CD} = 0.959$$

$$R_{out}^{CD} = 3.6k\Omega \left\| \frac{1}{g_m} \right\| = 3.6k\Omega \left\| \frac{1}{0.0142} \right\| = 69.1 \text{ }\Omega \quad | \quad v_{gs} \leq 0.2(2.20 - 1.50) [1 + 0.0142(1630)] = 3.38 \text{ V}$$

$$r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} = \frac{\frac{1}{0.015} + 5 + 2.21}{0.005} = 14.8 \text{ k}\Omega \quad | \quad R_L = 3600\Omega \parallel 3000\Omega \parallel 14.8k\Omega = 1470 \text{ }\Omega \quad | \quad A_v^{CD} = 0.954$$

$$\frac{W}{L} = \frac{K_n}{K'_n} = \frac{2 \times 10^{-2}}{5 \times 10^{-5}} = \frac{400}{1}$$

Page 501

$$A = \frac{g_m R_S}{1 + g_m R_S} \quad | \quad g_m = \frac{2(4.94 \text{ mA})}{(2.20 - 1.50)V} = 14.2 \text{ mS} \quad | \quad R_S = 3600 \text{ }\Omega \quad | \quad A_v^{CD} = 0.981 \quad | \quad R_{in} = R_G = 22 \text{ M}\Omega$$

$$R_{out}^{CD} = 3.6k\Omega \left\| \frac{1}{g_m} \right\| = 3.6k\Omega \left\| \frac{1}{0.0142} \right\| = 69.1 \text{ }\Omega \quad | \quad A_v^{CD} = A \frac{3000\Omega}{69.1\Omega + 3000\Omega} = 0.959$$

Page 504

Reverse the direction of the arrow on the emitter of the transistor as well as the values of V_{EE} and V_{CC} .

$$R_{in}^{CG} = R_E \left| \frac{1}{g_m} = 13k\Omega \right| \frac{1}{40(331\mu A)} = 75.1 \Omega \quad | \quad A_v^{CB} = \frac{75.1\Omega}{75\Omega + 75.1\Omega} (13.2mS)(7.58k\Omega) = 50.1$$

For $v_{CB} \geq 0$, we require $v_C \geq 0$. $V_C = 5 - I_C R_C = 2.29 \text{ V} \quad \therefore |v_c| \leq 2.29 \text{ V}$

$$v_o \leq 5mV(g_m R_L) = 5mV(13.2mS)(7580\Omega) = 0.500 \text{ V}$$

$$R_E = 75\Omega [1 + 40(7.5 - 0.7)] = 20.5 \text{ k}\Omega \text{ (a standard 1% value)} \quad | \quad I_C \cong \frac{6.8V}{20.5k\Omega} = 332 \mu A$$

$$50 = 40(332\mu A)R_L \frac{75}{75+75} \rightarrow R_L = 7.53k\Omega \rightarrow R_C = 8.14 \text{ k}\Omega \rightarrow 8.06 \text{ k}\Omega \text{ (a standard 1% value)}$$

$$V_{EC} = 0.7 + 7.5 - I_C R_C = 5.52 \text{ V}$$

Page 505

$$f_1 = \frac{1}{2\pi(R_i + R_{in})C_1} = \frac{1}{2\pi(75\Omega + 75.1\Omega)(0.022\mu F)} = 48.2 \text{ kHz}$$

$$f_2 = \frac{1}{2\pi(R_3 + R_{out})C_2} = \frac{1}{2\pi(100k\Omega + 8.2k\Omega)(33pF)} = 44.6 \text{ kHz}$$

We have two almost identical poles and can estimate f_L by applying the bandwidth shrinkage factor

$$\text{from Table 14.13 to the mean of the two frequencies: } f_L \cong 1.55 \left(\frac{48.2 + 44.6}{2} \right) \text{ kHz} = 72 \text{ kHz}$$

$$\text{Using the design value: } f_L \cong 1.55 \left(\frac{50 + 50}{2} \right) \text{ kHz} = 77.5 \text{ kHz}$$

$$5\% \text{ tolerances } I_C^{\max} \cong \frac{V_{EE}^{\max} - 0.7V}{R_E^{\min}} = \frac{5(1.05) - 0.7V}{13k\Omega(0.95)} = 368\mu A$$

$$V_C^{\min} = V_{CC}^{\min} - I_C^{\max} R_C^{\max} = 5V(0.95) - 368\mu A(8.2k\Omega)(1.05) = 1.58 \text{ V} \quad | \quad 1.58 \geq 0, \text{ so active region is ok.}$$

$$10\% \text{ tolerances } I_C^{\max} \cong \frac{V_{EE}^{\max} - 0.7V}{R_E^{\min}} = \frac{5(1.1) - 0.7V}{13k\Omega(0.9)} = 410\mu A$$

$$V_C^{\min} = V_{CC}^{\min} - I_C^{\max} R_C^{\max} = 5V(0.90) - 410\mu A(8.2k\Omega)(1.1) = 0.802 \text{ V} \quad | \quad 0.802 \geq 0, \text{ so active region is ok.}$$

$$v_{th} = v_i \frac{R_{in}^{CB}}{75\Omega + R_{in}^{CB}} g_m R_C = v_i \frac{75}{75\Omega + 75} (13.2mS)(8200\Omega) = 54.1v_i \quad | \quad R_{th} = R_{out}^{CB} = 8.2 \text{ k}\Omega$$

$$A_v^{CG} = \frac{v_o}{v_i} = \frac{v_{th}}{v_i} \frac{100k\Omega}{R_{th} + 100k\Omega} = 54.1 \frac{100k\Omega}{8.2k\Omega + 100k\Omega} = 50.0$$

Page 510

$$f_1 = \frac{1}{2\pi(R_I + R_{in})C_1} = \frac{1}{2\pi(75\Omega + 75\Omega)(0.022\mu F)} = 48.2 \text{ kHz}$$

$$f_2 = \frac{1}{2\pi(R_7 + R_{out})C_2} = \frac{1}{2\pi(100k\Omega + 100k\Omega)(20pF)} = 39.8 \text{ kHz}$$

$$f_3 = \frac{1}{2\pi(R_s \| 1/g_m)C_3} = \frac{1}{2\pi(9.1k\Omega \| 500\Omega)(0.0068\mu F)} = 49.4 \text{ kHz}$$

We have three almost identical poles and can estimate f_L by applying the bandwidth shrinkage factor from Table 14.13 to the mean of the three frequencies: $f_L \approx 1.95 \left(\frac{48.2 + 39.8 + 49.4}{3} \right) \text{ kHz} = 89 \text{ kHz}$

$$r_o \approx r_o = \frac{1}{\lambda I_D} = \frac{1}{0.015(2 \times 10^{-4})} = 333 \text{ k}\Omega$$

$$\text{or more exactly } V_{DS} = 25 - 10^5 I_D - 9.1 \times 10^3 I_D = 25 - 1.09 \times 10^5 (0.2mA) = 3.18 \text{ V}$$

$$r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} = \frac{\frac{1}{0.015}}{2 \times 10^{-4}} + 3.18 = 349 \text{ k}\Omega \quad | \quad R_L = 100k\Omega \| 100k\Omega \| 349k\Omega = 43.7 \text{ k}\Omega$$

$$A_v^{CS} = -(g_m R_L) \frac{R_{in}}{R_I + R_{in}} = -\frac{2(0.2mA)}{0.2V} (43.7k\Omega) \left(\frac{75\Omega}{75\Omega + 75\Omega} \right) = -43.7$$

$$I_D = \frac{0.01}{2} (0.25)^2 = 0.3125 \text{ mA} \quad | \quad V_{GS} - V_{TN} = 0.25 \text{ V} \quad | \quad V_{GS} = 0.25 - 2 = -1.75 \text{ V}$$

$$R_S = \frac{-V_{GS}}{I_D} = \frac{1.75V}{0.3125mA} = 5.60k\Omega \rightarrow 5.6 \text{ k}\Omega \quad | \quad R_L = 2 \frac{A_v}{g_m} = \frac{50(0.25V)}{0.3125mA} = 40 \text{ k}\Omega \quad | \quad R_D \| 100k\Omega = 40 \text{ k}\Omega$$

$R_D = 66.7k\Omega \rightarrow 68 \text{ k}\Omega \quad | \quad C_1 \text{ remains unchanged.}$

$$C_2 >> \frac{1}{10^6 \pi (68k\Omega + 100k\Omega)} = 1.90 \text{ pF} \rightarrow \text{Choose } C_2 = 20 \text{ pF}$$

$$C_3 >> \frac{1}{10^6 \pi (5.6k\Omega \| \frac{1}{2.5mS})} = 0.853nF \rightarrow \text{Choose } C_3 = 8200 \text{ pF}$$

$$v_{th} = v_i \frac{R_{in}^{CG}}{75\Omega + R_{in}^{CG}} g_m R_D = v_i \frac{75\Omega}{75\Omega + 75\Omega} (2mS) (100k\Omega) = 100v_i \quad | \quad R_{th} = R_{out}^{CG} = 100 \text{ k}\Omega$$

$$A_v^{CG} = \frac{v_o}{v_i} = \frac{v_{th}}{v_i} \frac{100k\Omega}{R_{th} + 100k\Omega} = 100 \frac{100k\Omega}{100k\Omega + 100k\Omega} = 50.0$$

Χοντινυεδ ον τηε νεξτ παγε ...

$$(c) \quad v_{th} = v_i \frac{75\Omega}{75\Omega + 75\Omega} (2mS)(100k\Omega || 100k\Omega) = 50.0 \quad | \quad R_{th} = 100k\Omega || 100k\Omega = 50k\Omega$$

$$A_v^{CG} = 50 \frac{100k\Omega}{50k\Omega + 100k\Omega} = 33.3$$

Page 512

$$M_1: \quad I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 \quad | \quad V_{GS} = -R_{S1}I_D \quad | \quad I_D = \frac{0.01}{2} (-200I_D + 2)^2 \rightarrow I_D = 5.00 \text{ mA}$$

$$V_{DS} = 15 - 5mA(820\Omega) = 10.9 \text{ V}$$

$$g_m = \sqrt{2K_n I_D} = \sqrt{2(0.01)(0.005)} = 10.0 \text{ mS} \quad | \quad r_o = \frac{1 + \lambda V_{DS}}{\lambda I_D} = \frac{1 + 0.02(10.9)}{0.02(5mA)} = 12.2 \text{ k}\Omega$$

$$Q_2: \quad V_{EQ} = \frac{22k\Omega}{22k\Omega + 78k\Omega} (15V) = 3.30 \text{ V} \quad | \quad R_{EQ} = 22k\Omega || 78k\Omega = 17.2 \text{ k}\Omega$$

$$I_C = 150 \frac{(3.30 - 0.6)V}{17.2k\Omega + 151(1.6k\Omega)} = 1.57 \text{ mA} \quad | \quad V_{CE} = 15 - 1.57mA \left(4.7k\Omega + \frac{151}{150} 1.6k\Omega \right) = 5.09V$$

$$g_m = (1.57mA)40/V = 62.8 \text{ mS} \quad | \quad r_\pi = \frac{150}{62.8mS} = 2.39 \text{ k}\Omega \quad | \quad r_o = \frac{80+5.09}{1.57mA} = 54.2 \text{ k}\Omega$$

$$Q_3: \quad V_{EQ} = \frac{120k\Omega}{120k\Omega + 91k\Omega} (15V) = 8.53 \text{ V} \quad | \quad R_{EQ} = 120k\Omega || 91k\Omega = 51.8 \text{ k}\Omega$$

$$I_C = 80 \frac{(8.53 - 0.6)V}{51.8k\Omega + 81(3.3k\Omega)} = 1.99 \text{ mA} \quad | \quad V_{CE} = 15 - 1.99mA \left(\frac{81}{80} 3.3k\Omega \right) = 8.35 \text{ V}$$

$$g_m = (1.96mA)40/V = 78.4 \text{ mS} \quad | \quad r_\pi = \frac{80}{78.4mS} = 2.39 \text{ k}\Omega \quad | \quad r_o = \frac{80+8.35}{1.99mA} = 34.4 \text{ k}\Omega$$

A typical op-amp gain is at least 10,000 which exceeds the amplification factor of a single transistor.

Page 515

$$R_{L1} = 478\Omega || 12.2k\Omega = 460 \text{ }\Omega \quad | \quad R_{L2} = 3.53k\Omega || 54.2k\Omega = 3.31 \text{ k}\Omega \quad | \quad R_{L3} = 232\Omega || 34.4k\Omega = 230 \text{ }\Omega$$

$$A_v = -10mS(460\Omega)(-62.8mS)(3.31k\Omega) \left[\frac{79.6mS(230\Omega)}{1 + 79.6mS(230\Omega)} \right] \left[\frac{1M\Omega}{10k\Omega + 1M\Omega} \right] = 898$$

$$20 \log(898) = 59.1 \text{ dB}$$

$$A_v \cong \left(-\frac{V_{DD}}{V_{GS} - V_{TN}} \right) (-10V_{CC})(1) = -\frac{15}{1} (-10)(15)(1) = 2250$$

$$A_v = -10mS(2.39k\Omega)(-62.8mS)(19.8k\Omega)(0.95)(0.99) = 28000$$

Page 519

$$R_{out} = 3300 \left(\frac{1}{0.0796S} + \frac{3990}{90.1} \right) = 55.9 \Omega$$

Note that the answers are obtained directly from SPICE.

Page 520

$$A_{v1} = -g_m R_{L1} = -\sqrt{2(0.01)(0.001)}(3k\Omega || 17.2k\Omega || 2.39k\Omega) = 5.52$$

$$A_v = -5.52(-222)(3.31k\Omega)(0.95)(0.99) = 1150$$

Page 523

$$(a) \quad V_{D1} = 15V - 620\Omega(5mA) = 11.9 V \quad | \quad V_{C2} = 15V - 4.7k\Omega(1.57mA) = 7.62 V$$

$$V_{TH2} = 15V \frac{22k\Omega}{22k\Omega + 78k\Omega} = 3.3V \quad | \quad R_{TH2} = (22k\Omega || 78k\Omega) = 17.1k\Omega$$

$$V_{B2} = 3.3V - \frac{1.57mA}{150}(17.16k\Omega) = 3.12 V$$

$$V_{TH3} = 15V \frac{120k\Omega}{91k\Omega + 120k\Omega} = 8.53V \quad | \quad R_{TH3} = (120k\Omega || 91k\Omega) = 51.75k\Omega$$

$$| \quad V_{B3} = 8.53V - \frac{1.99mA}{80}(51.75k\Omega) = 7.24 V$$

$$(b) \quad 3.1V = 15V - R_D \left(5mA + \frac{1.57mA}{150} \right) \rightarrow R_D = 2.37k\Omega \rightarrow 2.4k\Omega$$

$$7.2V = 15V - R_{C2} \left(1.57mA + \frac{1.99mA}{80} \right) \rightarrow R_{C2} = 4.89k\Omega \rightarrow 5.1 k\Omega \text{ or } 4.7 k\Omega$$

Page 525

$$(a) \quad I_{REF} = \frac{K'_n \left(\frac{W}{L} \right)_1}{2} (V_{GS} - V_{TN})^2 \quad | \quad I_{D2} = \frac{K'_n \left(\frac{W}{L} \right)_2}{2} (V_{GS} - V_{TN})^2$$

$$\frac{I_{D2}}{I_{REF}} = \frac{\left(\frac{W}{L} \right)_2}{\left(\frac{W}{L} \right)_1} \quad \text{or} \quad I_{D2} = I_{REF} \frac{\left(\frac{W}{L} \right)_2}{\left(\frac{W}{L} \right)_1}$$

$$(b) \quad I_{REF} = I_{C1} = I_{S1} \exp \left(\frac{V_{BE}}{V_T} \right) \quad | \quad I_O = I_{C2} = I_{S2} \exp \left(\frac{V_{BE}}{V_T} \right)$$

$$\frac{I_O}{I_{REF}} = \frac{I_{S2}}{I_{S1}} \quad \text{or} \quad I_O = I_{REF} \frac{I_{S2}}{I_{S1}} = I_{REF} \frac{A_{E2}}{A_{E1}}$$

CHAPTER 9

Page 547

$$f_L \cong \frac{1}{2\pi} \sqrt{10^2 + 1000^2 - 2(50)^2 - 2(0)^2} = 159 \text{ Hz} \quad | \quad f_L \cong \frac{1}{2\pi} \sqrt{100^2 + 1000^2 - 2(500)^2 - 2(0)^2} = 114 \text{ Hz}$$

Page 548

$$\left| \frac{200s}{(s+1000)} \right| \geq 0.9 \left| \frac{200s(s+100)}{(s+10)(s+1000)} \right| \quad | \quad 1 \geq 0.9 \frac{\sqrt{\omega^2 + 100^2}}{\sqrt{\omega^2 + 10^2}} \rightarrow 0.81 \leq \frac{\omega^2 + 10^2}{\omega^2 + 100^2} \rightarrow \omega \geq 205 \text{ rad/s}$$

Page 549


$$f_H \cong \frac{10^6}{2\pi} = 159 \text{ kHz}$$

Page 550

$$f_H \cong \frac{1}{2\pi} \frac{1}{\sqrt{\left(\frac{1}{10^5}\right)^2 + \left(\frac{1}{5 \times 10^5}\right)^2 - 2\left(\frac{1}{2 \times 10^5}\right)^2 - 2\left(\frac{1}{\infty}\right)^2}} = 21.7 \text{ kHz}$$

As s approaches 0, $A_H(s) = 100$ or $20 \log(100) = 40 \text{ dB}$

Page 553

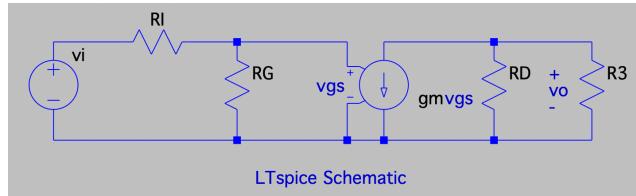

$$v_{gs} = v_i \frac{R_G}{R_I + R_G} \quad | \quad v_o = -g_m v_{gs} (R_D || R_3) \quad | \quad A_{dm} = \frac{v_o}{v_{gs}} = -g_m (R_D || R_3) + \frac{R_G}{R_I + R_G}$$

Page 555

The value of C_3 does not change A_{mid} , ω_{p1} , ω_{p2} , ω_{z1} , or ω_{z2} .

$$\omega_{p3} = -\frac{1}{2\mu F(1.3k\Omega \parallel \frac{1}{1.23mS})} = -1000 \text{ rad/s} \quad | \quad \omega_{z3} = -\frac{1}{2\mu F(1.3k\Omega)} = -385 \text{ rad/s}$$

$$f_L = \frac{1}{2\pi} \sqrt{41.0^2 + 95.9^2 + 1000^2 - 2(0^2 + 0^2 + 385^2)} = 135 \text{ Hz}$$

$$A_{\text{mid}} = 10^{\frac{13.5}{20}} = 4.732 \quad | \quad 4.3k\Omega \parallel 100k\Omega \parallel r_o = \frac{4.732}{1.23mS} \rightarrow r_o = 57.5 \text{ k}\Omega$$

Note that the SPICE value of g_m probably differs from 1.23 mS as well.

$$\omega_{p2} = -\frac{1}{0.1\mu F(4.3k\Omega \parallel 57.5k\Omega + 100k\Omega)} = -96.2 \text{ rad/s}$$

$$f_L = \frac{1}{2\pi} \sqrt{41.0^2 + 96.2^2 + 202^2 - 2(0^2 + 0^2 + 76.9^2)} = 31.8 \text{ Hz}$$

Page 558

$$r_\pi = \frac{140(0.025V)}{175\mu A} = 20.0 \text{ k}\Omega \quad | \quad R_{1S}C_1 = (1k\Omega + 75k\Omega \parallel 20.0k\Omega)2\mu F = 33.6 \text{ ms} \quad | \quad R_{th} = 75k\Omega \parallel 1k\Omega = 987 \text{ }\Omega$$

$$R_{2S}C_2 = (43k\Omega + 100k\Omega)0.1\mu F = 14.3 \text{ ms} \quad | \quad R_{3S}C_3 = \left(13k\Omega \parallel \frac{20.0k\Omega + 987\Omega}{141}\right)10\mu F = 1.47 \text{ ms}$$

$$f_L \cong \frac{1}{2\pi} \left(\frac{1}{33.6ms} + \frac{1}{1.47ms} + \frac{1}{14.3ms} \right) = 124 \text{ Hz}$$

Page 560

$$A_v = -\frac{R_{in}}{R_I + R_m} \left(\frac{\beta_o}{r_\pi} R_L \right) \cong -\left(\frac{1260}{2260} \right) \left(\frac{100}{1.51k\Omega} \right) (4.3k\Omega \parallel 100k\Omega) = -157$$

$$A_v = -\frac{R_{in}}{R_I + R_m} \left(\frac{\beta_o}{r_\pi} R_L \right) \cong -\left(\frac{1260}{2260} \right) \left(\frac{100}{1.51k\Omega} \right) (4.3k\Omega \parallel 100k\Omega \parallel 46.8k\Omega) = -140$$

r_o is responsible for most of the discrepancy. r_π and β_o will also differ from our hand calculations.

Note that 45% of the gain is lost because of the amplifier's low input resistance.

$$g_m = \frac{2(1.5mA)}{0.5V} = 6.00 \text{ mS} \quad | \quad R_{1S}C_1 = (1k\Omega + 243k\Omega)0.1\mu F = 24.4 \text{ ms}$$

$$R_{2S}C_2 = (4.3k\Omega + 100k\Omega)0.1\mu F = 10.4 \text{ ms} \quad | \quad R_{3S}C_3 = \left(1.3k\Omega \parallel \frac{1}{6.00mS}\right)10\mu F = 1.48 \text{ ms}$$

$$f_L \cong \frac{1}{2\pi} \left(\frac{1}{24.4ms} + \frac{1}{1.48ms} + \frac{1}{10.4ms} \right) = 129 \text{ Hz}$$

Page 562

$$g_m = 40(0.1mA) = 4.00 \text{ mS} \quad | \quad R_{1S}C_1 = \left(100\Omega + 43k\Omega \parallel \frac{1}{4.00mS} \right) 4.7\mu F = 1.64 \text{ ms}$$

$$R_{2S}C_2 = (22k\Omega + 75k\Omega)1\mu F = 97.0 \text{ ms} \quad | \quad f_L \cong \frac{1}{2\pi} \left(\frac{1}{1.64ms} + \frac{1}{97.0ms} \right) = 98.7 \text{ Hz}$$

$$A_{mid} = \frac{43k\Omega \parallel 250\Omega}{100\Omega + 43k\Omega \parallel 250\Omega} (4.00mS)(22k\Omega \parallel 75k\Omega) = 48.5$$

$$g_m = \frac{2(1.5mA)}{0.5V} = 6.00 \text{ mS} \quad | \quad R_{1S}C_1 = \left(100\Omega + 1.3k\Omega \parallel \frac{1}{6.00mS} \right) 1\mu F = 0.248 \text{ ms}$$

$$R_{2S}C_2 = (4.3k\Omega + 75k\Omega)0.1\mu F = 7.93 \text{ ms} \quad | \quad f_L \cong \frac{1}{2\pi} \left(\frac{1}{0.248ms} + \frac{1}{7.93ms} \right) = 662 \text{ Hz}$$

Page 563

$$g_m = 40(1mA) = 40.0 \text{ mS} \quad | \quad r_\pi = \frac{100}{.04S} = 2.50 \text{ k}\Omega$$

$$R_{1S}C_1 = \left(1k\Omega + 100k\Omega \parallel [2.5k\Omega + 101(3k\Omega \parallel 47k\Omega)] \right) 0.1\mu F = 7.52 \text{ ms}$$

$$R_{2S}C_2 = \left(47k\Omega + 3k\Omega \parallel \frac{2.5k\Omega + (100k\Omega \parallel 1k\Omega)}{101} \right) 100\mu F = 4.70 \text{ s} \quad | \quad f_L \cong \frac{1}{2\pi} \left(\frac{1}{7.52ms} + \frac{1}{4.7s} \right) = 21.2 \text{ Hz}$$

$$A_{mid} \cong \frac{(\beta_o + 1)R_L}{R_{th} + r_\pi + (\beta_o + 1)R_L} \left(\frac{R_I}{R_I + R_B} \right) = \frac{101(3k\Omega \parallel 47k\Omega)}{990\Omega + 2.5k\Omega + 101(3k\Omega \parallel 47k\Omega)} \left(\frac{100k\Omega}{1k\Omega + 100k\Omega} \right) = +0.978$$

Page 564

$$R_{1S}C_1 = (1k\Omega + 243k\Omega)0.1\mu F = 24.4 \text{ ms} \quad | \quad R_{2S}C_2 = \left(24k\Omega + 1.3k\Omega \parallel \frac{1}{1mS} \right) 47\mu F = 1.15 \text{ s}$$

$$f_L \cong \frac{1}{2\pi} \left(\frac{1}{24.4ms} + \frac{1}{1.15s} \right) = 6.66 \text{ Hz}$$

$$A_{mid} = + \left(\frac{R_G}{R_I + R_G} \right) \frac{g_m R_L}{1 + g_m R_L} = + \left(\frac{243k\Omega}{244k\Omega} \right) \left[\frac{1mS(1.3k\Omega \parallel 24k\Omega)}{1 + 1mS(1.3k\Omega \parallel 24k\Omega)} \right] = +0.550$$

Page 568

$$C_{\pi} = \frac{g_m}{\omega_T} - C_{\mu} \quad C_{\mu} = \frac{C_{\mu o}}{\sqrt{1 + \frac{V_{CB}}{\varphi_{jc}}}}$$

$$(100 \mu A, 8 V): \quad C_{\mu} = \frac{2 pF}{\sqrt{1 + \frac{7.3V}{0.6V}}} = 0.551 \text{ pF} \quad | \quad C_{\pi} = \frac{40(10^{-4})}{2\pi(500MHz)} - 0.551 \times 10^{-12} = 0.722 \text{ pF}$$

$$(2 mA, 5 V): \quad C_{\mu} = \frac{2 pF}{\sqrt{1 + \frac{4.3V}{0.6V}}} = 0.700 \text{ pF} \quad | \quad C_{\pi} = \frac{40(2 \times 10^{-3})}{2\pi(500MHz)} - 0.700 \times 10^{-12} = 24.8 \text{ pF}$$

$$(50 mA, 8 V): \quad C_{\mu} = \frac{2 pF}{\sqrt{1 + \frac{7.3V}{0.6V}}} = 0.551 \text{ pF} \quad | \quad C_{\pi} = \frac{40(5 \times 10^{-2})}{2\pi(500MHz)} - 0.551 \times 10^{-12} = 636 \text{ pF}$$

Page 571

$$C_{GS} = C_{GD} = \frac{1}{2} C_{ISS} = 0.5 \text{ pF}$$

$$C_{GS} + C_{GD} = \frac{g_m}{\omega_T} \quad | \quad 5C_{GD} + C_{GD} = \frac{\sqrt{2(0.01)(0.01)}}{2\pi(200MHz)} = 11.3 \text{ pF} \quad | \quad C_{GD} = 1.88 \text{ pF} \quad | \quad C_{GS} = 9.38 \text{ pF}$$

$$C_{\mu} = \frac{C_{\mu o}}{\sqrt{1 + \frac{V_{CB}}{\varphi_{jc}}}} = \frac{2 pF}{\sqrt{1 + \frac{7.3V}{0.6V}}} = 0.551 \text{ pF} \quad | \quad C_{\pi} = \frac{g_m}{\omega_T} - C_{\mu} = \frac{40(20\mu A)}{2\pi(500MHz)} - 0.551 \text{ pF} = -0.296 \text{ pF}$$

Page 573

$$\begin{aligned} A_v &= -\frac{R_{in}}{R_I + R_{in}} \left(\frac{\beta_o}{r_x + r_{\pi}} R_L \right) \quad | \quad R_{in} = 7.5k\Omega \parallel (1.51k\Omega + 250\Omega) = 1.43k\Omega \\ &\cong -\left(\frac{1430}{2430} \right) \left(\frac{100}{1.76k\Omega} \right) (4.3k\Omega \parallel 100k\Omega) = -139 \end{aligned}$$

$$A_v = -\frac{R_{in}}{R_I + R_{in}} \left(\frac{\beta_o}{r_{\pi}} R_L \right) \cong -\left(\frac{1260}{2260} \right) \left(\frac{100}{1.51k\Omega} \right) (4.3k\Omega \parallel 100k\Omega) = -157$$

Page 583

The term $C_L \frac{R_L}{r_{\pi o}}$ is added to the value of C_T .

$$C_L \frac{R_L}{r_{\pi o}} = 3 pF \left(\frac{4120}{656} \right) = 18.8 \text{ pF} \quad | \quad f_{P1} = \frac{1}{2\pi(656\Omega)(156+18.8)pF} = 1.39 \text{ MHz}$$

$$f_{P2} = \frac{g_m}{2\pi(C_\pi + C_L)} = \frac{0.064S}{2\pi(19.9+3)pF} = 445 \text{ MHz}$$

$$C_\pi = \frac{0.064}{2\pi(500\text{MHz})} - 10^{-12} = 19.4 \text{ pF}$$

$$C_T = 19.4 + 1 \left[1 + 0.064(4120) + \frac{4120}{656} \right] = 290 \text{ pF} \quad | \quad f_{P1} = \frac{1}{2\pi(656\Omega)290pF} = 837 \text{ kHz}$$

$$f_{P2} = \frac{g_m}{2\pi C_\pi} = \frac{0.064S}{2\pi(19.4pF)} = 525 \text{ MHz} \quad | \quad f_Z = \frac{g_m}{2\pi C_\mu} = \frac{0.064S}{2\pi(1pF)} = 10.2 \text{ GHz}$$

$A_{mid} = -135$ is not affected by the value of f_T .

$$\Delta = s^2 \left[C_\pi (C_\mu + C_L) + C_\mu C_L \right] + s \left[C_\pi g_L + C_\mu (g_m + g_{\pi 0} + g_L) + C_L g_{\pi 0} \right] + g_L g_{\pi 0}$$

$$C_\pi = 19.9 \text{ pF} \quad C_\mu = 0.5 \text{ pF} \quad C_L = 3 \text{ pF} \quad r_{\pi 0} = 656 \Omega \quad R_L = 4.12 \text{ k}\Omega \quad g_m = 64.0 \text{ mS}$$

$$C_L = 0 : \quad 9.95 \times 10^{-24} s^2 + 3.77 \times 10^{-14} s + 3.700 \times 10^{-7} = 0$$

MATLAB: roots([9.950E-24 3.771E-14 3.700E-7]) → $-3.7801 \times 10^9 \text{ rad/s}$, $-9.8373 \times 10^6 \text{ rad/s}$

$$C_L = 3 \text{ pF} : \quad 9.95 \times 10^{-24} s^2 + 3.77 \times 10^{-14} s + 3.700 \times 10^{-7} = 0$$

MATLAB: roots([7.115E-23 4.240E-14 3.700E-7]) → $-5.8707 \times 10^8 \text{ rad/s}$, $-8.8581 \times 10^6 \text{ rad/s}$

$$(a) \quad C_T = 10 + 2 \left[1 + 1.23mS(4.12k\Omega) + \frac{4120}{996} \right] = 30.4 \text{ pF} \quad | \quad f_{P1} = \frac{1}{2\pi(996\Omega)30.4pF} = 5.26 \text{ MHz}$$

$$f_{P2} = \frac{g_m}{2\pi C_{GS}} = \frac{1.23mS}{2\pi(10pF)} = 19.6 \text{ MHz} \quad | \quad f_Z = \frac{g_m}{2\pi C_{GD}} = \frac{1.23mS}{2\pi(2pF)} = 97.9 \text{ MHz}$$

$$f_T = \frac{g_m}{2\pi(C_{GS} + C_D)} = \frac{1.23mS}{2\pi(12pF)} = 16.3 \text{ MHz}$$

$$(b) \quad C_T = 10 + 2 \left[1 + 1.23mS(4.12k\Omega) + \frac{4120}{1296} \right] = 28.5 \text{ pF} \quad | \quad f_{P1} = \frac{1}{2\pi(1296\Omega)28.5pF} = 4.31 \text{ MHz}$$

Page 591

$$1 + g_m R_E = 1 + 0.064(100) = 7.40 \quad | \quad R_{iB} = 250 + 1560 + 101(100) = 11.9 \text{ k}\Omega$$

$$r_{\pi 0} = 11.9 \text{ k}\Omega \parallel (882 + 250) = 1030 \text{ }\Omega \quad | \quad A_i = \frac{10 \text{ k}\Omega \parallel 30 \text{ k}\Omega \parallel 11.9 \text{ k}\Omega}{1 \text{ k}\Omega + 10 \text{ k}\Omega \parallel 30 \text{ k}\Omega \parallel 11.9 \text{ k}\Omega} = 0.821$$

$$A_{mid} = -0.821 \left(\frac{264}{7.4} \right) = -29.3 \quad | \quad f_H = \frac{1}{2\pi(1.03 \text{ k}\Omega) \left[\frac{19.9 \text{ pF}}{7.4} + 0.5 \text{ pF} \left(1 + \frac{264}{7.4} + \frac{4120}{1030} \right) \right]} = 6.70 \text{ MHz}$$

$$GBW = 29.3(6.70 \text{ MHz}) = 196 \text{ MHz}$$

Page 592

$$A_{mid} \cong \frac{g'_m R_L}{1 + g'_m R_E} \quad | \quad g'_m = \frac{\beta_o}{r_x + r_\pi} = \frac{100}{250 + \frac{100}{40(0.1mA)}} = 3.96 \text{ mS} \quad | \quad A_{mid} \cong \frac{3.96 \text{ mS} (17.0 \text{ k}\Omega)}{1 + 3.96 \text{ mS} (100 \Omega)} = +48.2$$

$$f_H \cong \frac{1}{2\pi(17.0 \text{ k}\Omega)(0.5 \text{ pF})} = 18.7 \text{ MHz} \quad | \quad GBW = 903 \text{ MHz}$$

Page 593

$$R_{iS} = R_4 \parallel \frac{1}{g_m} = 1.3 \text{ k}\Omega \parallel \frac{1}{3 \text{ mS}} = 265 \text{ }\Omega$$

$$A_{mid} = 0.726(g_m R_L) = 0.726(3 \text{ mS})(4.12 \text{ k}\Omega) = 8.98 \quad | \quad f_H \cong \frac{1}{2\pi(4.12 \text{ k}\Omega)(4 \text{ pF})} = 9.66 \text{ MHz}$$

$$GBW = 86.7 \text{ MHz} \quad | \quad f_T \cong \frac{3 \text{ mS}}{2\pi(11 \text{ pF})} = 43.4 \text{ MHz}$$

Page 595

$$g_m = 40(1.5mA) = 60.0 \text{ mS} \quad r_\pi = \frac{100}{.06} = 1.67 \text{ k}\Omega \quad C_\pi = \frac{60.0 \text{ mS}}{2\pi(500 \text{ MHz})} - 0.5 \text{ pF} = 18.6 \text{ pF}$$

Using Eq. (17.138): $\omega_{p1} = \frac{1}{\{(990\Omega + 150\Omega)\| [1.67k\Omega + 101(2.82k\Omega)]\} \left[0.5 \text{ pF} + \frac{18.6 \text{ pF}}{1 + 60.0 \text{ mS}(2.82k\Omega)} \right]}$

$$f_{p1} = \frac{\omega_{p1}}{2\pi} = 230 \text{ MHz} \quad | \quad A_{be} = \frac{60.0 \text{ mS}(2.82k\Omega)}{1 + 60.0 \text{ mS}(2.82k\Omega)} = 0.9941$$


$$A_i = \frac{100k\Omega \| [150\Omega + 1.67k\Omega + 101(2.82k\Omega)]}{1k\Omega + 100k\Omega \| [150\Omega + 1.67k\Omega + 101(2.82k\Omega)]} = 0.9867 \quad | \quad A_v = 0.9867(0.9941) = 0.981$$

$$(a) R_L = 1.3k\Omega \| 24k\Omega = 1.23k\Omega \quad | \quad A_{mid} = 0.998 \frac{3mS(1.23k\Omega)}{1 + 3mS(1.23k\Omega)} = 0.785$$


$$f_H \cong \frac{1}{2\pi} \frac{1}{(1k\Omega \| 430k\Omega) \left(1pF + \frac{10pF}{1 + 3.69} \right)} = 50.9 \text{ MHz}$$

$$(b) f_H \cong \frac{1}{2\pi} \frac{1}{(250\Omega + 1k\Omega \| 430k\Omega) \left(1pF + \frac{10pF}{1 + 3.69} \right)} = 40.7 \text{ MHz}$$

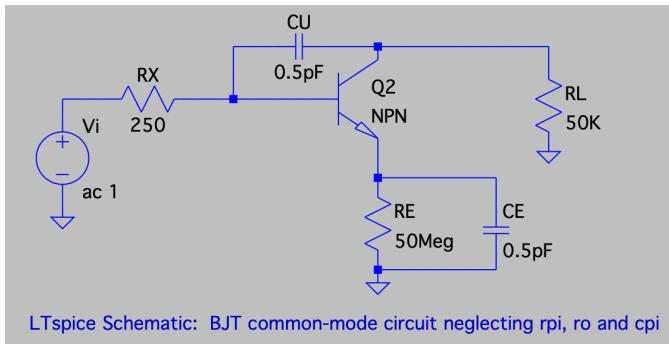Page 599 This exercise should refer to Fig. 9.46(c).





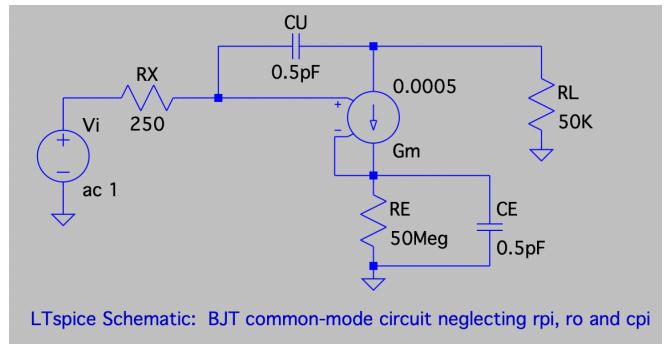LTspice Schematic: BJT common-mode circuit neglecting r_{pi} , r_o and c_{pi}





LTspice Schematic: BJT common-mode circuit neglecting r_{pi} , r_o and c_{pi}

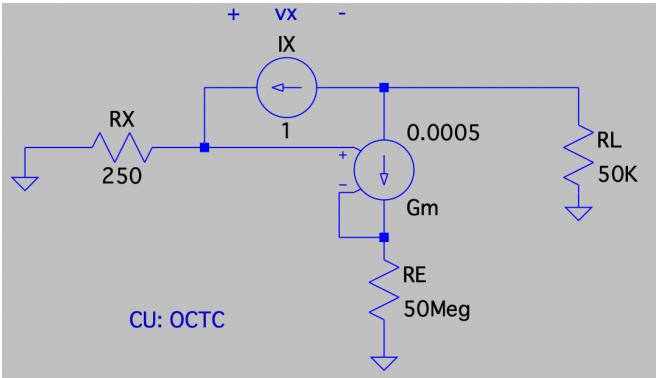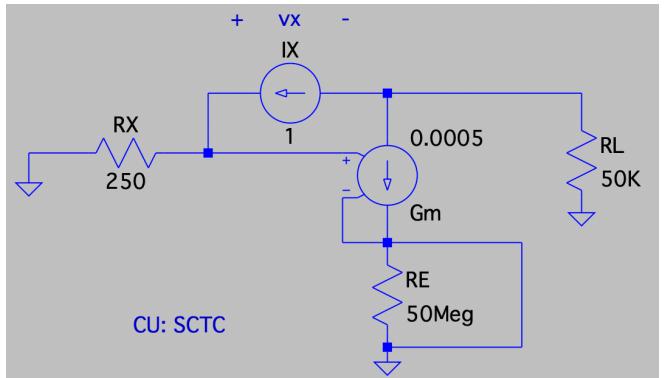In this case, C_π is not specified as it is negligible relative to the $C_{\mu g_m} R_L$ terms. We find f_Z and f_P using the SCTC and OCTC time constant methods. Note: $G_m = g_m$ and $R_E = 2R_{EE}$



$$SCTC: v_x = i_x r_x + (i_x + g_m i_x r_x) R_L \quad | \quad \frac{v_x}{i_x} = r_x + R_L (1 + g_m r_x) \cong r_x + R_L$$

$$OCTC: v_x = i_x r_x + i_x R_L + i_x r_x \left(\frac{g_m}{1 + 2g_m R_{EE}} \right) R_L \quad | \quad \frac{v_x}{i_x} \cong r_x + R_L + R_L \left(\frac{r_x}{2R_{EE}} \right) \cong r_x + R_L$$

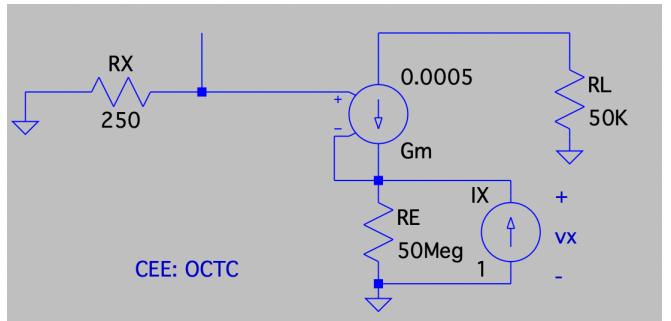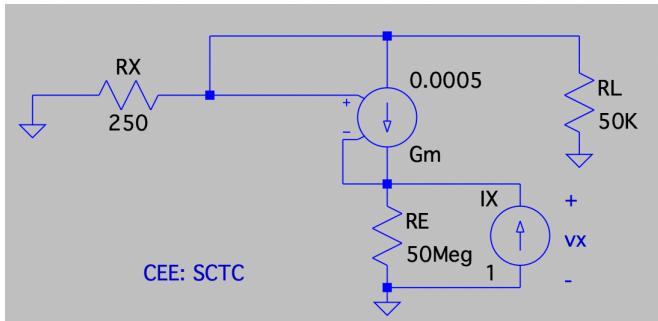

Note that the BJT is now connected as a diode in the left-hand figure, but not the right!

$$SCTC: v_x = i_x \left[2R_{EE} \parallel \left(\frac{1}{g_m} + r_x \parallel R_L \right) \right] \quad | \quad \frac{v_x}{i_x} \cong \frac{1}{g_m} + r_x$$

$$OCTC: v_x = i_x \left[2R_{EE} \parallel \left(\frac{1}{g_m} \right) \right] \quad | \quad \frac{v_x}{i_x} \cong \frac{1}{g_m}$$

Continued on next page

$$SCTC: \omega_Z = \frac{1}{C_\mu(r_x + R_L) + 0.5C_{EE}\left(\frac{1}{g_m} + r_x\right)} \mid f_Z = \frac{1}{2\pi(0.5pF)[500 + 50k + 2k]\Omega} = 6.06 \text{ MHz}$$

$$OCTC: \omega_P \cong \frac{1}{C_\mu(r_x + R_L)} + \frac{1}{C_{EE}/2g_m} \cong \frac{1}{C_{EE}/2g_m} \mid f_P = \frac{1}{2\pi(1000\Omega)0.5pF} = 318 \text{ MHz}$$

It would be good practice to directly derive the four SCTC and OCTC terms!

Page 600

$$\text{Differential Pair: } A_{dm} = -g_m R_C = -40(99.0\mu A)(50k\Omega) = -198$$

$$C_\pi = \frac{40(99.0\mu A)}{2\pi(500 \text{ MHz})} - 0.5pF = 0.761pF \mid r_\pi = \frac{100}{40(99.0\mu A)} = 25.3 k\Omega$$

$$f_H = \frac{1}{2\pi(250\Omega)\left[0.761pF + 0.5pF\left(1 + 198 + \frac{50k\Omega}{250\Omega}\right)\right]} = 3.18 \text{ MHz}$$

$$\text{CC - CB Cascade: } A_v = \frac{\frac{g_{m1}}{g_{m2}}}{1 + \frac{g_{m1}}{g_{m2}}} (g_m R_C) = +\frac{198}{2} = +99.0$$

$$f_H \cong \frac{1}{2\pi(50k\Omega)(0.5pF)} = 6.37 \text{ MHz}$$

Page 601

$$g_m = 40(1.6mA) = 64.0 \text{ mS} \mid r_\pi = \frac{100}{64mS} = 1.56 k\Omega \mid C_\pi = \frac{64.0mS}{2\pi(500 \text{ MHz})} - 0.5pF = 19.9 pF$$

$$A_{mid} = \frac{r_\pi}{R_I + r_x + r_\pi} (-g_m R_L) = \frac{1.56 k\Omega}{882\Omega + 250\Omega + 1.56 k\Omega} (-64.0mS)(4.12k\Omega) = -153$$

$$f_{P1} \cong \frac{1}{2\pi r_{\pi 0}(C_\pi + 2C_\mu)} = \frac{1}{2\pi(656\Omega)(19.9 + 1)pF} = 11.6 \text{ MHz}$$

$$f_{P2} \cong \frac{1}{2\pi R_L(C_\mu + C_L)} = \frac{1}{2\pi(4120\Omega)(0.5 + 5)pF} = 7.02 \text{ MHz}$$

Page 602

$$f_{P1} \cong \frac{1}{4\pi C_{GGD}r_{o2}} = \frac{0.02(100\mu A)}{4\pi(1pF)} = 159 \text{ kHz} \mid f_{P1} \cong \frac{1}{4\pi C_{GGD}r_{o2}} = \frac{0.02(25\mu A)}{4\pi(1pF)} = 39.8 \text{ kHz}$$

Page 610

$$X_c = \frac{1}{2\pi(530\text{Hz})39\text{pF}} = 7.69 \text{ M}\Omega \gg 2.39 \text{ k}\Omega$$

$$X_c = \frac{1}{2\pi(530\text{Hz})1\mu\text{F}} = 300 \text{ M}\Omega \quad | \quad 51.8\text{k}\Omega \parallel 19.8\text{k}\Omega = 14.3 \text{ k}\Omega \quad | \quad 300 \text{ M}\Omega \gg 14.3 \text{ k}\Omega$$

$$X_1 = \frac{1}{2\pi(667\text{kHz})0.01\mu\text{F}} = 23.9 \text{ }\Omega \ll 1.01 \text{ M}\Omega \quad | \quad X_2 = \frac{1}{2\pi(667\text{kHz})47\mu\text{F}} = 5.08 \text{ m}\Omega \ll 66.7 \text{ }\Omega$$

$$X_3 = \frac{1}{2\pi(667\text{kHz})1\mu\text{F}} = 239 \text{ m}\Omega \ll 2.69 \text{ k}\Omega$$

Page 615

$$Z_c = \frac{1}{2\pi j(5\text{MHz})0.01\mu\text{F}} = -j3.18 \text{ }\Omega$$

$$f_o = \frac{1}{2\pi\sqrt{(10\mu\text{H})(100\text{pF} + 20\text{pF})}} = 4.59 \text{ MHz} \quad | \quad r_o = \frac{50V + 15V - 1.6V}{3.2mA} = 19.8 \text{ k}\Omega$$

$$Q = \frac{100\text{k}\Omega \parallel 100\text{k}\Omega \parallel r_o}{2\pi(4.59 \text{ MHz})(10\mu\text{H})} = 49.2 \quad | \quad BW = \frac{4.59 \text{ MHz}}{49.2} = 93.3 \text{ kHz}$$

$$A_{mid} = -g_m(100\text{k}\Omega \parallel 100\text{k}\Omega \parallel r_o) = -\sqrt{2(0.005)(0.0032)}(100\text{k}\Omega \parallel 100\text{k}\Omega \parallel 19.8\text{k}\Omega) = -80.2$$

$$f_o \text{ is unchanged} \quad | \quad r_o = \frac{50V + 10V - 1.6V}{3.2mA} = 18.3 \text{ k}\Omega \quad | \quad Q = \frac{100\text{k}\Omega \parallel 100\text{k}\Omega \parallel r_o}{2\pi(4.59 \text{ MHz})(10\mu\text{H})} = 46.4$$

$$\phi_o = 4.59 \text{ MHz}$$

Page 621

$$L_s \cong \frac{R_{EQ}}{\omega_T} = \frac{L^2 R_{EQ}}{\mu_n(V_{GS} - V_{TN})} = \frac{(5 \times 10^{-5} \text{ cm})^2 75\Omega}{(400 \text{ cm}^2/V - s)(0.25V)} = 1.88 \times 10^{-9} \text{ H}$$

Page 623

$$f_{osc} = 100 \text{ MHz} + 10.7 \text{ MHz} = 110.7 \text{ MHz} \quad f_U = 100 \text{ MHz} + 110.7 \text{ MHz} = 210.7 \text{ MHz}$$

$$(a) \quad f_{osc} = 104.7 \text{ MHz} \pm 10.7 \text{ MHz} \rightarrow 94.0 \text{ MHz} \text{ or } 115.4 \text{ MHz}$$

$$(b) \quad f_{osc} = 88.1 \text{ MHz} \pm 10.7 \text{ MHz} \rightarrow 77.4 \text{ MHz} \text{ or } 98.8 \text{ MHz}$$

Page 624

$$A_{CG} = \frac{1}{A} \frac{A}{\pi} = \frac{1}{\pi} \quad | \quad 20\log\left(\frac{1}{\pi}\right) = -9.94 \text{ dB}$$

Page 627

$$A_{CG} = \frac{1}{A} \frac{2A}{\pi} = \frac{2}{\pi} \quad | \quad 20\log\left(\frac{2}{\pi}\right) = -3.92 \text{ dB}$$

Page 6.28

From Fig. 9.81(a), the amplitude of the output signal is approximately 70 mV, so the conversion gain is approximately:

$$A_{CG} = \frac{1}{100mV} (0.7) \left(\frac{200mV}{\pi} \right) = \frac{1.4}{\pi} \quad | \quad 20\log\left(\frac{1.4}{\pi}\right) = -7.02 \text{ dB}$$

From Fig. 9.81(b), the spectral components at 46 and 54 kHz have amplitudes of approximately 45 mV, so the conversion gain is:

$$A_{CG} = \frac{45mV}{100mV} = 0.45 \quad | \quad 20\log(0.45) = -6.93 \text{ dB} \quad | \quad \text{Note: } \frac{1.4}{\pi} = 0.446$$

Page 630

$$f_C - f_m = 20 - 0.01 = 19.99 \text{ MHz} \quad | \quad f_C + f_m = 20 + 0.01 = 20.01 \text{ MHz}$$

$$3f_C - f_m = 60 - 0.01 = 59.99 \text{ MHz} \quad | \quad 3f_C + f_m = 60 + 0.01 = 60.01 \text{ MHz}$$

$$5f_C - f_m = 100 - 0.01 = 99.99 \text{ MHz} \quad | \quad 5f_C + f_m = 100 + 0.01 = 100.01 \text{ MHz}$$

$$A_{f_C+f_m} = A_{f_C-f_m} = 3 \text{ V}$$

$$A_{3f_C+f_m} = A_{3f_C-f_m} = \frac{A_{f_C-f_m}}{3} = 1 \text{ V}$$

$$A_{5f_C+f_m} = A_{5f_C-f_m} = \frac{A_{f_C-f_m}}{5} = 0.6 \text{ V}$$
