

Microelectronic Circuit Design

Sixth Edition - Part III

Solutions to Exercises

CHAPTER 10

Page 651

$$(a) v_{id} = \frac{10V}{100} = 0.100V = 100mV$$

$$(b) v_{id} = \frac{10V}{5000} = 0.002V = 2.00 mV$$

$$(c) v_{id} = \frac{10V}{10^6} = 1.00 \times 10^{-5}V = 1.00 \mu V$$

Page 653

$$A_v = -\frac{360k\Omega}{68k\Omega} = -5.29 \quad | \quad v_o = -5.29(0.5V) = -2.65 V$$

$$i_i = \frac{0.5V}{68k\Omega} = 7.35 \mu A \quad | \quad i_o = -i_2 = -i_i = -7.35 \mu A$$

Page 655

V_I is a dc value

$$I_1 = \frac{2V}{3.9k\Omega} = 0.513 mA \quad | \quad I_2 = I_1 = 0.513 mA \quad | \quad I_O = -I_2 = -0.513 mA$$

$$A_v = -\frac{22k\Omega}{3.9k\Omega} = -5.64 \quad | \quad V_O = -5.64(2V) = -11.3 V$$

Page 657

$$A_{tr} = -R_2 = \frac{5V}{25\mu A} = 200 k\Omega \quad | \quad A_{tr} = -i_1 R_2 = -2 \times 10^5 A (4 \times 10^{-5} \sin 2000\pi t) = -8 \sin 2000\pi t$$

Page 659

$$A_v = 1 + \frac{36k\Omega}{2k\Omega} = +19.0 \quad | \quad v_o = 19.0(-0.2V) = -3.80 V \quad | \quad i_o = \frac{-3.80V}{36k\Omega + 2k\Omega} = -100 \mu A$$

$$A_v = 1 + \frac{39k\Omega}{1k\Omega} = +40.0 \quad | \quad A_{v dB} = 20 \log(40.0) = 32.0 \text{ dB} \quad | \quad R_{in} = 100k\Omega \parallel \infty = 100k\Omega$$

$$v_o = 40.0(0.25V) = 10.0 V \quad | \quad i_o = \frac{10.0V}{39k\Omega + 1k\Omega} = 0.250 mA$$

$$A_v = 10^{\frac{54}{20}} = 501 \quad 1 + \frac{R_2}{R_1} = 501 \quad \frac{R_2}{R_1} = 500 \quad i_o = \frac{v_o}{R_2 + R_1} \quad \frac{10}{R_2 + R_1} \leq 0.1 mA$$

$$R_1 + R_2 \geq 100k\Omega \quad 501R_1 \geq 100k\Omega \rightarrow R_1 \geq 200 \Omega \quad \text{There are many possibilities.}$$

($R_1 = 200 \Omega$, $R_2 = 100 k\Omega$), but ($R_1 = 220 \Omega$, $R_2 = 110 k\Omega$) is a better solution since resistor tolerances could cause i_o to exceed 0.1 mA in the first case.

Page 662

First exercise: all answers are incorrect! Correct answers appear below.

$$\text{Inverting Amplifier: } A_v = -\frac{30k\Omega}{1.5k\Omega} = -20.0 \quad | \quad R_{in} = R_1 = 1.5 k\Omega$$

$$v_o = -20.0(0.15V) = -3.00 V \quad | \quad i_o = \frac{v_o}{R_2} = \frac{-3.00V}{30k\Omega} = -100 \mu A$$

$$\text{Non-Inverting Amplifier: } A_v = 1 + \frac{30k\Omega}{1.5k\Omega} = +21.0 \quad | \quad R_{in} = \frac{v_i}{i_i} = \frac{0.15V}{0 A} = \infty$$

$$v_o = 21.0(0.15V) = 3.15 V \quad | \quad i_o = \frac{v_o}{R_2 + R_1} = \frac{3.15V}{30k\Omega + 1.5k\Omega} = 100 \mu A$$

Add resistor $R_3 = 2 k\Omega$ in parallel with the opamp input as in the schematic on page 659.

Page 663

$$V_{o1} = 3V \left(\frac{3k\Omega}{1k\Omega} \right) = -9V \quad | \quad V_{o2} = 4V \left(\frac{3k\Omega}{2k\Omega} \right) = -6V \quad | \quad v_o = (-9\sin 1000\pi t - 6\sin 2000\pi t) V$$

The summing junction is a virtual ground: $R_{in1} = \frac{v_1}{i_1} = R_1 = 1 k\Omega \quad | \quad R_{in2} = \frac{v_{12}}{i_2} = R_2 = 2 k\Omega$

$$I_{o1} = \frac{V_{o1}}{R_3} = \left(\frac{-9V}{3k\Omega} \right) = -3 mA \quad | \quad I_{o2} = \frac{V_{o2}}{R_3} = \left(\frac{-6V}{3k\Omega} \right) = -2 mA \quad | \quad v_o = (-3\sin 1000\pi t - 2\sin 2000\pi t) mA$$

Page 666

$$\text{Since } i_+ = 0, I_2 = \frac{3V}{10k\Omega + 100k\Omega} = 27.3 \mu A$$

$$A_v = -\frac{100k\Omega}{10k\Omega} = -10.0 \quad | \quad V_o = -10(3V - 5V) = +20.0 V \quad | \quad I_o = \frac{V_o - V_-}{100k\Omega} = \frac{V_o - V_+}{100k\Omega}$$

$$V_+ = V_2 \frac{R_4}{R_3 + R_4} = 5 \frac{100k\Omega}{10k\Omega + 100k\Omega} = 4.545V$$

$$I_o = \frac{20.0 - 4.545}{100k\Omega} = +155 \mu A \quad | \quad I_2 = \frac{5V}{10k\Omega + 100k\Omega} = 45.5 \mu A$$

$$A_v = -\frac{36k\Omega}{2k\Omega} = -18.0 \quad | \quad V_o = -18(8V - 8.25V) = 4.50 V \quad | \quad I_o = \frac{V_o - V_-}{36k\Omega} = \frac{V_o - V_+}{36k\Omega}$$

$$V_+ = V_2 \frac{R_2}{R_1 + R_2} = 8.25 \frac{36k\Omega}{2k\Omega + 36k\Omega} = 7.816 V \quad | \quad I_o = \frac{4.50 - 7.816}{36k\Omega} = -92.1 \mu A$$

Page 670

$$A_v = -\frac{R_2}{R_1} = -10^{\frac{26}{20}} = -20.0 \quad | \quad R_i = R_m = 10 k\Omega$$

$$R_2 = 20R_1 = 200 k\Omega \quad | \quad C = \frac{1}{2\pi(3kHz)(200k\Omega)} = 265 pF$$

Closest values: $R_1 = 10 k\Omega \quad | \quad R_2 = 200 k\Omega \quad | \quad C = 270 pF$

Page 671


$$A_v = -\frac{R_2}{R_1} = -10^{\frac{20}{20}} = -10.0 \quad | \quad R_i = R_m = 18 k\Omega$$

$$R_2 = 10R_1 = 180 k\Omega \quad | \quad C = \frac{1}{\omega_L R_1} = \frac{1}{2\pi(5kHz)(18k\Omega)} = 1.77 nF = 1770 pF$$

Closest values: $R_1 = 10 k\Omega \quad | \quad R_2 = 180 k\Omega \quad | \quad C = 1800 pF$

Page 672

$$R_{in} = R_1 = 10 \text{ k}\Omega \quad | \quad \Delta V = -\frac{I}{C} \Delta T \quad | \quad C = \frac{(10V/2)}{10k\Omega} \left(\frac{1}{10V} \right) (1ms) = 0.05 \mu F$$

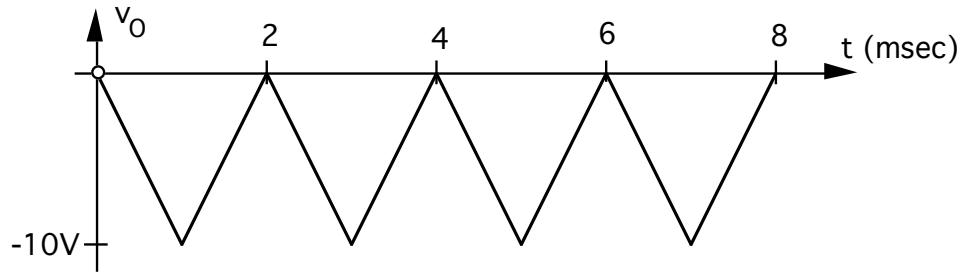

Page 675

$$v_o = -RC \frac{dv_I}{dt} = -(20k\Omega)(0.02\mu F)(2.50V)(2000\pi)(\cos 2000\pi t) = -6.28 \cos 2000\pi t \text{ V}$$

CHAPTER 11

Page 688

$$A_v^{ideal} = \frac{1}{\beta} = 100 \quad | \quad T = A\beta = \frac{10^5}{100} = 1000 \quad | \quad A_v = A_v^{ideal} \frac{T}{1+T} = 100 \frac{1000}{1001} = 99.90$$

$$v_o = A_v v_i = 99.9(0.1V) = 9.99 V \quad | \quad v_{id} = \frac{v_o}{A} = \frac{9.99V}{10^5} = 99.9 \mu V$$

$$A_v^{ideal} = -\frac{R_2}{R_1} \quad | \quad \frac{1}{\beta} = 1 + \frac{R_2}{R_1} \rightarrow \frac{R_2}{R_1} = 99 \quad | \quad A_v^{ideal} = -99 \quad | \quad T = A\beta = \frac{10^5}{100} = 1000$$

$$A_v = A_v^{ideal} \frac{T}{1+T} = -99 \frac{1000}{1001} = -98.90$$

$$v_o = A_v v_i = -98.9(0.1V) = -9.89 V \quad | \quad v_{id} = \frac{v_o}{A} = \frac{-9.89V}{10^5} = -98.9 \mu V$$

Values taken from OP - 27 specification sheet

(www.jaegerblalock.com or www.analog.com)

Values taken from OP - 27 specification sheet

(www.jaegerblalock.com or www.analog.com)

Note that as Specification Sheets are updated over time, the various values may change.

Page 689

$$A_v^{ideal} = \frac{1}{\beta} = 1 + \frac{R_2}{R_1} = 1 + \frac{39k\Omega}{1k\Omega} = +40.0 \quad | \quad T = A\beta = \frac{10^4}{40} = 250 \quad | \quad A_v = A_v^{ideal} \frac{T}{1+T} = 40 \frac{250}{251} = 39.8$$

$$FGE = \frac{1}{1+T} = 0.00398 \text{ or } 0.398 \% \quad | \quad FGE \cong \frac{1}{T} = 0.40 \%$$

$$A_v^{ideal} = -\frac{R_2}{R_1} = -\frac{39k\Omega}{1k\Omega} = -39.0 \quad | \quad \beta = \frac{1}{1 + \frac{R_2}{R_1}} = \frac{1}{40} \quad | \quad T = A\beta = \frac{10^4}{40} = 250 \quad |$$

$$A_v = A_v^{ideal} \frac{T}{1+T} = -39 \frac{250}{251} = -38.8 \quad | \quad FGE = \frac{1}{1+T} = 0.00398 \text{ or } 0.398 \% \quad | \quad FGE \cong \frac{1}{T} = 0.40 \%$$

Page 691

Values taken from OP - 77 specification sheet (www.jaegerblalock.com or www.analog.com)
 Note that as Specification Sheets are updated over time, the various values may change.

Page 692

$$1 + T = \frac{R_o}{R_{out}} \rightarrow T = \frac{50\Omega}{0.1\Omega} - 1 = 499 \quad | \quad A = T \left(\frac{1}{\beta} \right) = 499(40) = 2.00 \times 10^4$$

$$A_v = A_v^{ideal} \frac{T}{1+T} \quad | \quad A_v^{ideal} = 1 + \frac{R_2}{R_l} = 1 + \frac{39k\Omega}{1k\Omega} = +40.0$$

$$T = A\beta = 10^4 \frac{1k\Omega}{0.05k\Omega + 39k\Omega + 1k\Omega} = 249.7 \quad | \quad A_v = A_v^{ideal} \frac{T}{1+T} = 40 \frac{249.7}{250.7} = 39.8$$

$$A_v^{\max} = 1 + \frac{39k\Omega(1.05)}{1k\Omega(0.95)} = 44.1 \quad | \quad GE = 44.2 - 40.0 = 4.20 \quad | \quad FGE = \frac{4.20}{40} = 10.5 \%$$

$$A_v^{\min} = 1 + \frac{39k\Omega(0.95)}{1k\Omega(1.05)} = 36.3 \quad | \quad GE = 36.3 - 40.0 = -3.70 \quad FGE = \frac{-3.70}{40} = -9.3 \%$$

Page 693

$$1 + T = \frac{R_o}{R_{out}} \rightarrow T = \frac{200\Omega}{0.1\Omega} - 1 = 1999 \quad | \quad A = T \left(\frac{1}{\beta} \right) = 1999(100) = 2.00 \times 10^5 \text{ or } 106 \text{ dB}$$

Page 695

Values taken from op - amp specification sheets (www.jaegerblalock.com or www.analog.com)
 Note that as Specification Sheets are updated over time, the various values may change.

Page 696

$$R_{in} = R_{id}(1+T) \mid T = A\beta = 10^4 \left(\frac{10k\Omega \| 1M\Omega}{10k\Omega \| 1M\Omega + 390k\Omega} \right) = \frac{10^4}{40.39} = 248$$

$$R_{in} = 1M\Omega [1+248] = 249 M\Omega$$

$$i_- = -\frac{v_i}{R_{in}} = -\frac{1V}{249M\Omega} = -4.02 nA \mid i_1 = \frac{\beta v_o}{R_1} \mid v_o = A_v^{ideal} \frac{T}{1+T} v_i = 40 \frac{248}{249} v_i = 39.8 v_i$$

$$i_1 = \frac{\beta v_o}{R_1} = \frac{39.8}{40.4} \left(\frac{1V}{10k\Omega} \right) = 98.5 \mu A \mid \text{Yes, } |i_1| >> |i_-|$$

$$\text{If we assume } 1M\Omega \gg 10k\Omega, T = A\beta = 10^4 \left(\frac{10k\Omega}{10k\Omega + 390k\Omega} \right) = \frac{10^4}{40} = 250$$

$$R_{in} = 1M\Omega [1+250] = 251 M\Omega$$

$$i_- = -\frac{v_i}{R_{in}} = -\frac{1V}{251M\Omega} = -3.98 nA \mid i_1 = \frac{\beta v_o}{R_1} \mid v_o = A_v^{ideal} \frac{T}{1+T} v_i = 40 \frac{250}{251} v_i = 39.8 v_i$$

$$i_1 = \frac{\beta v_o}{R_1} = \frac{39.8}{40} \left(\frac{1V}{10k\Omega} \right) = 99.5 \mu A \mid \text{Yes, } |i_1| >> |i_-|$$

Page 697

$$R_{in} \cong R_1 + R_{id} \left\| \frac{R_2}{1+A} = 1k\Omega + 1M\Omega \right\| \frac{100k\Omega}{1+10^5} = 1001 \Omega \mid R_{in}^{ideal} = R_1 = 1000 \Omega \mid 1 \Omega \text{ or } 0.1 \%$$

Page 705

$$A_v^{ideal} = 1 + \frac{R_2}{R_1} = 1 + \frac{91k\Omega}{10k\Omega} = 10.1$$

$$R_{in}^D = R_{id} + R_i \| (R_2 + R_o) = 25k\Omega + 10k\Omega \| (91k\Omega + 1k\Omega) = 34.0 \text{ k}\Omega$$

$$R_{out}^D = R_o \| [R_2 + R_i \| R_{id}] = 1k\Omega \| [91k\Omega + 10k\Omega \| 25k\Omega] = 990 \text{ }\Omega$$

$$T = A_o \frac{R_i \| R_{id}}{R_o + R_2 + R_i \| R_{id}} = 10^4 \frac{10k\Omega \| 25k\Omega}{1k\Omega + 91k\Omega + 10k\Omega \| 25k\Omega} = 720$$

$$A_v = A_v^{ideal} \frac{T}{1+T} = 10.1 \frac{720}{1+720} = 10.1$$

$$R_{in} = R_{in}^D (1+T) = 34.0k\Omega (1+720) = 24.5 M\Omega$$

$$R_{out} = \frac{R_{out}^D}{1+T} = \frac{990\Omega}{1+720} = 1.37 \text{ }\Omega$$

$$A_v^{ideal} = 1 + \frac{R_2}{R_1} = 1 + \frac{91k\Omega}{10k\Omega} = 10.1$$

$$R_{in}^D = R_I + R_{id} + R_i \| (R_2 + R_o \| R_L) = 2k\Omega + 25k\Omega + 10k\Omega \| (91k\Omega + 1k\Omega \| 5k\Omega) = 36.0 \text{ k}\Omega$$

$$R_{out}^D = R_L \| [R_o \| (R_2 + R_i \| (R_{id} + R_I))] = 5k\Omega \| 1k\Omega \| [91k\Omega + 10k\Omega \| (25k\Omega + 2k\Omega)] = 826 \text{ }\Omega$$

$$v_{th} = \left(A_o \frac{R_L}{R_o + R_L} v_{id} \right) \frac{R_i}{R_L \| R_o + R_2 + R_i} = 10^4 \frac{5k\Omega}{1k\Omega + 5k\Omega} v_{id} \frac{10k\Omega}{1k\Omega \| 5k\Omega + 91k\Omega + 10k\Omega} = 818v_{id}$$

$$R_{th} = R_i \| (R_2 + R_L \| R_o) = 10k\Omega \| (91k\Omega + 1k\Omega \| 5k\Omega) = 9.02 \text{ k}\Omega$$

$$T = \left(\frac{v_{th}}{v_{id}} \right) \frac{R_{id}}{R_{th} + R_{id} + R_I} = 818 \frac{25k\Omega}{9.02k\Omega + 25k\Omega + 2k\Omega} = 568$$

$$A_v = A_v^{ideal} \frac{T}{1+T} = 10.1 \frac{568}{1+568} = 10.1$$

$$R_{in} = R_{in}^D (1+T) = 36.0k\Omega (1+568) = 20.5 M\Omega$$

$$R_{out} = \frac{R_{out}^D}{1+T} = \frac{826\Omega}{1+568} = 1.45 \text{ }\Omega$$

Continued on next page.

Page 705 cont.

$$A_v^{ideal} = 1 + \frac{R_2}{R_1} = 1 + \frac{91k\Omega}{10k\Omega} = 10.1$$

$$R_{in}^D = R_{id} = 25k\Omega \quad | \quad R_{out}^D = R_o = 1 k\Omega$$

$$T = A_o \frac{R_1}{R_1 + R_2} = 10^4 \frac{10k\Omega}{10k\Omega + 91k\Omega} = 990$$

$$A_v = A_v^{ideal} \frac{T}{1+T} = 10.1 \frac{990}{1+990} = 10.1$$

$$R_{in} = R_{in}^D (1 + T) = 25.0k\Omega (1 + 990) = 24.8 M\Omega$$

$$R_{out} = \frac{R_{out}^D}{1+T} = \frac{1k\Omega}{1+990} = 1.01 \Omega$$

$$A_v^{ideal} = 1 + \frac{R_2}{R_1} = 1 + \frac{91k\Omega}{10k\Omega} = 10.1$$

$$R_{in}^D = R_I + R_{id} + R_l \parallel (R_2 + R_o) = 5k\Omega + 25k\Omega + 10k\Omega \parallel (91k\Omega + 1k\Omega) = 39.0 k\Omega$$

$$R_{out}^D = R_o \parallel [R_2 + R_l] \parallel (R_{id} + R_I) = 1k\Omega \parallel [91k\Omega + 10k\Omega] \parallel (25k\Omega + 5k\Omega) = 990 \Omega$$

$$v_{th} = A_o v_{id} \frac{R_1}{R_o + R_2 + R_l} = 10^4 v_{id} \frac{10k\Omega}{1k\Omega + 91k\Omega + 10k\Omega} = 980 v_{id}$$

$$R_{th} = R_l \parallel (R_2 + R_o) = 10k\Omega \parallel (91k\Omega + 1k\Omega) = 9.02 k\Omega$$


$$T = \frac{v_{th}}{v_{id}} \frac{R_{id}}{R_{th} + R_{id} + R_I} = 980 \frac{25k\Omega}{9.02k\Omega + 25k\Omega + 5k\Omega} = 628$$

$$A_v = A_v^{ideal} \frac{T}{1+T} = 10.1 \frac{628}{1+628} = 10.1$$

$$R_{in} = R_{in}^D (1 + T) = 39.0k\Omega (1 + 628) = 24.5 M\Omega$$

$$R_{out} = \frac{R_{out}^D}{1+T} = \frac{990\Omega}{1+628} = 1.57 \Omega$$

Page 709

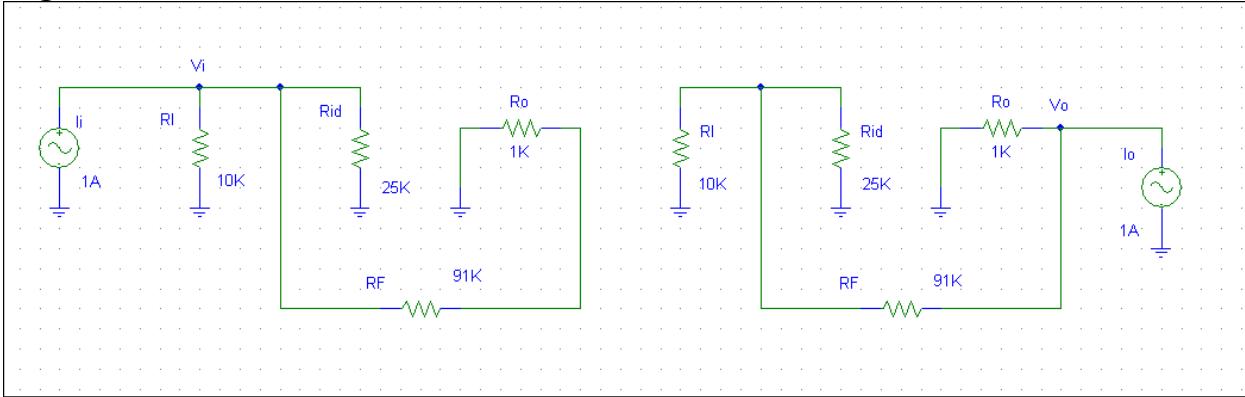

$$R_{in}^D = \frac{V_i}{I_i} = R_I \| R_{id} \| (R_F + R_o) \quad | \quad R_{out}^D = \frac{V_o}{I_o} = R_o \| (R_F + R_{id}) \| R_I$$

Page 711

$$A_{tr}^{ideal} = -R_F = -91k\Omega$$

$$R_{in}^D = R_I \| (R_F + R_o) = 10k\Omega \| (91k\Omega + 1k\Omega) = 9.02 k\Omega$$

$$R_{out}^D = R_o \| (R_F + R_I) = 1k\Omega \| (91k\Omega + 10k\Omega) = 990 \Omega$$

$$T = A_o \frac{R_I}{R_o + R_F + R_I} = 10^4 \frac{10k\Omega}{1k\Omega + 91k\Omega + 10k\Omega} = 980$$

$$A_{tr} = A_{tr}^{ideal} \frac{T}{1+T} = -91k\Omega \frac{980}{1+980} = -90.9 k\Omega$$

$$R_{in} = \frac{R_{in}^D}{1+T} = \frac{9.02k\Omega}{1+980} = 9.19 \Omega \quad R_{out} = \frac{R_{out}^D}{1+T} = \frac{990\Omega}{1+980} = 1.01 \Omega$$

$$A_{tr}^{ideal} = -R_F = -91k\Omega$$

$$R_{in}^D = R_{id} \| (R_F + R_o) = 25k\Omega \| (91k\Omega + 1k\Omega) = 19.7 k\Omega$$

$$R_{out}^D = R_o \| (R_F + R_{id}) = 1k\Omega \| (91k\Omega + 25k\Omega) = 991 \Omega$$

$$T = A_o \frac{R_{id}}{R_o + R_F + R_{id}} = 10^4 \frac{25k\Omega}{1k\Omega + 91k\Omega + 25k\Omega} = 2137$$

$$A_{tr} = A_{tr}^{ideal} \frac{T}{1+T} = -91k\Omega \frac{2137}{1+2137} = -91.0 k\Omega$$

$$R_{in} = \frac{R_{in}^D}{1+T} = \frac{19.7k\Omega}{1+2137} = 9.21 \Omega \quad R_{out} = \frac{R_{out}^D}{1+T} = \frac{991\Omega}{1+2137} = 0.464 \Omega$$

Page 716

$$A_{ic}^{ideal} = -\frac{1}{R} = -\frac{1}{10k\Omega} = -10^{-4} S$$

$$R_{in}^D = R_{id} + R \parallel R_o = 25k\Omega + 10k\Omega \parallel 1k\Omega = 25.9 k\Omega$$

$$R_{out}^D = R_o + R \parallel R_{id} = 1k\Omega + 10k\Omega \parallel 25k\Omega = 8.14 k\Omega$$

$$T = -\left(\frac{v_{th}}{v_{id}}\right) \frac{R_{id}}{R_{th} + R_{id}} = 9090 \frac{25k\Omega}{0.909k\Omega + 25k\Omega} = 8770$$


$$A_{ic} = -\frac{1}{R} \left(\frac{T}{1+T} \right) = -\frac{1}{10k\Omega} \left(\frac{8770}{1+8770} \right) = -0.100 mS$$

$$R_{in} = R_{in}^D (1+T) = 25.9k\Omega (1+8770) = 227 M\Omega$$

$$R_{out} = R_{out}^D (1+T) = 8.14k\Omega (1+8770) = 71.4 M\Omega$$

Page 718

LTS defense Drawing

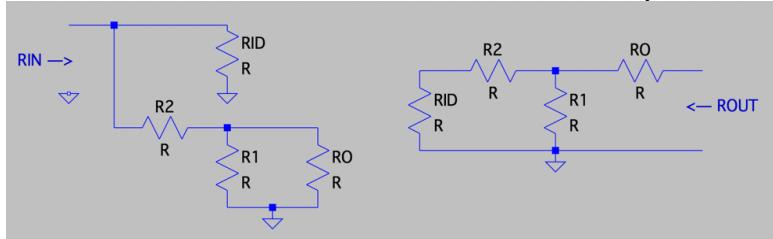

$$R_{in} = R_{id} \parallel (R_2 + R_1) \parallel R_o \quad | \quad R_{in} = R_o + R_1 \parallel (R_2 + R_{id})$$

Page 720

$$A_i^{ideal} = 1 + \frac{R_2}{R_1} = 1 + \frac{27k\Omega}{3k\Omega} = +10$$

$$R_{in}^D = R_{id} \parallel (R_2 + R_1) \parallel R_o = 25k\Omega \parallel (27k\Omega + 3k\Omega \parallel 1k\Omega) = 13.2 k\Omega$$

$$R_{out}^D = R_o + R_1 \parallel (R_2 + R_{id}) = 1k\Omega + 3k\Omega \parallel (27k\Omega + 25k\Omega) = 3.84 k\Omega$$

$$T = A_o \frac{\left[R_1 \parallel (R_2 + R_{id}) \right]}{R_1 \parallel (R_2 + R_{id}) + R_o} \left(\frac{R_{id}}{R_2 + R_{id}} \right)$$

$$T = 10^4 \frac{3k\Omega \parallel (27k\Omega + 25k\Omega)}{1k\Omega + 3k\Omega \parallel (27k\Omega + 25k\Omega)} \left(\frac{25k\Omega}{27k\Omega + 25k\Omega} \right) = 3555$$

$$A_i = +10 \left(\frac{T}{1+T} \right) = +10 \left(\frac{3555}{1+3555} \right) = +10.0$$

$$R_{in} = \frac{R_{in}^D}{(1+T)} = \frac{13.2k\Omega}{1+3555} = 3.71 \Omega$$

$$R_{out} = R_{out}^D (1+T) = 3.84k\Omega (1+3555) = 13.7 M\Omega$$

Page 721

$$R'_{id} = R_I \parallel R_{id} = 10k\Omega \parallel 25k\Omega = 7.14 \text{ k}\Omega$$

$$A_i^{ideal} = 1 + \frac{R_2}{R_1} = 1 + \frac{270k\Omega}{30k\Omega} = +10$$

$$R_{in}^D = R'_{id} \parallel (R_2 + R_I) \parallel R_o = 7.14k\Omega \parallel (270k\Omega + 30k\Omega \parallel 1k\Omega) = 6.96 \text{ k}\Omega$$

$$R_{out}^D = R_o + R_I \parallel (R_2 + R'_{id}) = 1k\Omega + 30k\Omega \parallel (270k\Omega + 7.14k\Omega) = 28.1 \text{ k}\Omega$$

$$T = A_o \frac{\left[R_I \parallel (R_2 + R'_{id}) \right]}{R_I \parallel (R_2 + R'_{id}) + R_o} \left(\frac{R'_{id}}{R_2 + R'_{id}} \right)$$

$$T = 10^4 \frac{30k\Omega \parallel (270k\Omega + 7.14k\Omega)}{30k\Omega \parallel (270k\Omega + 7.14k\Omega) + 1k\Omega} \left(\frac{7.14 \text{ k}\Omega}{270k\Omega + 7.14k\Omega} \right) = 248.5$$

$$A_i = +10 \left(\frac{T}{1+T} \right) = +10 \left(\frac{248.5}{1+248.5} \right) = +9.96$$

$$R_{in} = \frac{R_{in}^D}{1+T} = \frac{6.96k\Omega}{1+248.5} = 27.9 \text{ }\Omega$$

$$R_{out} = R_{out}^D (1+T) = 28.1k\Omega (1+248.5) = 7.01 M\Omega$$

Page 726

$$V_o = V_{os} \frac{A}{1+A} = 0.001V \left(\frac{1000}{1001} \right) = .999 \text{ mV} \quad | \quad V_o = AV_{os} = 100(0.001V) = 1.00V$$

Page 727

Values taken from op - amp specification sheets (www.jaegerblalock.com or www.analog.com)

$$|V_o| \leq 50(0.002V) \rightarrow -0.100 \text{ V} \leq V_o \leq +0.100 \text{ V}$$

Note that as Specification Sheets are updated over time, the various values may change.

Page 730

Values taken from op - amp specification sheets (via www.jaegerblalock.com or www.analog.com)

$$R = 39k\Omega \parallel 1k\Omega = 975 \text{ }\Omega$$

$R = 1 \text{ k}\Omega$ is the closest 5% value, or one could use $39 \text{ k}\Omega$ and $1 \text{ k}\Omega$ resistors in parallel.

$$v_o(t) = V_{os} + \frac{V_{os}}{RC} t + \frac{I_{B2}}{C} t \quad | \quad 1.5mV + \frac{1.5mV}{10k\Omega(100pF)} t + \frac{100nA}{100pF} t = 15V \rightarrow t = 6.00 \text{ ms}$$

Note that as Specification Sheets are updated over time, the various values may change.

Page 731

Values taken from op - amp specification sheets (via www.jaegerblalock.com or www.analog.com)

Page 733

Values taken from op-amp specification sheets (via www.jaegerblalock.com or www.analog.com)

$$R_{EQ} = R_L \left\| (R_2 + R_1) \geq \frac{20V}{5mA} = 4k\Omega \quad R_1 + R_2 \geq \left(\frac{1}{4k\Omega} - \frac{1}{5k\Omega} \right)^{-1} = 20k\Omega \right.$$

Including 5% tolerances, $R_1 + R_2 \geq 21k\Omega \quad A_v = 10 \rightarrow R_2 = 9R_1$

A few possibilities: 27 k Ω and 3 k Ω , 270 k Ω and 30 k Ω , 180 k Ω and 20 k Ω , etc.

$$I_O^{Max} = \frac{10V}{[0.9(100k\Omega)][0.9(5k\Omega)]} = 2.33 mA$$

Page 735

Values taken from op - amp specification sheets (via www.jaegerblalock.com or www.analog.com)

Page 737

$$v_o = A \left(v_{id} + \frac{v_{ic}}{CMRR} \right)$$

$$v_o^{\min} = A \left(v_{id} + \frac{v_{ic}}{CMRR} \right) = 2500 \left(0.002 - \frac{5.000}{10^4} \right) = 3.750 V$$

$$v_o^{\max} = A \left(v_{id} + \frac{v_{ic}}{CMRR} \right) = 2500 \left(0.002 + \frac{5.000}{10^4} \right) = 6.250 V \quad | \quad 3.750 V \leq v_o \leq 6.250 V$$

Page 739

$$A_v = \frac{A \left(1 + \frac{1}{2CMRR} \right)}{1 + A \left(1 - \frac{1}{2CMRR} \right)} = \frac{10^4 \left(1 + \frac{1}{2 \times 10^4} \right)}{1 + 10^4 \left(1 - \frac{1}{2 \times 10^4} \right)} = 1.000 \quad A_v = \frac{10^3 \left(1 + \frac{1}{2 \times 10^3} \right)}{1 + 10^3 \left(1 - \frac{1}{2 \times 10^3} \right)} = 1.000$$

Page 740

$$GE = FGE(A_v) \leq 5 \times 10^{-5} (1) = 5 \times 10^{-5} \quad \text{Worst case occurs for negative CMRR: } GE \cong \frac{1}{A} + \frac{1}{CMRR}$$

If both terms make equal contributions: $A = CMRR = \frac{1}{2.5 \times 10^{-5}} = 4 \times 10^4$ or 92 dB

For other cases: $CMRR = \left(5 \times 10^{-5} - \frac{1}{A}\right)^{-1}$ or $A = \left(5 \times 10^{-5} - \frac{1}{CMRR}\right)^{-1}$

$$A = 100 \text{ dB} \quad CMRR = \left(5 \times 10^{-5} - \frac{1}{10^5}\right)^{-1} = 2.5 \times 10^4 \text{ or } 88 \text{ dB}$$

$$CMRR = 100 \text{ dB} \quad A = \left(5 \times 10^{-5} - \frac{1}{10^5}\right)^{-1} = 2.5 \times 10^4 \text{ or } 88 \text{ dB}$$

Page 741

Values taken from op-amp specification sheets (via www.jaegerblalock.com or www.analog.com)
Note that as Specification Sheets are updated over time, the various values may change.

Page 745

$$A_o = 10^{\frac{100}{20}} = 10^5 \quad | \quad \omega_B = \frac{\omega_T}{A_o} = \frac{2\pi(5 \times 10^6)}{10^5} = \frac{10^7 \pi}{10^5} = 100\pi \quad | \quad f_B = \frac{100\pi}{2\pi} = 50 \text{ Hz}$$

$$A(s) = \frac{\omega_T}{s + \omega_B} = \frac{10^7 \pi}{s + 100\pi}$$

$$A_v(s) = \frac{\omega_T}{s + \frac{\omega_T}{A_o}} = \frac{2\pi x 10^6}{s + \frac{2\pi x 10^6}{2 \times 10^5}} = \frac{2\pi x 10^6}{s + 10\pi}$$

Page 748

$$A_o = 10^{\frac{90}{20}} = 31600 \quad | \quad f_B = \frac{f_T}{A_o} = \frac{5 \times 10^6}{31600} = 158 \text{ Hz} \quad | \quad f_H \cong \beta f_T = 0.01(5 \text{ MHz}) = 50 \text{ kHz}$$

$$A(s) = \frac{\omega_T}{s + \omega_B} = \frac{2\pi(5 \times 10^6)}{s + 2\pi(158)} = \frac{10^7 \pi}{s + 316\pi} \quad | \quad A_v(s) = \frac{2\pi(5 \times 10^6)}{s + 2\pi(5 \times 10^4)} = \frac{10^7 \pi}{s + 10^5 \pi}$$

$$A\beta = \frac{\omega_T}{s + \omega_B} \beta \quad | \quad \text{For } \omega_H \gg \omega_B: A\beta \cong \frac{\beta \omega_T}{j\omega_H} = \frac{1}{j} = -j1 \quad \text{since } \omega_H = \beta \omega_T$$

Page 750

$$A_o = 10^{\frac{90}{20}} = 31600 \quad | \quad f_B = \frac{f_T}{A_o} = \frac{5 \times 10^6}{31600} = 158 \text{ Hz} \quad | \quad f_H \cong \beta f_T = \frac{5 \text{ MHz}}{1 + 10^{\frac{50}{20}}} = 15.8 \text{ kHz}$$

$$A(s) = \frac{2\pi(5 \times 10^6)}{s + 2\pi(158)} = \frac{10^7 \pi}{s + 316\pi} \quad | \quad A_v(s) = \frac{2\pi(5 \times 10^6)}{s + 2\pi(16.0 \times 10^3)} = \frac{10^7 \pi}{s + 3.20 \times 10^4 \pi}$$

$$f_H \cong \beta f_T = 1(10 \text{ MHz}) = 10 \text{ MHz} \quad | \quad f_H \cong \beta f_T = \frac{1}{2}(10 \text{ MHz}) = 5 \text{ MHz}$$

Page 751

$$A_o = 10^{\frac{100}{20}} = 10^5 \quad | \quad f_B = \frac{f_T}{A_o} = \frac{10 \times 10^6}{10^5} = 100 \text{ Hz} \quad | \quad f_H \cong \beta f_T = \frac{10 \text{ MHz}}{10^{\frac{60}{20}}} = \frac{10 \text{ MHz}}{1000} = 10 \text{ kHz}$$

$$A(s) = \frac{\omega_T}{s + \omega_B} = \frac{2\pi(10^7)}{s + 2\pi(100)} = \frac{2 \times 10^7 \pi}{s + 200\pi} \quad | \quad A_v(s) = \frac{2 \times 10^7 \pi}{s + 2.02 \times 10^4 \pi} \cong \frac{2 \times 10^7 \pi}{s + 2 \times 10^4 \pi}$$

Page 753

$$V_M \leq \frac{SR}{\omega} = \frac{5 \times 10^5 V/s}{2\pi(20 \text{ kHz})} = 3.98 \text{ V} \quad | \quad f_M = \frac{SR}{2\pi V_{FS}} = \frac{5 \times 10^5 V/s}{2\pi(10V)} = 7.96 \text{ kHz}$$

Page 754

Values taken from op-amp specification sheets (via www.jaegerblalock.com or www.analog.com)

$$A_o = 1.8 \times 10^6 \quad | \quad f_T = 8 \text{ MHz} \quad | \quad \omega_B = \frac{\omega_T}{A_o} = \frac{2\pi(8 \text{ MHz})}{1.8 \times 10^6} = 8.89\pi \quad | \quad RC = \frac{1}{\omega_B} = \frac{1}{8.89\pi} \text{ s}$$

Note that as Specification Sheets are updated over time, the various values may change.

Page 761

$$0.01 = \exp\left(-\frac{\pi\xi}{\sqrt{1-\xi^2}}\right) \quad | \quad \text{Let } \kappa = \left(\frac{\ln 100}{\pi}\right)^2 \quad | \quad \xi = \sqrt{\frac{\kappa}{1+\kappa}} = 0.826$$

$$\phi_M = \tan^{-1} \frac{2\xi}{\left(\sqrt{4\xi^4 + 1} - 2\xi^2\right)^{0.5}} = 70.9^\circ$$

$$\cos(45^\circ) = \sqrt{4\xi^4 + 1} - 2\xi^2 \rightarrow \xi = 0.420 \quad | \quad \text{Overshoot} = 100\% \exp\left(-\frac{\pi\xi}{\sqrt{1-\xi^2}}\right) = 23.4 \%$$

Settling within the 10% error bars requires $\omega_n t \geq 13$. $\therefore \omega_n \geq \frac{13}{10^{-5}s} = 1.3 \times 10^6 \text{ rad/s}$

$$\omega_n = \sqrt{\omega_B \omega_2 (1 + A_o \beta)} \cong \sqrt{\omega_B \omega_2 A_o \beta} = \sqrt{\beta \omega_T \omega_2} \quad | \quad f_2 = \frac{f_n^2}{\beta f_T} \geq \frac{(1.3 \times 10^6 / 2\pi)^2}{0.1(10^6)} = 428 \text{ kHz}$$

Page 762

$$\angle T(j\omega_1) = -180^\circ \rightarrow 3 \tan^{-1} \frac{\omega_1}{1} = 180 \rightarrow \omega_1 = \sqrt{3}$$

$$|T(j\omega_{180})| = \frac{5}{\left(\sqrt{\omega_1^2 + 1}\right)^3} = \frac{5}{\left(\sqrt{3+1}\right)^3} = \frac{5}{8} \quad | \quad GM = \frac{8}{5} = 1.60 \text{ or } 4.08 dB$$

Page 766

From the upper graph, the final value of the first step is 5 mV, and the peak of the response is

$$\text{approximately } 4mV + 2mV \left(\frac{9.5mm}{11mm} \right) = 5.7 \text{ mV. Overshoot} = 100\% \frac{5.7mV - 5mV}{5mV} = 14 \%$$

$$0.14 = \exp\left(-\frac{\pi\xi}{\sqrt{1-\xi^2}}\right) \quad | \quad \text{Let } \kappa = \left(\frac{-\ln 0.14}{\pi}\right)^2 = 0.3917 \quad | \quad \xi = \sqrt{\frac{\kappa}{1+\kappa}} = 0.5305$$

$$\phi_M = \tan^{-1} \frac{2\xi}{\left(\sqrt{4\xi^4 + 1} - 2\xi^2\right)^{0.5}} = 54.2^\circ$$

From the lower graph, the final value of the first step is 5 mV, and the peak of the response is

$$\text{approximately } 5mV + 5mV \left(\frac{10mm}{12mm} \right) = 9.2 \text{ mV. Overshoot} = 100\% \frac{9.2mV - 5mV}{5mV} = 84 \%$$

$$0.84 = \exp\left(-\frac{\pi\xi}{\sqrt{1-\xi^2}}\right) \quad | \quad \text{Let } \kappa = \left(\frac{-\ln 0.84}{\pi}\right)^2 = 0.3080 \quad | \quad \xi = \sqrt{\frac{\kappa}{1+\kappa}} = 0.05541$$

$$\phi_M = \tan^{-1} \frac{2\xi}{\left(\sqrt{4\xi^4 + 1} - 2\xi^2\right)^{0.5}} = 6.34^\circ$$

The μA741 curves will be distorted by slew rate limiting.

CHAPTER 12

Page 784

$$A_{vA} = A_{vB} = A_{vC} = -\frac{R_2}{R_1} = -\frac{68k\Omega}{2.7k\Omega} = -25.2 \quad | \quad R_{inA} = R_{inB} = R_{inC} = R_i = 2.7 \text{ k}\Omega$$

The op - amps are ideal : $R_{outA} = R_{outB} = R_{outC} = 0$

$$A_v = A_{vA} A_{vB} A_{vC} = (-25.2)^3 = -16,000 \quad | \quad R_{in} = R_{inA} = 2.7 \text{ k}\Omega \quad | \quad R_{out} = R_{outC} = 0$$

$$A_v = (-25.2)^3 \left(\frac{2.7k\Omega}{R_{out} + 2.7k\Omega} \right)^2 \geq 0.99 (25.2)^3 \quad | \quad \left(\frac{2.7k\Omega}{R_{out} + 2.7k\Omega} \right)^2 \geq 0.99$$

$$\frac{2.7k\Omega}{R_{out} + 2.7k\Omega} \geq 0.9950 \rightarrow R_{out} \geq 13.6 \Omega$$

Page 789

$$A_v(0) = 50(25) = 1250 \quad | \quad |A_v(\omega_H)| = \frac{1250}{\sqrt{2}} = 884$$

$$\left[1 + \frac{\omega_H^2}{(10000\pi)^2} \right] \left[1 + \frac{\omega_H^2}{(20000\pi)^2} \right] = 2 \rightarrow (\omega_H^2)^2 + 4.935 \times 10^9 \omega_H^2 - 3.896 \times 10^{18} = 0$$

$$\omega_H^2 = 6.925 \times 10^8 \rightarrow \omega_H = 26.3 \times 10^3 \rightarrow f_H = \frac{26.3 \times 10^3}{2\pi} = 4190 \text{ Hz}$$

$$A_v(0) = -100(66.7)(50) = -3.33 \times 10^5 \quad | \quad |A_v(\omega_H)| = \frac{-3.34 \times 10^5}{\sqrt{2}} = -2.36 \times 10^5$$

$$\left[1 + \frac{\omega_H^2}{(10000\pi)^2} \right] \left[1 + \frac{\omega_H^2}{(15000\pi)^2} \right] \left[1 + \frac{\omega_H^2}{(20000\pi)^2} \right] = 2$$

$$\omega_H^6 + 7.156 \times 10^9 \omega_H^4 + 1.486 \times 10^{10} \omega_H^2 - 8.562 \times 10^{27} = 0$$

$$\text{Using MATLAB, } \omega_H = 21.7 \times 10^3 \rightarrow f_H = \frac{21.7 \times 10^3}{2\pi} = 3450 \text{ Hz}$$

$$A_v(0) = (-30)^3 = -2.70 \times 10^4 \quad | \quad f_H = (33.3 \text{ kHz}) \sqrt{2^{\frac{1}{3}} - 1} = 17.0 \text{ kHz}$$

Page 795

$$A_{v_1} = 1 + \frac{130k\Omega}{22k\Omega} = 6.909 \quad | \quad v_{o1} = 0.001(6.909) = 6.91 \text{ mV} \quad | \quad v_{o2} = 0.001V(6.909)^2 = 47.7 \text{ mV}$$

$$v_{o3} = 0.001(6.909)^3 = 330 \text{ mV} \quad | \quad v_{o4} = 0.001V(6.909)^4 = 2.28 \text{ V}$$

$$v_{o5} = 0.001V(6.909)^5 = 15.7 \text{ V} > 15 \text{ V}. \quad \therefore v_{o5} = V_O^{\max} = 15 \text{ V}$$

$$v_{o6} = 15V(6.909) = 104 \text{ V} > 15 \text{ V}. \quad \therefore v_{o6} = V_O^{\max} = 15 \text{ V}$$

Page 798

$$V_A = V_1 + IR_2 \quad | \quad V_B = V_2 - IR_2 \quad | \quad I = \frac{V_A - V_B}{2R_1} = \frac{5.001V - 4.999V}{2k\Omega} = 1.00 \mu A$$

$$V_A = V_1 + IR_2 = 5.001V + 1.00\mu A(49k\Omega) = 5.05 \text{ V}$$

$$V_B = V_2 - IR_2 = 4.999V - 1.00\mu A(49k\Omega) = 4.95 \text{ V}$$

$$V_O = \left(-\frac{R_4}{R_3}\right)(V_A - V_B) = \left(-\frac{10k\Omega}{10k\Omega}\right)(5.05 - 4.95) = -0.100 \text{ V}$$

Page 801

$$A_{LP}(s) = \frac{\omega_o^2}{s^2 + s\frac{\omega_o}{Q} + \omega_o^2} \quad | \quad A_{LP}(0) = \frac{\omega_o^2}{\omega_o^2} = 1 \text{ or } 0 \text{ dB}$$

$$\text{For } Q = \frac{1}{\sqrt{2}}: A_{LP}(j\omega) = \frac{\omega_o^2}{-\omega^2 + j\omega\sqrt{2}\omega_o + \omega_o^2} \quad | \quad |A_{LP}(j\omega_H)|^2 = \frac{\omega_o^4}{(\omega_o^2 - \omega_H^2)^2 + 2\omega_o^2\omega_H^2} = \left(\frac{1}{\sqrt{2}}\right)^2$$

$$2\omega_o^4 = \omega_o^4 + \omega_H^4 \rightarrow \omega_H = \omega_o$$

To increase the cutoff frequency from 5 kHz to 10 kHz while maintaining the resistances

the same, we must decrease the capacitances by a factor of $\frac{10\text{kHz}}{5\text{kHz}} = 2$

$$\therefore C_1 = \frac{0.02\mu F}{2} = 0.01 \mu F \quad | \quad C_2 = \frac{0.01\mu F}{2} = 0.005 \mu F$$

$$A_{LP}(j\omega) = \frac{\omega_o^2}{-\omega^2 + j\omega\frac{\omega_o}{Q} + \omega_o^2} \quad | \quad A_{LP}(j\omega_o) = \frac{\omega_o^2}{-\omega_o^2 + j\frac{\omega_o^2}{Q} + \omega_o^2} = -jQ \quad | \quad |A_{LP}(j\omega_o)| = Q$$

Page 802

To decrease the cutoff frequency from 5 kHz to 2 kHz, we must increase the

$$\text{resistances by a factor of } \frac{5\text{kHz}}{2\text{kHz}} = 2.50 \rightarrow R_1 = R_2 = 2.50(2.26k\Omega) = 5.65 k\Omega$$

$$Q = \sqrt{\frac{2C}{C} \frac{\sqrt{R^2}}{2R}} = \frac{\sqrt{2}}{2} = \frac{1}{\sqrt{2}} \quad | \quad Q \text{ is unchanged.}$$

$$\frac{1}{\sqrt{2}} = \sqrt{\frac{C}{C} \frac{\sqrt{R_1 R_2}}{R_1 + R_2}} \rightarrow R_1^2 + 2R_1 R_2 + R_2^2 = 2R_1 R_2 \rightarrow R_1^2 = -R_2^2 \quad \text{-- can't be done!}$$

$$Q = \frac{\sqrt{R_1 R_2}}{R_1 + R_2} \quad \frac{dQ}{dR_2} = \frac{1}{(R_1 + R_2)^2} \left[\frac{R_1(R_1 + R_2)}{2\sqrt{R_1 R_2}} - \sqrt{R_1 R_2} \right] = 0 \rightarrow R_2 = R_1 \rightarrow Q_{\max} = \frac{1}{2}$$

Page 803

$$|A_{HP}(j\omega_o)| = K \left| \frac{-\omega_o^2}{-\omega_o^2 + j(3-K)\omega_o^2 + \omega_o^2} \right| = \frac{K}{3-K} \quad | \quad A_{HP}(j\omega_o) = \frac{K}{3-K} \angle 90^\circ$$

$$f_o = \frac{1}{2\pi\sqrt{10k\Omega(20k\Omega)(0.0047\mu F)(0.001\mu F)}} = 5.19 \text{ kHz}$$

$$Q = \left[\sqrt{\frac{10k\Omega}{20k\Omega}} \frac{4.7nF + 1.0nF}{\sqrt{4.7nF(1.0nF)}} + (1-2) \sqrt{\frac{20k\Omega(1.0nF)}{10k\Omega(4.7nF)}} \right]^{-1} = 0.829$$

Page 804

$$S_K^Q = \frac{K}{Q} \frac{dQ}{dK} \quad | \quad Q = \frac{1}{3-K} \quad | \quad \frac{dQ}{dK} = \frac{-1}{(3-K)^2} (-1) = Q^2 \quad | \quad S_K^Q = \frac{K}{Q} \frac{dQ}{dK} = KQ$$

$$Q = \frac{1}{3-K} \rightarrow KQ = 3Q - 1 \quad S_K^Q = 3Q - 1 = \frac{3}{\sqrt{2}} - 1 = 1.12$$

Page 805

$$R_{th} = 2k\Omega \parallel 2k\Omega = 1k\Omega \quad | \quad f_o = \frac{1}{2\pi\sqrt{1k\Omega(82k\Omega)(0.02\mu F)(0.02\mu F)}} = 879 \text{ Hz} \quad | \quad Q = \frac{1}{2} \sqrt{\frac{82k\Omega}{1k\Omega}} = 4.53$$

Page 807

$$S_{C_1}^Q = \frac{C_1}{Q} \frac{dQ}{dC_1} = \frac{C_1}{Q} \left[\frac{1}{2\sqrt{C_1 C_2}} \frac{\sqrt{R_l R_2}}{R_l + R_2} \right] = \frac{C_1}{Q} \frac{Q}{2C_1} = 0.5$$

$$S_{R_2}^Q = \frac{R_2}{Q} \frac{dQ}{dR_2} \quad | \quad R_l = R_2 \rightarrow Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \rightarrow S_{R_2}^Q = 0$$

$$S_R^{\omega_o} = \frac{R}{\omega_o} \frac{d\omega_o}{dR} = \frac{R}{\omega_o} \left(\frac{-1}{R^2 C} \right) = -\frac{\omega_o}{\omega_o} = -1 \quad | \quad S_C^{\omega_o} = \frac{C}{\omega_o} \frac{d\omega_o}{dR} = \frac{C}{\omega_o} \left(\frac{-1}{RC^2} \right) = -\frac{\omega_o}{\omega_o} = -1$$

$$S_K^Q = \frac{K}{Q} \frac{dQ}{dK} = \frac{K}{Q} \frac{(-1)(-1)}{(3-K)^2} = \frac{K}{Q} Q^2 = KQ = \frac{K}{3-K}$$

$$S_{R_1}^{\omega_o} = \frac{R_1}{\omega_o} \frac{d\omega_o}{dR_1} = \frac{R_1}{\omega_o} \left(-\frac{\omega_o}{2R_{th}} \right) \frac{dR_{th}}{dR_1} = -\frac{R_1}{2R_{th}} \left(\frac{R_{th}^2}{R_l^2} \right) = -\frac{1}{2} \frac{R_3}{R_l + R_3}$$

$$S_{R_2}^{\omega_o} = \frac{R_2}{\omega_o} \frac{d\omega_o}{dR_2} = \frac{R_2}{\omega_o} \left(-\frac{\omega_o}{2R_2} \right) = -\frac{1}{2}$$

$$S_{R_3}^{\omega_o} = \frac{R_3}{\omega_o} \frac{d\omega_o}{dR_3} = \frac{R_3}{\omega_o} \left(-\frac{\omega_o}{2R_{th}} \right) \frac{dR_{th}}{dR_3} = -\frac{R_3}{2R_{th}} \left(\frac{R_{th}^2}{R_3^2} \right) = -\frac{1}{2} \frac{R_l}{R_l + R_3}$$

$$S_C^{\omega_o} = \frac{C}{\omega_o} \frac{d\omega_o}{dC} = \frac{C}{\omega_o} \left(-\frac{\omega_o}{C} \right) = -1$$

$$S_{R_1}^Q = \frac{R_1}{Q} \frac{dQ}{dR_1} = \frac{R_1}{Q} \left(-\frac{Q}{2R_{th}} \right) \frac{dR_{th}}{dR_1} = -\frac{R_1}{2R_{th}} \left(\frac{R_{th}^2}{R_l^2} \right) = -\frac{1}{2} \frac{R_3}{R_l + R_3}$$

$$S_{R_2}^Q = \frac{R_2}{Q} \frac{dQ}{dR_2} = \frac{R_2}{Q} \left(\frac{Q}{2R_2} \right) = +\frac{1}{2}$$

$$S_{R_3}^Q = \frac{R_3}{Q} \frac{dQ}{dR_3} = \frac{R_3}{Q} \left(-\frac{Q}{2R_{th}} \right) \frac{dR_{th}}{dR_3} = -\frac{R_3}{2R_{th}} \left(\frac{R_{th}^2}{R_3^2} \right) = -\frac{1}{2} \frac{R_l}{R_l + R_3}$$

$$S_C^Q = \frac{C}{Q} \frac{dQ}{dC} = \frac{C}{Q} (0) = 0 \quad | \quad S_C^{BW} = \frac{C}{BW} \frac{dBW}{dC} = \frac{C}{BW} \left(-\frac{BW}{C} \right) = -1$$

Page 808

$$(a) R_1 = R_2 = 5(2.26k\Omega) = 11.3 k\Omega \quad | \quad C_1 = \frac{0.02\mu F}{5} = 0.004 \mu F \quad | \quad C_2 = \frac{0.01\mu F}{5} = 0.002 \mu F$$

$$f_o = \frac{1}{2\pi\sqrt{(11.3k\Omega)(11.3k\Omega)(0.004\mu F)(0.002\mu F)}} = 4980 \text{ Hz}$$

$$Q = \sqrt{\frac{11.3k\Omega}{11.3k\Omega}} \frac{\sqrt{(0.004\mu F)(0.002\mu F)}}{0.004\mu F + 0.002\mu F} = \frac{\sqrt{2}}{3} = 0.471$$

$$(b) R_1 = R_2 = 0.885(2.26k\Omega) = 2.00 k\Omega \quad | \quad C_1 = \frac{0.02\mu F}{0.885} = 0.0226 \mu F \quad | \quad C_2 = \frac{0.01\mu F}{0.885} = 0.0113 \mu F$$

$$f_o = \frac{1}{2\pi\sqrt{(2.00k\Omega)(2.00k\Omega)(0.0226\mu F)(0.0113\mu F)}} = 4980 \text{ Hz}$$

$$Q = \sqrt{\frac{2.00k\Omega}{2.00k\Omega}} \frac{\sqrt{(0.0226\mu F)(0.0113\mu F)}}{0.0226\mu F + 0.0113\mu F} = \frac{\sqrt{2}}{3} = 0.471$$

$$f_o = \frac{1}{2\pi\sqrt{(2k\Omega)(2k\Omega)(82k\Omega)(0.02\mu F)(0.02\mu F)}} = 879 \text{ Hz} \quad | \quad Q = \sqrt{\frac{82k\Omega}{1k\Omega}} \frac{\sqrt{(0.02\mu F)(0.02\mu F)}}{0.02\mu F + 0.02\mu F} = 4.53$$

The values of the resistors are unchanged. $C_1 = C_2 = \frac{0.02\mu F}{4} = 0.005 \mu F$

$$f_o = \frac{1}{2\pi\sqrt{(1k\Omega)(82k\Omega)(0.005\mu F)(0.005\mu F)}} = 3520 \text{ Hz} \quad | \quad Q = \sqrt{\frac{82k\Omega}{1k\Omega}} \frac{\sqrt{(0.005\mu F)(0.005\mu F)}}{0.005\mu F + 0.005\mu F} = 4.53$$

Page 810

$$\Delta v_o = -\frac{C_1}{C_2} V_I = -\frac{2pF}{0.5pF} 0.1V = -0.4 V$$

$$v_o(T) = 0 + \Delta v_o = -0.4 V \quad | \quad v_o(5T) = 0 + 5\Delta v_o = -2.0 V \quad | \quad v_o(9T) = 0 + 9\Delta v_o = -3.6 V$$

Page 812

$$f_o = \frac{1}{2\pi} f_C \sqrt{\frac{C_3 C_4}{C_1 C_2}} = \frac{200kHz}{2\pi} \sqrt{\frac{4pF(0.25pF)}{3pF(3pF)}} = 10.6 kHz$$

$$Q = \sqrt{\frac{C_3}{C_4} \frac{\sqrt{C_1 C_2}}{C_1 + C_2}} = \sqrt{\frac{4pF}{0.25pF} \frac{\sqrt{3pF(3pF)}}{3pF + 3pF}} = 2 \quad | \quad \text{BW} = \frac{f_o}{Q} = \frac{10.6 kHz}{2} = 5.30 kHz$$

$$A_{BP}(j\omega_o) = -\frac{R_2}{2R_1} = -\frac{C_3}{2C_4} = -\frac{4pF}{0.5pF} = -8.00$$

Page 815

$$0.01100001_2 = \left(2^{-2} + 2^{-3} + 2^{-8}\right)_{10} = 0.37890625_{10} \quad | \quad 0.10001000_2 = \left(2^{-1} + 2^{-5}\right)_{10} = 0.53125_{10}$$

Page 816

(a) $V_o = \frac{5.12V}{2^{12}} (2^{11} + 2^9 + 2^7 + 2^5 + 2^3 + 2^1) = 3.41250 \text{ V}$
 $V_{LSB} = \frac{5.12V}{2^{12}} = 1.25 \text{ mV} \quad | \quad V_{MSB} = \frac{5.12V}{2} = 2.56 \text{ V}$

Page 818

Answers are correct

$$V_{OS} = V_o(000) = 0.100 \text{ V}_{FS} \quad | \quad V_{LSB} = \frac{0.8V_{FS} - 0.1V_{FS}}{7} = 0.1 \text{ V}_{FS}$$

Page 819

$$2R = 1 \text{ k}\Omega \quad | \quad 4R = 2 \text{ k}\Omega \quad | \quad 8R = 4 \text{ k}\Omega \quad | \quad 16R = 8 \text{ k}\Omega \quad | \quad 32R = 16 \text{ k}\Omega \quad | \quad 64R = 32 \text{ k}\Omega$$

$$128R = 64 \text{ k}\Omega \quad | \quad 256R = 128 \text{ k}\Omega \quad | \quad R = 500 \text{ }\Omega$$

Page 820

$$R_{Total} = R + 2R + 2R + (n-1)(2R+R) = (3n+2)R \quad | \quad R_{Total} = (3 \times 8 + 2)(1\text{k}\Omega) = 26 \text{ k}\Omega$$

$$R = 1 \text{ k}\Omega \quad | \quad 2R = 2 \text{ k}\Omega \quad | \quad 4R = 4 \text{ k}\Omega \quad | \quad 8R = 8 \text{ k}\Omega \quad | \quad 16R = 16 \text{ k}\Omega \quad | \quad 32R = 32 \text{ k}\Omega$$

$$64R = 64 \text{ k}\Omega \quad | \quad 128R = 128 \text{ k}\Omega \quad | \quad 256R = 256 \text{ k}\Omega \quad | \quad R_{Total} = 511 \text{ k}\Omega$$

$$\text{In general: } R_{Total} = R(2^0 + 2^1 + \dots + 2^{n-1} + 2^n) = (2^{n+1} - 1)R \quad | \quad R_{Total} = (2^{8+1} - 1)1\text{k}\Omega = 511 \text{ k}\Omega$$

Page 821

The general case requires 2^n resistors, and the number of switches is

$$(2^1 + 2^2 + \dots + 2^n) = 2(2^0 + 2^1 + \dots + 2^{n-1}) = 2(2^n - 1) = 2^{n+1} - 2$$

$$2^{10} = 1024 \text{ resistors} \quad | \quad 2^{10+1} - 2 = 2046 \text{ switches.}$$

Page 822

(a) In general: $C_{Total} = C(2^0 + 2^1 + \dots + 2^n) = (2^{n+1} - 1)C \quad | \quad C_{Total} = (2^{8+1} - 1)1\text{pF} = 511 \text{ pF}$

(b) In general: $C_{Total} = 2C + 2C + (n-1)(2C+C) = (3n+1)C \quad | \quad C_{Total} = 25(1\text{pF}) = 25 \text{ pF}$

(c) $A = \frac{25\text{pF}}{5\text{fF}/\mu\text{m}^2} = \frac{25 \times 10^{-12}}{5 \times 10^{-15}} \mu\text{m}^2 = 5000 \text{ }\mu\text{m}^2$

Page 823

$$V_{LSB} = \frac{5V}{2^8} = 19.53 \text{ mV} \quad | \quad 1.2V \frac{2^8 LSB}{5V} = 61.44 \text{ LSB} \quad | \quad \text{The closest code is } 61_{10} = 00111101_2$$

Page 825

$$2^n \geq 10^6 \quad | \quad n \geq \frac{6 \log 10}{\log 2} = 19.93 \rightarrow n \geq 20 \text{ bits}$$

The minimum width is 0 corresponding to the missing code 110.

The maximum code width is 2.5 LSB corresponding to output code 101.

$$DNL = 2.5 - 1 = 1.5 \text{ LSB}$$

At code 110, the ADC transfer characteristic is 1 LSB off of the fitted line.

$$\therefore INL = 1 \text{ LSB}$$

Page 826

$$T_T^{\max} = \frac{2^n}{f_C} = \frac{2^{12}}{2 \times 10^6} = 2.048 \text{ ms} \quad | \quad N_{\max} = \frac{1}{T_T^{\max}} = \frac{1}{2.048 \text{ ms}} = 488 \frac{\text{conversions}}{\text{second}}$$

Page 827

$$T_T = \frac{n}{f_C} = \frac{12}{2 \times 10^6} = 6.00 \mu\text{s} \quad | \quad N_{\max} = \frac{1}{T_T} = \frac{1}{6 \mu\text{s}} = 167,000 \frac{\text{conversions}}{\text{second}}$$

Page 830

$$V_{FS} = \frac{1}{RC} \int_0^T V_R(t) dt = \frac{V_R T}{RC} \quad | \quad RC = \frac{V_R}{V_{FS}} T = \frac{V_R}{V_{FS}} \frac{2^n}{f_C} = \frac{2.00V}{5.12V} \left(\frac{2^8}{1 \text{ MHz}} \right) = 0.100 \text{ ms}$$

Page 831

$$T_T^{\max} = \frac{2^{n+1}}{f_C} = \frac{2^{17}}{10^6 \text{ Hz}} = 0.131 \text{ s} \quad | \quad N_{\max} = \frac{1}{T_T^{\max}} = \frac{1}{0.131 \text{ s}} = 7.63 \frac{\text{conversions}}{\text{second}}$$

Page 832

In general, 2^n resistors and $(2^n - 1)$ comparators :

$2^{10} = 1024$ resistors and $(2^{10} - 1) = 1023$ comparators

Page 840

$$f_o = \frac{1}{2\pi(10k\Omega)(1nF)} = 15.9kHz \quad | \quad |v_o| = \frac{3(0.6V)}{\left(2 - \frac{10k\Omega}{10k\Omega}\right)\left(1 + \frac{24k\Omega}{12k\Omega}\right) - \frac{24k\Omega}{10k\Omega}} = 3.00 V$$

SPICE Results : 15.90 kHz, 3.33 V

Page 841

For $v_I > 0$, the diode will conduct and pull the output up to $v_O = v_I = 1.0 V$.

$$v_I = v_O + v_D = 1.0 + 0.6 = 1.6 V$$

For a negative input, there is no path for current through R, so $v_O = 0 V$. The op-amp sees a -1V input so the output will limit at the negative power supply : $v_O = -10 V$.

(Note that the output voltage will actually be determined by the reverse saturation current of the diode : $v_O = -I_S R \approx 0$.)

The diode has a 10- V reverse bias across it, so $V_Z > 10 V$.

Page 843

$v_S = +2 V$: Diode D₂ conducts, and D₁ is off. The negative input is a virtual ground.

$v_I = -v_{D2} = -0.6 V$. The current in R is 0, so $v_O = 0 V$.

$v_I = -2 V$: Diode D₁ conducts, and D₂ is off. The negative input is a virtual ground.

$$v_O = -\frac{R_2}{R_1}v_I = -\frac{68k\Omega}{22k\Omega}(-2V) = +6.18 V \quad | \quad v_I = v_O + v_{D1} = 6.78 V.$$

The maximum output voltage is $v_O^{\max} = 15V - 0.6V = 14.4 V$.

$$A_v = -\frac{68k\Omega}{22k\Omega} = -3.09 \quad | \quad v_I = \frac{14.4V}{-3.09} = -4.66 V$$

When $v_O = 15 V$, $v_{D2} = -15 V$, so $V_Z = 15 V$.

Page 844

$$v_O = \frac{20k\Omega}{20k\Omega} \left(\frac{10.2k\Omega}{3.24k\Omega} \right) \frac{2V}{\pi} = 2.00 V$$

Page 846

$$V_{I-} = -\frac{R_1}{R_1 + R_2} V_{EE} = -\frac{1k\Omega}{1k\Omega + 9.1k\Omega} 10V = -0.990 V$$

$$V_{I+} = +\frac{R_1}{R_1 + R_2} V_{CC} = \frac{1k\Omega}{1k\Omega + 9.1k\Omega} 10V = +0.990 V$$

$$V_n = 0.990V - (-0.990V) = 1.98 V$$

Page 847

$$T = 2RC \ln \frac{1+\beta}{1-\beta} \quad | \quad \beta = \frac{R_1}{R_1 + R_2} = \frac{6.8k\Omega}{6.8k\Omega + 6.8k\Omega} = \frac{1}{2}$$

$$T = 2(10k\Omega)(0.001\mu F) \ln \left(\frac{1+0.5}{1-0.5} \right) = 21.97\mu s \quad | \quad f = \frac{1}{T} = 45.5 \text{ kHz}$$

Page 851

$$\beta = \frac{R_1}{R_1 + R_2} = \frac{22k\Omega}{22k\Omega + 18k\Omega} = 0.550 \quad | \quad T = (11k\Omega)(0.002\mu F) \ln \left[\frac{1 + \frac{0.7}{5}}{1 - 0.550} \right] = 20.4 \mu s$$

$$T_r = (11k\Omega)(0.002\mu F) \ln \left[\frac{1 + 0.55 \left(\frac{5V}{5V} \right)}{1 - \frac{0.7}{5}} \right] = 13.0 \mu s \quad | \quad T_{\min} = 20.4\mu s + 13.0\mu s = 33.4 \mu s$$

CHAPTER 13

Page 870

$$I_C = \alpha_F I_E = \frac{60}{61} \left[\frac{15 - 0.7}{2(75k\Omega)} \right] = 93.8 \mu A \quad | \quad V_{CE} = 15 - 93.8\mu A (75k\Omega) - (-0.7V) = 8.67 V$$

$$I_C = \alpha_F I_E = \frac{60}{61} \left[\frac{15 - V_{BE}}{2(75k\Omega)} \right] \quad \text{and} \quad V_{BE} = 0.025V \ln \left(\frac{I_C}{0.5 \times 10^{-15} A} \right) \rightarrow I_C = 94.7 \mu A, V_{BE} = 0.649 V$$

$$I_S = \frac{I_C}{\exp \left(\frac{V_{BE}}{V_T} \right)} = \frac{94.7 \mu A}{\exp \left(\frac{0.700V}{25.9mV} \right)} = 0.173 fA$$

Page 872

$$v_{id} = v_1 - v_2 = 1.01 - 0.990 = 0.020 V \quad | \quad v_{ic} = \frac{v_1 + v_2}{2} = \frac{1.01 + 0.99}{2} = 1.00 V$$

$$v_{id} = v_1 - v_2 = 4.995 - 5.005 = -0.010 V \quad | \quad v_{ic} = \frac{v_1 + v_2}{2} = \frac{4.995 + 5.005}{2} = 5.00 V$$

$$v_{od} = A_{dd}v_{id} + A_{cd}v_{ic} \quad | \quad v_{oc} = A_{dc}v_{id} + A_{cc}v_{ic}$$

$$\begin{bmatrix} v_{od} \\ v_{oc} \end{bmatrix} = \begin{bmatrix} A_{dd} & A_{cd} \\ A_{dc} & A_{cc} \end{bmatrix} \begin{bmatrix} v_{id} \\ v_{ic} \end{bmatrix} \quad | \quad \begin{bmatrix} 2.2 \\ 1.002 \end{bmatrix} = \begin{bmatrix} A_{dd} & A_{cd} \\ A_{dc} & A_{cc} \end{bmatrix} \begin{bmatrix} 0.02 \\ 1 \end{bmatrix} \quad | \quad \begin{bmatrix} 0 \\ 5.001 \end{bmatrix} = \begin{bmatrix} A_{dd} & A_{cd} \\ A_{dc} & A_{cc} \end{bmatrix} \begin{bmatrix} -0.01 \\ 5 \end{bmatrix}$$

$$v_{id} = v_1 - v_2 = 4.995 - 5.005 = -0.01 V \quad | \quad v_{ic} = \frac{v_1 + v_2}{2} = 4.995 + 5.005 = 5.00 V$$

$$v_{od} = A_{dd}v_{id} + A_{cd}v_{ic} \quad | \quad v_{oc} = A_{dc}v_{id} + A_{cc}v_{ic}$$

$$\begin{bmatrix} 2.20 \\ 0 \end{bmatrix} = \begin{bmatrix} 0.02 & 1.00 \\ -0.01 & 5.00 \end{bmatrix} \begin{bmatrix} A_{dd} \\ A_{cd} \end{bmatrix} \quad | \quad \begin{bmatrix} 1.002 \\ 5.001 \end{bmatrix} = \begin{bmatrix} 0.02 & 1.00 \\ -0.01 & 5.00 \end{bmatrix} \begin{bmatrix} A_{dc} \\ A_{cc} \end{bmatrix}$$

$$A_{dd} = 100 \quad | \quad A_{cd} = 0.200 \quad | \quad A_{dc} = 0.0818 \quad | \quad A_{cc} = 1.00$$

Page 877

Differential output: $A_{dm} = A_{dd} = -20V_{CC} = -300 \quad | \quad A_{cm} = 0 \quad | \quad CMRR = \infty$

Single-ended output: $A_{dm} = \frac{A_{dd}}{2} = +10V_{CC} = 150 \quad | \quad A_{cm} = -\frac{150}{300} = -0.5$

$CMRR = 20V_{EE} = 300 \quad | \quad CMRR_{dB} = 20 \log(300) = 49.5 dB$

Page 880

$$V_{IC} = 15V \left[\frac{1 - \frac{100}{101} \left(\frac{R_C}{2R_C} \right) \frac{15 - 0.7}{15}}{1 + \frac{100}{101} \left(\frac{R_C}{2R_C} \right)} \right] = 5.30 \text{ V}$$

Page 881

$$I_{DC} = I_{SS} - \frac{V_o}{R_{SS}} = 100\mu A - \frac{15V}{750k\Omega} = 80 \text{ } \mu A$$

Page 884

$$I_D = \frac{I_{SS}}{2} = 100 \text{ } \mu A \quad | \quad V_{DS} = 12 - I_D R_D + V_{GS} = 12 - 100\mu A (62k\Omega) + V_{GS} = 5.8V + V_{GS}$$

$$V_{GS} = V_{TN} + \sqrt{\frac{2I_D}{K_n}} = V_{TN} + 0.2V \quad | \quad V_{TN} = 1 + 0.75 \left(\sqrt{V_{SB} + 0.6} - \sqrt{0.6} \right) \quad | \quad V_{SB} = -V_{GS} - (-12V)$$

$$V_{SB} = 11.8 - V_{TN} \quad | \quad V_{TN} = 1 + 0.75 \left(\sqrt{12.4 - V_{TN}} - \sqrt{0.6} \right) \rightarrow V_{TN} = 2.75V \quad | \quad V_{DS} = 8.75 \text{ V}$$

Q-point: $(100 \text{ } \mu A, 8.75 \text{ V})$

Page 885 The problem should refer to Fig. 13.6.

The MOS schematic will be identical except resistors r_π are removed.

The analyses are identical to Section 13.1.5 except $g_\pi = 0$ and $R_{id} = \infty$.

Page 888

$$R_{od} = 2r_o \cong 2 \frac{V_A}{I_C} = 2 \frac{60V}{37.5\mu A} = 3.20 \text{ } M\Omega \quad | \quad R_{oc} \cong 2\mu_f R_{EE} = 2(40)(60)(1M\Omega) = 4.80 \text{ } G\Omega$$

$$i_{dm} = g_m v_{dm} = 40(37.5\mu A)v_{dm} = 1.5 \times 10^{-3}v_{dm} \quad | \quad i_{cm} \cong \frac{v_{cm}}{2R_{EE}} = \frac{v_{cm}}{2M\Omega} = 5.00 \times 10^{-7}v_{cm}$$

Page 892

$$I_{C1} = I_{C2} = \frac{100}{101} \left(\frac{150\mu A}{2} \right) = 74.3 \text{ } \mu A \quad | \quad I_{C3} = \frac{15V}{20k\Omega} = 750 \text{ } \mu A \quad | \quad V_{CE3} = 15 - 0 = 15.0 \text{ V}$$

$$V_{CE1} = 15 - 74.3\mu A (10k\Omega) - (-0.7) = 15.0 \text{ V} \quad | \quad V_{CE2} = 15 - (74.3\mu A - 7.5\mu A)(10k\Omega) - (-0.7) = 15.0 \text{ V}$$

$$V_{EB3} = (74.3\mu A - 7.5\mu A)(10k\Omega) = 0.668 \text{ V} \quad | \quad I_{S3} = \frac{750\mu A}{\exp\left(\frac{0.668V}{0.025}\right)} = 1.87 \times 10^{-15} \text{ A}$$

$(74.3 \text{ } \mu A, 15 \text{ V}), (74.3 \text{ } \mu A, 15 \text{ V}), (750 \text{ } \mu A, 15 \text{ V})$

Page 895

$$A_{dm}^{\max} = 560 \left(15\right) = 8400 \quad | \quad I_{C1} \leq 50 \left(1\mu A\right) = 50 \mu A \quad | \quad A_{dm} = \frac{8400}{1 + \frac{28}{100} \left(\frac{500\mu A}{50\mu A}\right)} = 2210$$

$$I_{C1} \leq 50 \left(1\mu A\right) = 50 \mu A \quad | \quad A_{dm} = \frac{8400}{1 + \frac{28}{100} \left(\frac{5mA}{50\mu A}\right)} = 290$$

$$R_{in} = 2r_\pi = 2 \frac{50}{40 \left(50\mu A\right)} = 50 k\Omega \quad | \quad R_{out} \cong \frac{15V}{0.5mA} = 30 k\Omega$$

$$R_{in} = 2r_\pi = 2 \frac{50}{40 \left(50\mu A\right)} = 50 k\Omega \quad | \quad R_{out} \cong \frac{15V}{5mA} = 3.0 k\Omega$$

$$A_{dm}^{\max} = 560 \left(1.5\right) = 840$$

Page 896

$$CMRR \cong g_{m2}R_1 = 40 \left(50\mu A\right) \left(750k\Omega\right) = 1500 \quad | \quad CMRR_{dB} = 20 \log(1500) = 63.5 dB$$

Page 897

$$A_{dm} = \frac{g_{m2}}{2} \left(\frac{R_C r_{\pi 3}}{R_C + r_{\pi 3}} \right) \left(g_{m3} r_{o3} \right) = \frac{40}{2} \left(\frac{I_{C2} R_C r_{\pi 3}}{R_C + r_{\pi 3}} \right) \left(40 I_{C3} r_{o3} \right) \cong 800 \left(\frac{0.7 r_{\pi 3}}{R_C + r_{\pi 3}} \right) \left(V_{A3} \right) = \frac{560 V_{A3}}{1 + \frac{R_C}{r_{\pi 3}}}$$

$$A_{dm} = \frac{560 V_{A3}}{1 + \frac{40 I_{C3} R_C}{\beta_{o3}}} = \frac{560 V_{A3}}{1 + \frac{40 I_{C2} R_C}{\beta_{o3}} \left(\frac{I_{C3}}{I_{C2}} \right)} = \frac{560 V_{A3}}{1 + \frac{40(0.7)}{\beta_{o3}} \left(\frac{I_{C3}}{I_{C2}} \right)} = \frac{560 V_{A3}}{1 + \frac{28}{\beta_{o3}} \left(\frac{I_{C3}}{I_{C2}} \right)}$$

$$A_{dm}^{\max} = 560 \left(75\right) = 42000 \quad | \quad I_{C1} \leq 50 \left(1\mu A\right) = 50 \mu A$$

$$A_{dm} = \frac{42000}{1 + \frac{28}{100} \left(\frac{500\mu A}{50\mu A}\right)} = 11000 \quad | \quad A_{dm} = \frac{42000}{1 + \frac{28}{100} \left(\frac{5mA}{50\mu A}\right)} = 1450$$

$$R_{in} = 2r_\pi = 2 \frac{50}{40 \left(50\mu A\right)} = 50 k\Omega \quad | \quad R_{out} \cong r_{o3} = \frac{75V + 15V}{0.5mA} = 180 k\Omega$$

$$R_{in} = 2r_\pi = 2 \frac{50}{40 \left(50\mu A\right)} = 50 k\Omega \quad | \quad R_{out} \cong \frac{90V}{5mA} = 18.0 k\Omega$$

Page 902

$$A_{vt1} = -3.50 \quad | \quad A_{vt2} = -22mS(150k\Omega \| 162k\Omega \| 203k\Omega) = -1238$$

$$A_{vt3} = \frac{0.198S(2k\Omega \| 18k\Omega)}{1 + 0.198S(2k\Omega \| 18k\Omega)} = 0.9971 \quad | \quad A_{dm} = -3.50(-1238)(0.9971) = 4320$$

$$R_{in} = 2r_\pi = 2 \frac{100}{40(49.5\mu A)} = 101 k\Omega \quad | \quad R_{out} \cong \frac{1}{g_{m4}} + \frac{r_{o3}\|R_2}{\beta_{o4} + 1} = \frac{1}{40(4.95mA)} + \frac{162k\Omega \| 150k\Omega}{101} = 776 \Omega$$

$$P \cong (I_1 + I_2 + I_3)(V_{CC} + V_{EE}) = (100 + 500 + 5000)\mu A(30V) = 168 mW$$

$$I_C = 50\mu A \left(\frac{150}{151} \right) = 49.7 \mu A \quad | \quad I_{C3} = 500\mu A + \frac{5mA}{151} = 533 \mu A \quad | \quad R_C = \frac{0.7V}{\left(49.7 - \frac{533}{150} \right)\mu A} = 15.2 k\Omega$$

$$r_{\pi3} = \frac{150}{40(533\mu A)} = 7.04 k\Omega \quad | \quad A_{vt2} = -20(49.7\mu A)(15.2k\Omega \| 7.04k\Omega) = -4.68$$

$$I_{C4} = \frac{150}{151} 5mA = 4.97 mA \quad | \quad r_{\pi4} = \frac{150}{40(4.97mA)} = 755 \Omega \quad | \quad r_{o3} = \frac{75 + 14.3}{533\mu A} = 168 k\Omega$$

$$A_{vt2} = -40(533\mu A) [168k\Omega \| 755 + 151(2k\Omega)] = -2304$$

$$g_{m4} = 40(4.97mA) = 0.199 S \quad | \quad A_{vt3} = \frac{0.199S(2k\Omega)}{1 + 0.199S(2k\Omega)} = 0.998$$

$$A_{dm} = -4.78(-2304)(0.998) = 11000$$

$$R_{id} = 2r_{\pi1} = 2 \frac{150}{40(49.7\mu A)} = 151 k\Omega \quad | \quad R_{out} \cong \frac{1}{g_{m4}} + \frac{r_{o3}\|R_2}{\beta_{o4} + 1} = \frac{1}{40(4.95mA)} + \frac{168k\Omega}{151} = 1.12 k\Omega$$

CMRR is set by the input stage and doesn't change since the bias current is the same.

$$r_{o3} = \frac{50 + 14.3}{550\mu A} = 117 k\Omega \quad | \quad A_{vt2} = -22mS(117k\Omega \| 203k\Omega) = -1630 \quad | \quad A_{dm} = -3.50(-1630)(0.998) = 5700$$

$$2 \frac{100}{40(49.5\mu A)} = 101 k\Omega \quad | \quad R_{out} \cong \frac{1}{g_{m4}} + \frac{r_{o3}\|R_2}{\beta_{o4} + 1} = \frac{1}{40(4.95mA)} + \frac{117k\Omega}{101} = 1.16 k\Omega$$

CMRR and input resistance are set by the input stage and don't change.

$$A_v = \frac{T}{1 + T} = \frac{6920}{6921} = 0.99986 \quad | \quad T_{OC} = T \quad | \quad T_{SC} = 0 \quad | \quad R_{out} = \frac{R_o}{1 + T} = \frac{1.62k\Omega}{1 + 6920} = 0.234 \Omega$$

$$R_{in} \cong R_{id}(1 + T_{SC}) = 101k\Omega(6921) = R_{id}(1 + T) = 699 M\Omega \quad (\text{Assuming } T_{OC} \ll 1)$$

Page 904

$$V_{GS3} = 1 + \sqrt{\frac{2(500\mu A)}{2.5mA}} = 1.63 V \quad | \quad R_D = \frac{1.63V}{100\mu A} = 16.3 k\Omega$$

$$A_{vt1} = -\frac{1}{2}\sqrt{2(0.005)(100\mu A)}(16.3k\Omega) = -8.16$$

$$A_{vt2} = -g_m r_o = -\sqrt{2(0.0025)(0.0005)}\left(\frac{1}{0.01(0.5mA)}\right) = -316$$

$$g_{m4} = \sqrt{2(0.005mA)(0.005mA)} = 7.07 mS \quad | \quad A_{vt3} = \frac{7.07mS(2k\Omega)}{1+7.07mS(2k\Omega)} = 0.934$$

$$A_{dm} = -8.16(-316)(0.934) = 2410 \quad | \quad R_{id} = \infty \quad | \quad R_o = \frac{1}{g_{m4}} = \frac{1}{7.07mS} = 141 \Omega$$

$$CMRR = g_m R_1 = 1.00mS(375k\Omega) = 375 \text{ or } 51.5 dB$$

$$P \cong (I_1 + I_2 + I_3)(V_{DD} + V_{SS}) = (5.7mA)(24V) = 137 mW$$

Page 905

$$A_{dd1} = -\sqrt{\frac{K'_n}{K'_P}} \sqrt{\frac{(W/L)_2}{(W/L)_{L2}}} \quad | \quad 10 = \sqrt{2.5} \sqrt{\frac{(W/L)_2}{4}} \rightarrow (W/L)_2 = \frac{160}{1}$$

Page 911

$$V_{GS1} + V_{SG2} = 0.5mA(4.4k\Omega) = 2.2 V \quad | \quad \text{Since the device parameters are the same,}$$

$$V_{GS1} = V_{SG2} = 1.1 V \quad | \quad I_D = \frac{0.025}{2}(1.1 - 1)^2 = 125 \mu A$$

$$\text{Since the device parameters are the same, } V_{BE1} = V_{EB2} = \frac{0.5mA(2.4k\Omega)}{2} = 0.6 V$$

$$I_C = (10^{-14} A) \exp\left(\frac{0.6}{0.025}\right) = 265 \mu A$$


Page 914

$$A_{v1} = \frac{v_d}{v_g} = -g_m n^2 R_L = -(50mA/V^2)(2V - 1V)(10)^2(8\Omega) = -40.0$$

$$A_{vo} = A_{v1} \frac{1}{n} = -\frac{40.0}{10} = -4.00 \quad | \quad |v_g| \leq 0.2(2 - 1)V = 0.200 V \quad | \quad |v_d| \leq 0.2V(40) = 8.00 V$$

$$|v_o| \leq \frac{8V}{10} = 0.800 V$$

Page 918

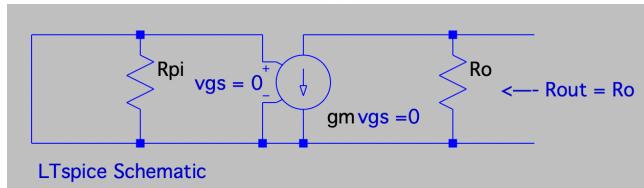

Bipolar Schematic. The MOS schematic is the same except R_{pi} is not included. $R_{out} = R_o$ in both cases.

Page 922

$$R_B \rightarrow 0 \quad | \quad R_{out} = 432k\Omega \left[1 + \frac{150(18.4k\Omega)}{18.8k\Omega + 18.4k\Omega} \right] = 32.5 M\Omega$$

$$V_{EQ} = -15V \frac{270k\Omega}{110k\Omega + 270k\Omega} = -10.66 V \quad | \quad R_{EQ} = 110k\Omega \parallel 270k\Omega = 78.2 k\Omega$$

$$I_C = 150 \frac{-10.66 - 0.7 - (-15)}{78.2k\Omega + 151(18k\Omega)} = 195 \mu A \quad | \quad V_B = V_{EQ} - I_B R_{EQ} = -10.66 - \frac{195 \mu A}{150} (78.2 k\Omega) = -10.8 V$$

$$P_{R_1} = \frac{(-10.8 + 15)^2}{110k\Omega} = 0.160 mW \quad | \quad P_{R_2} = \frac{(-10.8)^2}{270k\Omega} = 0.432 mW$$

$$P_{R_E} = \frac{(-10.8 - 0.7 + 15)^2}{18k\Omega} = 1.33 mW \quad | \quad r_o = \frac{(75 + 11.5)V}{195\mu A} = 446 k\Omega \quad | \quad r_\pi = \frac{150}{40(195\mu A)} = 19.3 k\Omega$$

$$R_{out} = 446k\Omega \left[1 + \frac{150(18k\Omega)}{78.2k\Omega + 19.3k\Omega + 18k\Omega} \right] = 10.9 M\Omega$$

$$R_1 + R_2 \cong \frac{15V}{20\mu A} = 750k\Omega \quad | \quad \text{Using a spreadsheet with } I_o = 200 \mu A \text{ yields } V_{BB} = 9V.$$

$$R_1 = 750k\Omega \left(\frac{9V}{15V} \right) = 450 k\Omega \quad | \quad R_1 = 300 k\Omega \quad | \quad R_E = \frac{150}{151} \left[\frac{9 - 0.7 - 1.33\mu A(180k\Omega)}{200\mu A} \right] = 40.0 k\Omega$$

$$R_{out} = \left(\frac{75 + 15 - 8.3}{2 \times 10^{-4}} \right) \left[1 + \frac{150(40.0k\Omega)}{180k\Omega + 18.75k\Omega + 40.0k\Omega} \right] = 10.7 M\Omega$$

Page 925

$$V_{DS} \geq V_{GS} - V_{TN} = 1 + \sqrt{\frac{2(0.2mA)}{2.49mA/V^2}} = 1.40 \text{ V}$$

$$V_D = V_S + 1.40 = -15 + 0.2mA(18.2k\Omega) + 1.40 = -9.96 \text{ V}$$

$$\frac{W}{L} = \frac{K_n}{K_n'} = \frac{2.49mA/V^2}{25\mu A/V^2} = \frac{99.6}{1}$$

$$V_C \geq -15 + \frac{I_o}{\alpha_F} R_E + 0.7 \geq -15 + \frac{151}{150}(200\mu A)(18.4k\Omega) + 0.7 = -10.6 \text{ V}$$

$$P_{R_s} = (0.2mA)^2 18.2k\Omega = 0.728 \text{ mW} \quad | \quad I_{BIAS} = \frac{15V}{499k\Omega + 249k\Omega} = 20.1 \mu A$$

$$P_{R_4} = (20.1\mu A)^2 499k\Omega = 0.202 \text{ mW} \quad | \quad P_{R_3} = (20.1\mu A)^2 249k\Omega = 0.101 \text{ mW}$$

$$V_{GG} = -15V \frac{510k\Omega}{510k\Omega + 240k\Omega} = -10.2 \text{ V} \quad | \quad -10.2 - V_{GS} - 18000I_D = -15 \text{ V}$$

$$4.8 - V_{GS} - 18000 \frac{2.49mA}{2} (V_{GS} - 1)^2 = 0 \quad | \quad V_{GS} = 1.390 \text{ V} \quad | \quad I_D = 189 \mu A$$

$$R_{out} \cong \mu_f R_s \cong \frac{1}{0.01} \sqrt{\frac{2(2.49 \times 10^{-3})}{189 \times 10^{-6}}} [1 + 0.01(11.6)](18k\Omega) = 10.3 M\Omega$$

CHAPTER 14

Page 948

$$R_{avg} = 10k\Omega(1 + 0.2) = 12 \text{ k}\Omega \quad | \quad 12k\Omega(1 - 0.01) \leq R \leq 12k\Omega(1 + 0.01) \quad | \quad 11.88 \text{ k}\Omega \leq R \leq 12.12 \text{ k}\Omega$$

Page 951

$$V_{DS1} = V_{TN} + \sqrt{\frac{2I_{REF}}{K_n(1 + \lambda V_{DS1})}} \quad | \quad V_{DS1} = 1 + \sqrt{\frac{2(150\mu A)}{250\mu A/V^2[1 + 0.0133V_{DS1}]}} \rightarrow V_{DS1} = 2.08 \text{ V}$$

$$I_O = 150\mu A \frac{1 + 0.0133(10)}{1 + 0.0133(2.08)} = 165 \text{ } \mu A$$

$$V_{DS} \geq V_{GS} - V_{TN} \quad | \quad V_D - (-10V) \geq \sqrt{\frac{2I_D}{K_n}} \quad | \quad V_D \geq -10V + \sqrt{\frac{2(150\mu A)}{250\mu A/V^2}} = -8.91 \text{ V}$$

Page 952

$$MR_1 = \frac{25/1}{3/1} = 8.33 \quad | \quad MR_2 = \frac{2/1}{5/1} = 0.400 \quad | \quad MR_3 = \frac{7.5/1}{3/1} = 2.5$$

$$V_{DS1} = 1V + \sqrt{\frac{2(50\mu A)}{3(25\mu A/V^2)}} = 2.16 \text{ V} \quad | \quad MR_1 = 8.33 \frac{1 + 0.02(15)}{1 + 0.02(2.16)} = 10.4$$

$$V_{DS2} = 1V + \sqrt{\frac{2(50\mu A)}{5(25\mu A/V^2)}} = 1.89 \text{ V} \quad | \quad MR_2 = 0.400 \frac{1 + 0.02(10)}{1 + 0.02(1.89)} = 0.462$$

$$V_{DS3} = 1V + \sqrt{\frac{2(50\mu A)}{3(25\mu A/V^2)}} = 2.16 \text{ V} \quad | \quad MR_3 = 2.5 \frac{1 + 0.02(12)}{1 + 0.02(2.16)} = 2.97$$

Page 954

$$I_{REF} = I_S \exp\left(\frac{V_{BE1}}{V_T}\right) \left(1 + \frac{V_{BE1}}{V_{A1}} + \frac{2}{\beta_{FO}}\right)$$

$$100\mu A = (0.1fA) \exp(40V_{BE1}) \left(1 + \frac{V_{BE1}}{50V} + \frac{2}{100}\right) \rightarrow V_{BE1} = 0.690$$

$$V_{CE} \geq V_{BE} \rightarrow V_C \geq -V_{EE} + 0.690 \text{ V}$$

Page 955

$$(a) MR_1 = \frac{0.5A}{A} = 0.5 \quad | \quad MR_2 = \frac{5A}{2A} = 2.50 \quad | \quad MR_3 = \frac{4.3A}{A} = 4.30$$

$$(b) MR_1 = \frac{0.5}{1 + \frac{1.5}{75}} = 0.490 \quad | \quad MR_2 = \frac{2.50}{1 + \frac{3.5}{75}} = 2.39 \quad | \quad MR_3 = \frac{4.3}{1 + \frac{5.3}{75}} = 4.02$$

$$(c) MR_1 = 0.5 \frac{1 + \frac{15}{60}}{1 + \frac{0.7}{60} + \frac{1.5}{75}} = 0.606 \quad | \quad MR_2 = 2.5 \frac{1 + \frac{15}{60}}{1 + \frac{0.7}{60} + \frac{3.5}{75}} = 2.95 \quad | \quad MR_3 = 4.30 \frac{1 + \frac{5}{60}}{1 + \frac{0.7}{60} + \frac{5.3}{75}} = 4.30$$

Page 956

$$I_{o2} = 100\mu A \left(\frac{10/1}{5/1} \right) = 200 \mu A \quad | \quad I_{o3} = 100\mu A \left(\frac{20/1}{5/1} \right) = 400 \mu A$$

$$I_{o4} = 100\mu A \left(\frac{40/1}{5/1} \right) = 800 \mu A \quad | \quad I_{o5} = 100\mu A \left(\frac{2.5/1}{5/1} \right) = 50 \mu A$$

$$I_{o2} = 200\mu A \frac{1+0.02(10)}{1+0.02(2)} = 231 \mu A \quad | \quad I_{o3} = 400\mu A \frac{1+0.02(5)}{1+0.02(2)} = 423 \mu A$$

$$I_{o4} = 800\mu A \frac{1+0.02(12)}{1+0.02(2)} = 954 \mu A \quad | \quad I_{o5} = 50\mu A \frac{1+0.02(8)}{1+0.02(2)} = 55.8 \mu A$$

$$I_{o2} = 10\mu A \frac{1}{1 + \frac{17}{50}} = 7.46 \mu A \quad | \quad I_{o3} = 5(7.46\mu A) = 37.3 \mu A \quad | \quad I_{o4} = 10(7.46\mu A) = 74.6 \mu A$$

$$I_{o2} = 10\mu A \frac{1 + \frac{10}{50}}{1 + \frac{0.7}{50} + \frac{17}{50}} = 8.86 \mu A \quad | \quad I_{o3} = 50\mu A \frac{1 + \frac{10}{50}}{1 + \frac{0.7}{50} + \frac{17}{50}} = 44.3 \mu A$$

$$I_{o4} = 100\mu A \frac{1 + \frac{10}{50}}{1 + \frac{0.7}{50} + \frac{17}{50}} = 88.6 \mu A$$

Page 957

$$MR = \frac{10}{1 + \frac{11}{50(51)}} = 9.957 \quad | \quad FE = \frac{10 - 9.957}{10} = 4.3 \times 10^{-3} \quad | \quad V_{CE2} = V_{BE1} + V_{BE3} = 1.4 V$$

Page 958

MOS

$$I_{O_2} = 200\mu A \frac{1 + 0.02(10)}{1 + 0.02(2)} = 231 \mu A \quad | \quad R_{out2} = \frac{50V + 10V}{231\mu A} = 260 k\Omega$$

$$I_{O_3} = 400\mu A \frac{1 + 0.02(5)}{1 + 0.02(2)} = 423 \mu A \quad | \quad R_{out3} = \frac{50V + 5V}{423\mu A} = 130 k\Omega$$

BJT

$$I_{O_2} = 10\mu A \frac{1 + \frac{10}{50}}{1 + \frac{0.7}{50} + \frac{17}{100}} = 10.1 \mu A \quad | \quad R_{out2} = \frac{50V + 10V}{10.1\mu A} = 5.94 M\Omega$$

$$I_{O_3} = 50\mu A \frac{1 + \frac{10}{50}}{1 + \frac{0.7}{50} + \frac{17}{100}} = 50.7 \mu A \quad | \quad R_{out3} = \frac{50V + 10V}{50.7\mu A} = 1.19 M\Omega$$

Page 959

$$I_{C1} = 100\mu A \frac{1 + \frac{0.7V}{50V}}{1 + \frac{0.7V}{50V} + \frac{6}{50V}} = 89.4\mu A \quad | \quad I_{C2} = 500\mu A \frac{1 + \frac{10V}{50V}}{1 + \frac{0.7V}{50V} + \frac{6}{50V}} = 529\mu A$$

$$R_{in} \cong \frac{1}{g_{m1}} = \frac{1}{40(89.4\mu A)} = 280 \Omega \quad | \quad n = \frac{529\mu A}{89.4\mu A} = 5.92 \quad | \quad R_{out} = \frac{50V + 10V}{529\mu A} = 113 k\Omega$$

Page 960

$$V_{DS1} = V_{GS1} = 0.75V + \sqrt{\frac{2(100\mu A)}{1mA/V^2}} = 1.20 V \quad | \quad I_{D2} = 100\mu A \frac{1 + \frac{10V}{50V}}{1 + \frac{1.2}{50V}} = 117 \mu A$$

$$R_{in} \cong \frac{1}{g_{m1}} = \frac{1}{\sqrt{2(10^{-3})(10^{-4})}} = 2.24 k\Omega \quad | \quad n = \frac{117\mu A}{100\mu A} = 1.17 \quad | \quad R_{out} = \frac{50V + 10V}{117\mu A} = 513 k\Omega$$

Page 961

$$R = \frac{V_T}{I_O} \ln\left(\frac{I_{REF}}{I_O} \frac{A_{E2}}{A_{E1}}\right) = \frac{0.025V}{25\mu A} \ln\left(\frac{100\mu A}{25\mu A} 5\right) = 3000 \Omega$$

$$K = 1 + \ln\left(\frac{100\mu A}{25\mu A} 5\right) = 4.00 \quad | \quad R_{out} = 4\left(\frac{75V}{25\mu A}\right) = 12.0 M\Omega$$

Page 962

$$I_O = \frac{V_T}{R} \ln\left(\frac{I_{REF}}{I_O} \frac{A_{E2}}{A_{E1}}\right) \quad | \quad I_O = \frac{0.025V}{100\Omega} \ln\left(\frac{1000\mu A}{I_O}\right) \rightarrow I_O = 300.54 \mu A$$

$$K = 1 + \ln\left(\frac{100\mu A}{300.54\mu A} 10\right) = 2.202 \quad | \quad R_{out} = 2.202\left(\frac{75V}{300.54\mu A}\right) = 550 k\Omega$$

Page 963

$$I_O = \frac{1}{R} \sqrt{\frac{2I_{REF}}{K_{nl}}} \left(1 - \sqrt{\frac{I_O}{I_{REF}} \frac{(W/L)_1}{(W/L)_2}} \right) \quad | \quad I_O = \frac{1}{2k\Omega} \sqrt{\frac{2(200\mu A)}{25\mu A/V^2}} \left(1 - \sqrt{\frac{I_O}{200\mu A} \frac{1}{10}} \right)$$

$$I_O = 2.00mA \left(1 - \sqrt{\frac{I_O}{2.00mA}} \right) \rightarrow I_O = 764 \mu A$$

$$R_{out} = \frac{50V + 10V}{764\mu A} \left(1 + 2000 \sqrt{2(2.5 \times 10^{-4})(7.64 \times 10^{-4})} \right) = 176 k\Omega$$

Page 964

$$I_{D1} = I_{REF} = I_{DO} \exp\left(\frac{V_{GS} - V_{TN}}{nV_T}\right) \quad | \quad I_{D2} = 55I_{DO} \exp\left(\frac{V_{GS} - V_{TN} - I_{D2}R}{nV_T}\right) \quad | \quad I_{D2} = I_{D1}$$

$$\frac{I_{D2}}{I_{D1}} = \frac{55I_{DO} \exp\left(\frac{V_{GS} - V_{TN} - I_{D2}R}{nV_T}\right)}{I_{DO} \exp\left(\frac{V_{GS} - V_{TN}}{nV_T}\right)} \quad | \quad \frac{55I_{DO} \exp\left(\frac{V_{GS} - V_{TN} - I_{D2}R}{nV_T}\right)}{I_{DO} \exp\left(\frac{V_{GS} - V_{TN}}{nV_T}\right)} = 1$$

$$55 = \frac{\exp\left(\frac{V_{GS} - V_{TN}}{nV_T}\right)}{\exp\left(\frac{V_{GS} - V_{TN} - I_{D2}R}{nV_T}\right)} = \exp\left(\frac{I_{D2}R}{nV_T}\right)$$

$$I_{D2} = \frac{nV_T}{R} \ln(55) = \frac{1.4V_T}{10^7} \ln(55) = 5.610 \times 10^{-7} V_T$$

$$V_T = \frac{kT}{q} = \frac{1.381 \times 10^{-23}(300)}{1.602 \times 10^{-19}} = 25.86 mV \rightarrow I_{D2} = 14.5 nA$$

$$V_T = \frac{kT}{q} = \frac{1.381 \times 10^{-23}(350)}{1.602 \times 10^{-19}} = 30.17 mV \rightarrow I_{D2} = 16.9 nA$$

$$V_T = \frac{kT}{q} = \frac{1.381 \times 10^{-23}(400)}{1.602 \times 10^{-19}} = 34.48 mV \rightarrow I_{D2} = 19.3 nA$$

Page 967

$$R_{out} \cong \frac{\beta_o r_o}{2} = \frac{150}{2} \left(\frac{50V + 15V}{50\mu A} \right) = 97.5 \text{ } M\Omega \quad | \quad R_{out} = r_o = \frac{50V + 15V}{50\mu A} = 1.30 \text{ } M\Omega$$

$$\text{SPICE: } r_o = 1.27 \text{ } M\Omega \quad | \quad R_{out} = 115.8 \text{ } M\Omega$$

$$\beta = 150 \left(1 + \frac{V_{CB}}{50} \right) = 150 \left(1 + \frac{14.3}{50} \right) = 193 \rightarrow R_{out} \cong 1.27 M\Omega \left(\frac{193}{2} \right) = 123 \text{ } M\Omega$$

Page 969

$$V_{DS2} = V_{GS2} = 0.8V + \sqrt{\frac{2(5 \times 10^{-5})}{2.5 \times 10^{-4}}} = 1.43 \text{ } V \quad | \quad V_{DS4} = 15 - 1.43 = 13.6 \text{ } V$$

$$R_{out} \cong \mu_{f4} r_{o2} = \sqrt{2(2.5 \times 10^{-4})(5 \times 10^{-5})[1 + 0.015(13.6)]} \left(\frac{\frac{1}{0.015}V + 13.6V}{50\mu A} \right) \left(\frac{\frac{1}{0.015}V + 1.43V}{50\mu A} \right) = 379 \text{ } M\Omega$$

$$R_{out} = r_o = \frac{66.7V + 15V}{50\mu A} = 1.63 \text{ } M\Omega$$

$$R_{out} \cong \frac{\beta_o r_o}{2} = \frac{100}{2} \left(\frac{67V + 14.3V}{50\mu A} \right) = 81.3 \text{ } M\Omega \quad | \quad R_{out} = r_o = \frac{67V + 15V}{50\mu A} = 1.64 \text{ } M\Omega$$

Page 973

$$I_O = 25.014\mu A + \frac{10V - 20V}{1.66G\Omega} = 25.008 \text{ } \mu A$$

$$V_{DS4} \geq V_{GS4} - V_{TN} = 0.2 \text{ } V \quad | \quad V_{D4} \geq V_{S4} + 0.2V \quad | \quad V_{D4} \geq 0.95 + 0.2 = 1.15 \text{ } V$$

$$I_O = 50\mu A \pm 0.1\% \quad | \quad \Delta I_O \leq 50 \text{ } nA \quad | \quad R_{out} \geq \frac{20V}{50nA} = 400 \text{ } M\Omega \quad | \quad \text{Choose } R_{out} = 1 \text{ } G\Omega.$$

$$r_o \cong \frac{50V}{50\mu A} = 1 \text{ } M\Omega \rightarrow \mu_f = 1000 \quad | \quad \mu_f \cong \frac{1}{\lambda} \sqrt{\frac{2K_n}{I_D}} \quad | \quad K_n = \left[\frac{0.01}{V} (1000) \right]^2 \frac{50\mu A}{2} = 2.5 \frac{mA}{V^2}$$

$$(W/L)_2 = (W/L)_4 = \frac{2.5 \times 10^{-3}}{5 \times 10^{-5}} = \frac{50}{1} \quad | \quad (W/L)_3 = (W/L)_1 = \frac{1}{2} \left(\frac{50}{1} \right) = \frac{25}{1}$$

Page 974

$$I_{REF} = \frac{5V - 0.7V}{43k\Omega} = 100 \mu A \quad | \quad I_{REF} = \frac{7.5V - 0.7V}{43k\Omega} = 158 \mu A$$

Since the transistors have the same parameters, $V_{GS1} = \frac{V_{DD} - (-V_{SS})}{3}$

$$I_{D2} = I_{D1} = \frac{4x10^{-4}}{2} (1.667 - 1)^2 = 89.0 \mu A \quad | \quad I_{D2} = I_{D1} = \frac{4x10^{-4}}{2} (2.5 - 1)^2 = 450 \mu A$$

$$I_O \cong \frac{0.025V}{6.8k\Omega} \ln \frac{5 - 1.4}{10^{-16}(39k\Omega)} = 101 \mu A \quad | \quad I_O \cong \frac{0.025V}{6.8k\Omega} \ln \frac{7.5 - 1.4}{10^{-16}(39k\Omega)} = 103 \mu A$$

$$S_{V_{EE}}^{IO} = \frac{V_{EE}}{I_O} \frac{\partial I_O}{\partial V_{EE}} = \frac{5V}{101\mu A} \frac{2\mu A}{2.5V} = 0.040$$

Page 975

$$I_O = \frac{V_T}{R} \ln \left(\frac{I_{C1} A_{E2}}{I_{C2} A_{E1}} \right) \quad | \quad I_O = \frac{0.025V}{1000\Omega} \ln [10(10)] = 115 \mu A$$

Assume that the collector-base junctions of Q₂ and Q₃ can never be forward biased
 $V_{CC} + V_{EE} \geq V_{EB3} + V_{BC3} + V_{BE1} = 0.6V + 0 + 0.6V = 1.2 V$

Similarly: $V_{CC} + V_{EE} \geq V_{EB4} + V_{CB2} + V_{BE1} = 0.6V + 0 + 0.6V = 1.2 V$

However, we know that we can actually forward-bias those junctions by 0.3 V or so and not effect the transistor behavior by much. In that case, the minimum bias would drop to 0.9 V.

$$T = 300 K \quad \& \quad TCR = -2000 \text{ ppm}/^\circ C$$

$$TC = \frac{1}{I} \frac{\partial I}{\partial T} = \frac{1}{T} - \frac{1}{R} \frac{\partial R}{\partial T}$$

$$(a) TC = \frac{1}{T} = \frac{1}{300K} = 3300 \text{ ppm}/^\circ K = 3300 \text{ ppm}/^\circ C$$

$$(b) TC = 3300 \text{ ppm}/^\circ C - (-2000 \text{ ppm}/^\circ C) = 5300 \text{ ppm}/^\circ C$$

Page 977

$$R = \sqrt{\frac{2}{5(25x10^{-6})(10^{-4})}} \left(1 - \sqrt{\frac{5}{50}} \right) = 8.65 k\Omega$$

Page 978

$$R = \frac{V_T}{I_O} \ln\left(\frac{I_{C1}}{I_{C2}} \frac{A_{E2}}{A_{E1}}\right) = \frac{0.025875V}{45\mu A} \ln\left(\frac{25}{5}\right) = 925 \Omega$$

$$A_{E1} = A \quad | \quad A_{E2} = 25A_{E1} = 25A \quad | \quad A_{E3} = A \quad | \quad A_{E4} = 5.58A_{E3} = 5.58A$$

Page 982

$$V_{PTAT} = V_T \ln\left(\frac{A_{E2}}{A_{E1}}\right) = (27.57mV) \ln(20) = 82.59 mV \quad | \quad R_i = \frac{V_{PTAT}}{I_E} = \frac{82.59mV}{25\mu A} = 3.30 k\Omega$$

$$V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right) = (27.57mV) \ln\left(\frac{25\mu A}{0.5fA}\right) = 0.6792 V$$

$$\frac{R_2}{R_i} = \frac{V_{GO} + 3V_T - V_{BE1}}{2V_{PTAT}} = \frac{1.12 + 3(0.02757) - 0.6792}{2(0.08259)} = 3.169 \quad | \quad R_2 = 3.169R_i = 10.5 k\Omega$$

$$V_{BG} = V_{BE1} + 2 \frac{R_2}{R_i} V_{PTAT} = 0.6792 + 2(3.169)(0.08259) = 1.203 V$$

The other resistors remain the same.

Page 985

$$I_{D3} = I_{D4} = I_{D1} = I_{D2} = \frac{250\mu A}{2} = 125 \mu A \quad | \quad V_{GS1} = 0.75V + \sqrt{\frac{2(125\mu A)}{250\mu A/V^2}} = 1.75 V$$

$$V_{GS3} = -0.75V - \sqrt{\frac{2(125\mu A)}{200\mu A/V^2}} = -1.87 V$$

$$V_{DS1} = V_{D1} - V_{S1} = (5 - 1.87) - (-1.75) = 4.88 V \quad | \quad V_{SD3} = V_{SG3} = 1.87 V$$

$$M_1 \text{ and } M_2 : (125 \mu A, 4.88 V) \quad | \quad M_3 \text{ and } M_4 : (125 \mu A, 1.87 V)$$

$$G_m = g_{m1} = \sqrt{2(2.5 \times 10^{-4})(1.25 \times 10^{-4})} = 250 \mu S$$

$$R_o = r_{o2} \| r_{o4} = \frac{75.2V + 4.88V}{125\mu A} \left\| \frac{75.2V + 1.87V}{125\mu A} \right. = 314 k\Omega \quad | \quad A_v = G_m R_o = 78.5$$

Page 986

$$CMRR \cong \mu_{f3} g_{m2} R_{SS} = \left(\frac{1}{\lambda} \sqrt{\frac{2K_{n3}}{I_{D3}}} \right) \left(\sqrt{2K_{n2}I_{D2}} \right) R_{SS} = \left(\frac{1}{\lambda} \sqrt{\frac{2K_{n3}}{I_{D3}}} \right) \left(\sqrt{2K_{n2}I_{D2}} \right) R_{SS}$$

$$K_{n3} = K_{n2} \quad | \quad I_{D2} = I_{D3} \quad | \quad CMRR = \frac{1}{0.0167} 2(0.005)10^7 = 5.99 \times 10^6 \quad \text{or} \quad 136 dB$$

Page 990

$V_{OS} = \frac{\Delta i}{g_m}$ where Δi is the difference in current on the two sides of the current mirror.

For the buffered current mirror, the error current is $\Delta i = 2 \frac{I_C}{\beta_{FO4}(\beta_{FO11}+1)}$

$$V_{OS} = \frac{\Delta i}{g_m} = \frac{2I_C}{\beta_{FO4}(\beta_{FO11}+1)} \left(\frac{V_T}{I_C} \right) = \frac{2V_T}{\beta_{FO4}(\beta_{FO11}+1)} = \frac{2(0.025V)}{80(81)} = 7.72 \mu V$$

Page 991

$$A_{v1} \cong \left(\beta_{o5} \frac{I_{C2}}{I_{C5}} \right) = \frac{150}{3} = 50$$

For the whole amplifier: $A_{dm} \cong A_{v1} A_{v2} A_{v3} \quad | \quad A_{v2} \cong \mu_{f5} \cong 40(75) = 3000 \quad | \quad A_{v3} \cong 1$

$A_{dm} \cong 50(3000)(1) = 150000 \quad | \quad$ Note that this assumes $R_L = \infty$.

Page 992

$$CMRR = \left[\frac{2}{\beta_{o3}} \left(\frac{1}{\beta_{o2}\mu_{f2}} - \frac{1}{2g_{m2}R_{EE}} \right) \right]^{-1} = \left[\frac{2}{100} \left(\frac{1}{100(40)(75)} - \frac{1}{2(40)(10^{-4})(10^7)} \right) \right]^{-1} = 5.45 \times 10^6 \rightarrow 135 \text{ dB}$$

Page 997 Note Twice: 14.7 V should be 14.3 V

$$A_{v2} \cong \frac{\mu_{f2}}{2} = \frac{40(60 + 14.3)}{2} \cong 1490 \quad | \quad A_{dm} = 5(1490)(1) = 7450 \quad | \quad r_{o5} = \frac{(60 + 14.3)}{2} \cong 149 \text{ k}\Omega$$

$$A_{dm} \cong A_{v1} A_{v2} A_{v3} \quad | \quad A_{v1} \cong \frac{I_{C2}}{I_{C5}} \beta_{o5} = \frac{I_{REF}}{2} \frac{\beta_{o5}}{5I_{REF}} = \frac{50}{10} = 5 \quad | \quad A_{v2} \cong \frac{\mu_{f5}}{2} \cong \frac{40(60 + 14.7)}{2} \cong 1500 \quad | \quad A_{v3} \cong 1$$

$A_{dm} \cong 5(1500)(1) = 7500$ assuming the input resistance of the emitter followers is much greater than

r_{o5} and $V_{A8} = V_{A5}$. Checking: $r_{o5} \cong \frac{60V + 14.7V}{500\mu A} = 149 \text{ k}\Omega \quad | \quad R_{iB6} \cong \beta_{o6} R_L = 300 \text{ M}\Omega$

$$I_{C5} = 10I_{C4} = 10I_{C3} \rightarrow A_{E5} = 10A \quad | \quad R_{id} = 2r_{\pi1} = 2 \frac{150}{40(50\mu A)} = 150 \text{ k}\Omega$$

Page 999

$$I_{REF} = \frac{22 + 22 - 1.4}{39k\Omega} = 1.09 \text{ mA} \quad | \quad I_1 = \frac{0.025V}{5k\Omega} \ln\left(\frac{1.09mA}{I_1}\right) \rightarrow I_1 = 20.0 \text{ } \mu\text{A}$$

$$I_2 = 0.75(1.09mA) \frac{1 + \frac{23.4V}{60V}}{1 + \frac{0.7V}{60V} + \frac{2}{50}} = 1.08 \text{ mA} \quad | \quad I_2 = 0.25(1.09mA) \frac{1 + \frac{21.3V}{60V}}{1 + \frac{0.7V}{60V} + \frac{2}{50}} = 351 \text{ } \mu\text{A}$$

$$R_o = r_{o21} \left[1 + \ln \frac{I_{C20}}{I_{C21}} \frac{A_{E20}}{A_{E21}} \right] = \frac{60V + 13.5V}{18.4\mu\text{A}} \left[1 + \ln \left(\frac{733\mu\text{A}}{18.4\mu\text{A}} \right) \right] = 18.7 \text{ M}\Omega$$

Page 1003

$$V_{CE6} = V_{CE5} + \frac{2V_{A6}}{\beta_{FO6}} = 0.7 + \frac{2(60V)}{100} = 1.90 \text{ V}$$

Page 1006

$$R_{th} = R_{out4} \parallel R_{out6} = 2r_{o4} \parallel 1.3r_{o6} = 2 \left(\frac{60 + 13}{7.25\mu\text{A}} \right) \parallel 1.3 \left(\frac{60 + 1.3}{7.16\mu\text{A}} \right) = 20.1 \text{ M}\Omega \parallel 11.1 \text{ M}\Omega = 7.15 \text{ M}\Omega$$

Page 1008

$$A_{v1} = -1.46 \times 10^{-4} (6.54 \text{ M}\Omega \parallel R_{in11}) = -1.46 \times 10^{-4} (6.54 \text{ M}\Omega \parallel 20.7 \text{ k}\Omega) = -3.01$$

Page 1010

$$R_{eq2} = r_{\pi15} + (\beta_{o15} + 1)R_L = \frac{50(0.025)}{2mA} + 51(2k\Omega) = 103 \text{ k}\Omega$$

$$R_{eq1} = r_{d14} + (r_{d13} + R_3) \parallel R_{eq2} = \frac{0.025V}{0.216mA} + \left[\frac{0.025V}{0.216mA} + 344k\Omega \right] \parallel 103k\Omega = 79.4 \text{ k}\Omega$$

$$R_{in12} = \frac{50(0.025V)}{0.216mA} + 51(79.4k\Omega) = 4.06 \text{ M}\Omega$$

$$R_{eq3} = (r_{d13} + R_3) \left\| \left(r_{d14} + \frac{r_{\pi12} + y_{22}^{-1}}{\beta_{o12} + 1} \right) \right\| = \left(\frac{0.025V}{0.216mA} + 344k\Omega \right) \left\| \left(\frac{0.025V}{0.216mA} + \frac{5.79k\Omega + 89.1k\Omega}{51} \right) \right\| = 1.97 \text{ k}\Omega$$

$$r_{\pi16} = 50 \frac{0.025}{2mA} = 625 \text{ }\Omega \quad | \quad R_{out} = \frac{625 + 1970}{51} + 27 = 78 \text{ }\Omega$$

$$I_{SC+} \cong \frac{0.7V}{27\Omega} = 25.9 \text{ mA} \quad | \quad I_{SC-} \cong -\frac{0.7V}{22\Omega} = -31.8 \text{ mA}$$

Page 1013

$$v_o = \left(\frac{R}{I_{EE}R_1R_3} \right) v_1 v_2 = K_M v_1 v_2 \quad | \quad K_M = \frac{|v_o|}{|v_1 v_2|} = \frac{5}{5^2} = 0.2 \quad | \quad K_M = \frac{|v_o|}{|v_1 v_2|} = \frac{1}{1^2} = 1$$

CHAPTER 15

Page 1034

$$I_{C4} = I_{C3} = I_{C2} = I_{C1} = \frac{I_1}{2} = 1 \text{ mA} \quad | \quad V_{CE2} = 0.7 \text{ V} \quad | \quad V_{EC3} = 0.7 \text{ V} \quad | \quad V_O = 0 \text{ V}$$

$$V_{EC4} = 5V - V_O = 5 - 0 = 5.0 \text{ V} \quad | \quad V_{EC1} = 5 - V_{C1} - V_{E1} = 5 - 0.7 - (-0.7) = 5.0 \text{ V}$$

$$(1 \text{ mA}, 5.0 \text{ V}), (1 \text{ mA}, 0.7 \text{ V}), (1 \text{ mA}, 0.7 \text{ V}), (1 \text{ mA}, 5.0 \text{ V})$$

Page 1036

With the output shorted, current cannot make it around the loop, so $T_{SC} = 0$.

$T_{OC} = 0$ is zero only if r_{o1} is neglected since the voltage across r_π must be zero for $i_b = 0$.

If we include r_{o1} , and start at the base of Q₂ assuming $r_{o1} \gg \frac{1}{g_{m3}}$ and a current mirror gain of 1:

$$v_{c4} \cong \frac{v_{e1}}{r_{o1}} (1) [r_{o4} \| R_{iB2} \| R_L \| r_{o4} (1 + g_{m2} r_{o1})] = \left(v_{b2} \frac{g_{m2} r_{o1}}{1 + g_{m2} r_{o1}} \right) \left(\frac{1}{r_{o1}} \right) [r_{o4} \| R_{iB2} \| R_L]$$

$$T_{OC} \cong \frac{r_{o4} \| R_{iB2} \| R_L}{r_{o1}} = \frac{55k\Omega \| 5.1k\Omega \| 10k\Omega}{55k\Omega} = 0.0579 \text{ - non-zero but small compared to 1.}$$

Evaluating Eq. 18.7 without R_L , $T_{OC} = g_{m2} (r_{o1} \| R_{iB2}) = 0.04 (55k\Omega \| 55k\Omega \| 5.1k\Omega) = 172$

Page 1042

$$T_{new} = \left[g_{m1} (R_3 \| r_{\pi2}) \right] \left[-g_{m2} \left([R_2 + R_1 \| R_{iE1}] \| R_S \| R_L \right) \right] \left(\frac{R_1 \| R_{iE1}}{R_1 \| R_{iE1} + R_2} \right)$$

$$T_{new} = T_{old} \frac{R_3 \| r_{\pi2}}{R_3 \| R_{iB2}} (1 + g_{m2} R_4) = -2.01 \frac{1k\Omega \| 2.5k\Omega}{970\Omega} \left[1 + 0.04S(300\Omega) \right] = -19.2$$

$$A_v = 10 \frac{19.2}{1 + 19.2} = 9.50 \quad | \quad \text{Now } R_{iC2} = r_{o2} = \infty \quad | \quad R_{in}^D \cong 31.7 \text{ k}\Omega \quad | \quad R_{out}^D \cong 1.74 \text{ k}\Omega$$

$$\text{Scaling using the previous result : } T_{SC} = -19.2 \left(\frac{1.86}{2.01} \right) = 17.8 \quad | \quad R_{in} = 31.7k\Omega \frac{1 + 17.8}{1 + 0} = 596k\Omega$$

$$R_{out} = 1.74k\Omega \frac{1 + 0}{1 + 19.2} = 86.1 \text{ }\Omega \quad | \quad \text{Removing } R_L : R'_{out} = \left[\frac{1}{86.1} - \frac{1}{10^4} \right]^{-1} = 86.8 \text{ }\Omega$$

Page 1044

$$R_x^D = R_x^D \frac{1+T_{SC}}{1+T_{OC}} \quad | \quad R_x^D = R_3 \| R_{iD1} \| R_{iG3} = R_3 \| 2r_{o1} \| R_{iG3} = 3k\Omega \| \infty \| \infty = 3k\Omega$$

$$T_{SC} = 0 \quad | \quad T_{OC} = T = 61.1 \quad | \quad R_x^D = 3k\Omega \left(\frac{1+0}{1+61.1} \right) = 48.3 \Omega$$

$$I_{D2} = I_{D1} = \frac{I_1}{2} = 0.500 \text{ mA} \quad | \quad I_{D4} = I_2 = 2.00 \text{ mA} \quad | \quad I_{D3} = \frac{1.63V - (-5V)}{13k\Omega} = 0.510 \text{ mA}$$

$$V_{DS1} = 3.5 + V_{GS1} \quad | \quad V_{GS1} = 1 + \sqrt{\frac{2(0.5mA)}{10mA}} = 1.32 \text{ V} \quad | \quad V_{DS1} = 3.5 + 1.32 = 4.82 \text{ V}$$

$$V_{DS2} = 5 + 1.32 = 6.32 \text{ V} \quad | \quad V_{DS3} = 5 - 1.63 = 3.37 \text{ V} \quad | \quad V_{DS4} = 5 - V_O = 5.00 \text{ V}$$

$$(0.5 \text{ mA}, 4.82 \text{ V}), (0.5 \text{ mA}, 6.32 \text{ V}), (0.51 \text{ mA}, 3.37 \text{ V}), (2 \text{ mA}, 5.0 \text{ V})$$

Page 1048

R_i appears in parallel with r_π : $r'_\pi = r_\pi \| R_i = 4.69k\Omega \| 10k\Omega = 3.19 \text{ k}\Omega$

$$T = g_m (R_C \| (R_F + r'_\pi) \| r_o) \left(\frac{r'_\pi}{r'_\pi + R_F} \right) = 0.032S (5k\Omega \| (50k\Omega + 3.19k\Omega) \| 62.4k\Omega) \left(\frac{3.19k\Omega}{3.19k\Omega + 50k\Omega} \right)$$

$$T = 8.17 \quad | \quad A_{tr} = A_{tr}^{Ideal} \frac{T}{1+T} = -50k\Omega \frac{8.17}{1+8.17} = -44.5 \text{ k}\Omega$$

$$R_{in}^D = r'_\pi \| (R_F + R_C \| r_o) = 3.19k\Omega \| (50k\Omega + 5k\Omega \| 62.4k\Omega) = 3.01 \text{ k}\Omega \quad | \quad T_{SC} = 0 \quad | \quad |T_{OC}| = |T|$$

$$R_{in} = 3.01k\Omega \frac{1+0}{1+8.17} = 328 \text{ }\Omega$$

$$R_{out}^D = R_C \| r_o \| (R_F + r'_\pi) = 5k\Omega \| 62.4k\Omega \| (50k\Omega + 3.19k\Omega) = 4.26 \text{ k}\Omega \quad | \quad T_{SC} = 0 \quad | \quad |T_{OC}| = |T|$$

$$R_{out} = 4.26k\Omega \frac{1+0}{1+8.17} = 463 \text{ }\Omega$$

Page 1049

$$A_v = -\left(\frac{R_F}{R_i + R_{in}}\right)\left(\frac{R_L}{R_{out} + R_L}\right) = -\left(\frac{45.1k\Omega}{2k\Omega + 340\Omega}\right)\left(\frac{10k\Omega}{336\Omega + 10k\Omega}\right) = -18.6$$

$$A_v = -\left(\frac{R_F}{R_i + R_{in}}\right)\left(\frac{R_L}{R_{out} + R_L}\right) = -\left(\frac{45.1k\Omega}{10k\Omega + 340\Omega}\right)\left(\frac{2k\Omega}{336\Omega + 2k\Omega}\right) = -3.73$$

$$T = \frac{-A_{tr}}{R_F + A_{tr}} = \frac{48.5k\Omega}{50k\Omega - 48.5k\Omega} = 32.3 \quad | \quad g_{m3} = \frac{1}{R_{out}} \left(\frac{1}{1+T} \right) = \frac{1}{12\Omega} \left(\frac{1}{1+32.3} \right) = 2.50 \text{ mS}$$

$$R_{in} = \left(R_F + \frac{1}{g_{m3}} \right) \left(\frac{1}{1+T} \right) = \left(50k\Omega + \frac{1}{2.5mS} \right) \left(\frac{1}{1+32.3} \right) = 1.51 \text{ k}\Omega$$

Page 1053

$$T \text{ is the same: } |T| = 306 \quad | \quad A_v^{Ideal} = 1 \quad | \quad A_v = A_{tr}^{Ideal} \frac{T}{1+T} = 1 \left(\frac{306}{1+306} \right) = 0.997$$

$$R_{out}^D = R_F \parallel \frac{1}{g_{m5}} = 10k\Omega \parallel \frac{1}{3.16mS} = 307 \text{ }\Omega \quad | \quad T_{SC} = 0 \quad | \quad |T_{OC}| = |T|$$

$$R_{out} = 307\Omega \frac{1+0}{1+306} = 1.00 \text{ }\Omega$$

Page 1054

$$T \text{ is the same: } |T| = 306 \quad | \quad A_v^{Ideal} = 1 \quad | \quad A_v = A_{tr}^{Ideal} \frac{T}{1+T} = 1 \left(\frac{306}{1+306} \right) = 0.997$$

$$R_{in}^D = r_{o1} \left(1 + g_{m1} \frac{2}{g_{m2}} \right) \left\| \frac{1}{g_{m3}} = 600k\Omega \parallel \frac{1}{2.00mS} = 500 \text{ }\Omega \quad | \quad |T_{OC}| = 306 \right.$$

Note: The impedance looking in the source of a transistor with a high resistance load of r_o is $2/g_m$ rather than $1/g_m$.

$$T_{SC} = -\frac{g_{m2}}{2} \left(2r_{o2} \| r_{o4} \right) \frac{g_{m5}R_F}{1+g_{m5}R_F} = -\frac{3.16mS}{2} (400k\Omega \| 200k\Omega) \frac{3.16mS(10k\Omega)}{1+3.16mS(10k\Omega)} = -204$$

$$R_{out} = 500\Omega \frac{1+204}{1+306} = 334 \text{ }\Omega$$

Page 1057

$$T \text{ is the same: } |T| = 152 \quad | \quad A_v^{ideal} = -\frac{R_2}{R_I} = -1 \quad | \quad A_v = A_{tr}^{ideal} \frac{T}{1+T} = -1 \left(\frac{152}{1+152} \right) = -0.993$$

$$R_{out}^D = (R_2 + R_I) \| R_1 \| \frac{1}{g_m} = 40k\Omega \| 10k\Omega \| \frac{1}{3.16mS} = 304 \Omega \quad | \quad T_{sc} = 0 \quad | \quad |T_{oc}| = |T| = 152$$

$$R_{out} = 304\Omega \frac{1+0}{1+152} = 1.99 \Omega$$

Page 1059

$$\text{There are approximately 15 cycles in } 0.8 \mu\text{sec: } f \cong \frac{15\text{cycles}}{0.8\mu\text{s}} = 18.8 \text{ MHz}$$

$$f_T = \frac{1}{2\pi} \frac{g_m}{C_{GS} + C_{GD}} \quad | \quad g_m = \sqrt{2K_n I_D} \quad | \quad f_{T2} = f_{T1} = \frac{1}{2\pi} \frac{\sqrt{2(0.01)(0.0005)}}{5pf + 1pF} = 83.9 \text{ MHz}$$

$$f_{T3} = \frac{1}{2\pi} \frac{\sqrt{2(0.004)(0.0005)}}{5pf + 1pF} = 53.1 \text{ MHz} \quad | \quad f_{T4} = \frac{1}{2\pi} \frac{\sqrt{2(0.01)(0.002)}}{5pf + 1pF} = 168 \text{ MHz}$$

Page 1069

$$G_m = g_{m2} = \sqrt{2(10^{-3})(5 \times 10^{-5})} = 0.316 mS \quad | \quad R_o = r_{o4} \| r_{o2} \cong \frac{1}{2\lambda I_D} = \frac{1}{2(0.02)5 \times 10^{-5}} = 500 \text{ k}\Omega$$

$$f_T = \frac{1}{2\pi} \left(\frac{G_m}{C_C} \right) = \frac{1}{2\pi} \left(\frac{0.316mS}{20\text{pF}} \right) = 2.51 \text{ MHz}$$

$$f_B = \frac{1}{2\pi} \left[\frac{1}{R_o C_C (1 + A_{v2})} \right] = \frac{1}{2\pi} \left[\frac{1}{R_o C_C (1 + \mu_{f2})} \right] \cong \frac{1}{2\pi} \left[\frac{1}{500k\Omega (20\text{pF}) \left[1 + \frac{1}{0.02} \sqrt{\frac{2(0.001)}{5 \times 10^{-4}}} \right]} \right] = 158 \text{ Hz}$$

Page 1070

$$f_z \cong \frac{1}{2\pi} \frac{g_{m5}}{C_C} = \frac{1}{2\pi} \frac{\sqrt{2(0.001)5 \times 10^{-4}}}{20 \times 10^{-12}} = 7.96 \text{ MHz} \quad | \quad R = \frac{1}{g_{m5}} = \frac{1}{\sqrt{2(0.001)5 \times 10^{-4}}} = 1.00 \text{ k}\Omega$$

$$G_m = g_{m2} = 40(5 \times 10^{-5}) = 2.00 \text{ mS} \quad | \quad R_o = r_{\pi 5} \cong \frac{100V}{40(5.5 \times 10^{-4} A)} = 4.54 \text{ k}\Omega$$

$$f_T = \frac{1}{2\pi} \left(\frac{G_m}{C_C} \right) = \frac{1}{2\pi} \left(\frac{2.00 \text{ mS}}{30 \text{ pF}} \right) = 10.6 \text{ MHz} \quad | \quad f_Z = \frac{1}{2\pi} \left(\frac{g_{m5}}{C_C} \right) = \frac{1}{2\pi} \left[\frac{40(5 \times 10^{-4})}{3 \times 10^{-11}} \right] = 106 \text{ MHz}$$

$$f_B = \frac{1}{2\pi} \left[\frac{1}{r_{\pi 5} C_C (1 + \mu_{f2})} \right] \cong \frac{1}{2\pi} \left[\frac{1}{4.54 \text{ k}\Omega (30 \text{ pF}) [1 + 40(50)]} \right] = 584 \text{ Hz}$$

Page 1073

$$SR = \frac{100 \mu A}{20 \text{ pF}} = 5.00 \times 10^6 \frac{V}{s} = 5.00 \frac{V}{\mu s}$$

$$SR = \frac{100 \mu A}{20 \text{ pF}} = 5.00 \times 10^6 \frac{V}{s} = 5.00 \frac{V}{\mu s}$$

Page 1077

$$G_m = g_{m2} = 40(2.5 \times 10^{-4}) = 10.0 \text{ mS} \quad | \quad f_T = \frac{1}{2\pi} \left(\frac{G_m / 2}{C_C + C_{\mu 3}} \right) = \frac{1}{4\pi} \left(\frac{10.0 \text{ mS}}{50.8 \text{ pF}} \right) = 15.7 \text{ MHz}$$

$$\phi_M = 90 - \tan^{-1} \left(\frac{15.7 \text{ MHz}}{142 \text{ MHz}} \right) + \tan^{-1} \left(\frac{15.7 \text{ MHz}}{173 \text{ MHz}} \right) + \tan^{-1} \left(\frac{15.7 \text{ MHz}}{192 \text{ MHz}} \right) + \tan^{-1} \left(\frac{15.7 \text{ MHz}}{206 \text{ MHz}} \right) = 69.5^\circ$$

Page 1081

$$SR \cong \frac{I_1}{C_C + C_{GD5}} = \frac{1mA}{65pF} = 15.4 \times 10^6 \frac{V}{s} = 15.4 \frac{V}{\mu s}$$

$$30^\circ = \tan^{-1}\left(\frac{f_T}{49.2MHz}\right) + \tan^{-1}\left(\frac{f_T}{82.1MHz}\right) + \tan^{-1}\left(\frac{f_T}{100MHz}\right) \rightarrow f_T = 16.6 MHz$$

$$C_C = 65pF \left(\frac{8.5MHz}{16.6MHz} \right) - 2pF = 31.3 pF$$

$$(a) I_{D5} = I_{D4} = 500 \mu A \quad | \quad I_{D6} = 1 mA \quad | \quad \text{Current error } \Delta I = 500 \mu A \quad | \quad g_m \propto \sqrt{W/L}$$

$$V_{os} = \frac{\Delta I}{G_{m12}} = \frac{\Delta I}{A_{v1}g_{m5}} = \frac{500 \mu A}{-192 \left(\frac{-4.33mS}{\sqrt{2}} \right)} = +0.85 mV$$

$$(b) I_{D5} = 3I_{D4} = 1.500 \mu A \quad | \quad I_{D6} = 1 mA \quad | \quad \text{Current error } \Delta I = -500 \mu A \quad | \quad g_m \propto \sqrt{W/L}$$

$$V_{os} = \frac{\Delta I}{G_{m12}} = \frac{\Delta I}{A_{v1}g_{m5}} = \frac{-500 \mu A}{-192 \left(-4.33mS \sqrt{1.5} \right)} = -0.49 mV$$

Page 1085

For the Hartley circuit in Fig. 18.34(a), $Z_{gs} = j\omega L_2$ and $Z_s = j\omega L_1$

$$Z_{in} = j\omega L_2 [1 + g_m(j\omega L_1)] + j\omega L_1 = j\omega(L_1 + L_2) - \omega^2 g_m L_1 L_2$$

$$\text{Re}(Z_{in}) = -\omega^2 g_m L_1 L_2$$

Page 1086

When the circuit is drawn symmetrically, capacitor $2C_{GD}$ is replaced with 2 capacitors of value $4C_{GD}$ in series. The circuit can then be cut vertically down the middle to form a differential mode half-circuit. The total capacitance at the drain end of inductor L is $C_{EQ} = C + C_{GS} + 4C_{GD}$.

Page 1089

$$f_p = \frac{1}{2\pi \sqrt{31.8mH \left[\frac{31.8fF(7pF)}{7.0318pF} \right]}} = 5.016 MHz \quad | \quad f_p = \frac{1}{2\pi \sqrt{31.8mH \left[\frac{31.8fF(25pF)}{25.0318pF} \right]}} = 5.008 MHz$$

Page 1091

Three cascaded inverting amplifiers assuming a normal rolloff: $3\phi = -360^\circ$ | $\phi = -120^\circ$
