

# MICROELECTRONIC CIRCUIT DESIGN

## Fifth Edition

**Richard C. Jaeger and Travis N. Blalock**

**Answers to Selected Problems – Updated 07/05/15**

### Chapter 1

**1.5** 1.52 years, 5.06 years

**1.6** 1.95 years, 6.52 years

**1.9** 402 MW, 1.83 MA

**1.11** 19.53 mV/bit,  $10011101_2$

**1.13** 2.441 mV, 5.00 V, 5.724 V

**1.15** 11 bits, 20 bits

**1.17**  $0.0075 \text{ A}$ ,  $0.003 \cos(1000t) \text{ A}$

**1.20**  $v_{DS} = [5 + 2 \sin(2500t) + 4 \sin(1000t)] \text{ V}$

**1.22** 6.12 V, 1.88 V, 78.4  $\mu\text{A}$ , 125  $\mu\text{A}$

**1.23** 100  $\mu\text{A}$ , 100  $\mu\text{A}$ , 8.2 V

**1.25**  $39.8 \Omega$ ,  $v_i$

**1.28** (a)  $75 \text{ k}\Omega$ , 89.6  $v_i$

**1.30**  $2 \text{ M}\Omega$ ,  $1.00 \times 10^8 i_i$

**1.31** (c)  $4 \text{ k}\Omega$

**1.38**  $50/-12^\circ$ ,  $10/-45^\circ$

**1.40**  $-82.4 \sin 750\pi t \text{ mV}$ ,  $11.0 \sin 750\pi t \mu\text{A}$

**1.42**  $1 + R_2/R_1$

**1.44** -1.875 V, -2.500 V

**1.46** Band-pass amplifier

**1.48**  $50.0 \sin(2000\pi t) + 30.0 \cos(8000\pi t) \text{ V}$

**1.50** 0 V

**1.52**  $[4653 \Omega, 4747 \Omega]$ ,  $[4465 \Omega, 4935 \Omega]$ ,  $[4230 \Omega, 5170 \Omega]$

**1.57**  $6200 \Omega$ ,  $4.96 \Omega/\text{ }^\circ\text{C}$

**1.64** 3.29, 0.995, -6.16; 3.295, 0.9952, -6.155

## Chapter 2

**2.3** 500 mA

**2.4** 144  $\Omega$ , 287  $\Omega$

**2.6** 305.2 K

**2.7** For Ge :  $2.63 \times 10^{-4} / cm^3$ ,  $2.27 \times 10^{13} / cm^3$ ,  $8.04 \times 10^{15} / cm^3$ ,

**2.10**  $-1.75 \times 10^6 cm/s$ ,  $+6.25 \times 10^5 cm/s$ ,  $2.80 \times 10^4 A/cm^2$ ,  $1.00 \times 10^{-10} A/cm^2$

**2.11** 1.60 MA/cm<sup>2</sup>, 160 pA/cm<sup>2</sup>

**2.12** 4 MA/cm<sup>2</sup>

**2.16** 316.6 K

**2.21** Donor, acceptor

**2.22** 100 V/cm

**2.23** 1800 atoms

**2.24** p-type,  $7 \times 10^{18}/cm^3$ ,  $14.3/cm^3$ ,  $5.28 \times 10^9/cm^3$ ,  $7.54 \times 10^{-10}/cm^3$

**2.27**  $4 \times 10^{17}/cm^3$ ,  $250/cm^3$

**2.29**  $4 \times 10^{16}/cm^3$ ,  $2.50 \times 10^5/cm^3$

**2.31**  $40/cm^3$ ,  $2.5 \times 10^{18}/cm^3$ ,  $187 cm^2/s$ ,  $58.7 cm^2/s$ , p-type,  $42.5 m\Omega\text{-cm}$

**2.33**  $10^4/cm^3$ ,  $10^{16}/cm^3$ ,  $727 cm^2/s$ ,  $153 cm^2/s$ , p-type,  $4.08 \Omega\text{-cm}$

**2.35**  $1.25 \times 10^{19}/cm^3$

**2.38**  $5.66 M\Omega\text{-cm}$

**2.39**  $9.67 \times 10^{19}/cm^3$ ,  $1.37 \times 10^{20}/cm^3$

**2.42**  $1.89/\Omega\text{-cm}$ ,  $3.30 \times 10^{17}/cm^3$

**2.43** 75K: 6.64 mV, 150K: 12.9 mV, 300K: 25.8 mV, 400K: 34.5 mV

**2.44** -56.1 kA/cm<sup>2</sup>

**2.45**  $1.20 \times 10^5 \exp(-5000 x/cm) A/cm^2$ , 12.0 mA

**2.49** 1.108  $\mu m$

**2.52** 8 atoms,  $1.60 \times 10^{-22} cm^3$ ,  $5.00 \times 10^{22} atoms/cm^3$ ,  $3.73 \times 10^{-23} g$ ,  $1.66 \times 10^{-24} g/proton$

## Chapter 3

- 3.1**  $0.0373 \mu\text{m}$ ,  $0.0339 \mu\text{m}$ ,  $3.39 \times 10^{-3} \mu\text{m}$ ,  $0.979 \text{ V}$ ,  $5.24 \times 10^5 \text{ V/cm}$
- 3.4**  $10^{18}/\text{cm}^3$ ,  $10^2/\text{cm}^3$ ,  $10^{18}/\text{cm}^3$ ,  $10^2/\text{cm}^3$ ,  $0.921 \text{ V}$ ,  $0.0488 \mu\text{m}$
- 3.6**  $6.80 \text{ V}$ ,  $1.22 \mu\text{m}$
- 3.9** (b)  $640 \text{ kA/cm}^2$
- 3.11**  $7.50 \times 10^{20}/\text{cm}^4$
- 3.15** (a)  $290 \text{ K}$
- 3.17**  $339.2 \text{ K}$
- 3.19**  $1.34$ ,  $3.21 \text{ pA}$
- 3.20**  $0.776 \text{ V}$ ;  $0.707 \text{ V}$ ;  $0 \text{ A}$ ;  $9.39 \text{ aA}$ ,  $-10.0 \text{ aA}$
- 3.23**  $1.34 \text{ V}$ ;  $1.38 \text{ V}$
- 3.26**  $[0.535 \text{ V}, 0.651 \text{ V}]$
- 3.27**  $327.97 \text{ K}$ ,  $290.05 \text{ K}$
- 3.31**  $0.573 \text{ V}$ ;  $0.528 \text{ V}$
- 3.32**  $-1.59 \text{ mV/K}$
- 3.35**  $0.691 \text{ V}$ ,  $0.950 \mu\text{m}$ ,  $3.74 \mu\text{m}$ ,  $11.5 \mu\text{m}$
- 3.37**  $1500 \text{ V}$
- 3.39**  $4 \text{ V}$ ,  $0 \Omega$
- 3.42**  $10.5 \text{ nF/cm}^2$ ;  $58.2 \text{ pF}$
- 3.43**  $1.00 \text{ pF}$ ,  $25 \text{ fC}$ ;  $12 \text{ pF}$ ,  $0.3 \text{ pC}$
- 3.46**  $9.87 \text{ MHz}$ ;  $15.5 \text{ MHz}$
- 3.47**  $0.495 \text{ V}$ ,  $0.668 \text{ V}$
- 3.49**  $0.708 \text{ V}$ ,  $0.718 \text{ V}$ ;  $0.808 \text{ V}$
- 3.52** (a) Load line:  $(450 \mu\text{A}, 0.500 \text{ V})$ ; SPICE:  $(443 \mu\text{A}, 0.575 \text{ V})$   
(b) Load line:  $(-667 \mu\text{A}, -4 \text{ V})$ ;  
(c) Load line:  $(0 \mu\text{A}, -3 \text{ V})$ ;
- 3.55** (a)  $(1.4 \text{ mA}, 0.5 \text{ V})$ , (e)  $(-2.1 \text{ mA}, -4 \text{ V})$
- 3.62** Load line:  $(50 \mu\text{A}, 0.5 \text{ V})$ ; Mathematical model:  $(49.9 \mu\text{A}, 0.501 \text{ V})$ ; Ideal diode model:  $(100 \mu\text{A}, 0 \text{ V})$ ; CVD model:  $(40.0 \mu\text{A}, 0.6 \text{ V})$
- 3.66** (a)  $0.625 \text{ mA}$ ,  $-5 \text{ V}$ ;  $0.625 \text{ mA}$ ,  $+3 \text{ V}$ ;  $0 \text{ A}$ ,  $7 \text{ V}$ ;  $0 \text{ A}$ ,  $-5 \text{ V}$

- 3.70** (a-c) (270  $\mu$ A, 0 V), (409  $\mu$ A, 0 V); (b-c) (190  $\mu$ A 0.7 V), (345  $\mu$ A, 0.7 V)
- 3.71** (c) (0.861 mA, 0.650 V) (0 mA, -1.51 V) (0.951 mA, 0.650 V)  
(d) (0 A, -0.450 V) (0 A, -0.950 V) (1.16 mA, 0.650 V)
- 3.73** (1.50 mA, 0 V) (0 A, -5 V) (1.00 mA, 0 V)
- 3.76** (b)  $(I_Z, V_Z) = (127 \mu\text{A}, 6.00 \text{ V})$
- 3.78** (d) 12.6 mW
- 3.80** 1.25 W, 3.50 W
- 3.85** 17.1 V
- 3.89** -7.91 V, 1.05 F, 17.8 V, 3530 A, 840 A ( $\Delta T = 0.628 \text{ ms}$ )
- 3.91** (b) -7.91V, 904  $\mu$ F, 17.8 V, 3540 A, 839 A
- 3.92** 10.1 F, 8.6 V, 3.04 V, 1240 A, 16400 A
- 3.97** -11.7 V, 0.782 F, 25.5 V, 3750 A, 742 A
- 3.101** 5.05 F, 8.6 V, 6.08 V, 1240 A, 6280 A
- 3.107** 1330  $\mu$ F, 2500 V, 1770 V, 126 A, 1250 A
- 3.114** 5 mA, 4.4 mA, -3.6 mA, 6.39 ns
- 3.118** (0.969 A, 0.777 V); 0.753 W; 1 A, 0.864 V
- 3.121** 1.11  $\mu$ m - far infrared; 0.875  $\mu$ m - near infrared

## Chapter 4

- 4.3**  $10.5 \text{ nF/cm}^2$
- 4.4**  $43.2 \mu\text{A/V}^2$ ,  $86.4 \mu\text{A/V}^2$ ,  $173 \mu\text{A/V}^2$ ,  $346 \mu\text{A/V}^2$ , ,
- 4.8** (a)  $4.00 \text{ mA/V}^2$  (b)  $8.00 \text{ mA/V}^2$ ,  $15.00 \text{ mA/V}^2$
- 4.11**  $+840 \mu\text{A}$ ;  $-880 \mu\text{A}$
- 4.15**  $23.0 \Omega$ ;  $50.0 \Omega$
- 4.18**  $125 \mu\text{A/V}^2$ ;  $1.5 \text{ V}$ ; enhancement mode;  $1.25/1$
- 4.20**  $0 \text{ A}$ ,  $0 \text{ A}$ ,  $1.88 \text{ mA}$ ,  $7.50 \text{ mA}$ ,  $3.75 \text{ mA/V}^2$
- 4.22** (i)  $1.56 \text{ mA}$ , saturation region;  $460 \mu\text{A}$ , triode region;  $0 \text{ A}$ , cutoff
- 4.23** Saturation; cutoff; saturation; triode; triode; triode
- 4.27**  $6.50 \text{ mS}$ ,  $13.0 \text{ mS}$
- 4.31**  $2.59 \text{ mA}$ ;  $2.25 \text{ mA}$
- 4.34**  $9.03 \text{ mA}$ ,  $18.1 \text{ mA}$ ,  $11.3 \text{ mA}$
- 4.37**  $1.13 \text{ mA}$ ;  $1.29 \text{ mA}$
- 4.39** Triode region
- 4.40**  $99.5 \mu\text{A}$ ;  $199 \mu\text{A}$ ;  $99.5 \mu\text{A}$ ;  $199 \mu\text{A}$
- 4.44**  $0$ ;  $0$
- 4.45**  $5.17 \text{ V}$
- 4.50**  $40.0 \mu\text{A}$ ;  $72.0 \mu\text{A}$ ;  $4.41 \mu\text{A}$ ;  $32.8 \mu\text{A}$
- 4.53**  $581/1$ ;  $233/1$
- 4.55**  $235 \Omega$ ;  $235 \Omega$
- 4.56**  $0.629 \text{ A/V}^2$
- 4.57**  $400 \mu\text{A}$
- 4.60** The transistor must be a depletion-mode device and the symbol is not correct.
- 4.64** (a)  $6.91 \times 10^{-8} \text{ F/cm}^2$ ;  $1.73 \text{ fF}$
- 4.66**  $17.3 \text{ pF/cm}$
- 4.68**  $20.7 \text{ nF}$
- 4.70** (a)  $1.35 \text{ fF}$ ,  $0.20 \text{ ff}$ ,  $0.20 \text{ ff}$
- 4.73**  $50\text{U}$ ,  $0.5\text{U}$ ,  $2.5\text{U}$ ,  $1\text{V}$ ,  $0$
- 4.75** (a)  $10\text{U}$ ,  $0.5\text{U}$ ,  $1.25\text{U}$ ,  $-1\text{V}$ ,  $0$

- 4.76**  $432 \mu\text{A}/\text{V}^2$ ,  $1.94 \text{ mA}$ ;  $864 \mu\text{A}/\text{V}^2$ ,  $0.972 \text{ mA}$
- 4.79**  $6.37 \text{ GHz}$ ,  $2.55 \text{ Ghz}$ ;  $637 \text{ GHz}$ ,  $255 \text{ GHz}$
- 4.81** Velocity saturation; cutoff; velocity saturation; triode; triode; velocity saturation
- 4.86**  $22\lambda \times 12\lambda$ ;  $15.2\%$
- 4.89**  $12\lambda \times 12\lambda$ ;  $13.9\%$
- 4.92**  $(572 \mu\text{A}, 7.94 \text{ V})$ ;  $(688 \mu\text{A}, 7.52 \text{ V})$
- 4.94**  $(50.3 \mu\text{A}, 8.43 \text{ V})$ ;  $(54.1 \mu\text{A}, 8.16 \text{ V})$
- 4.101** (a)  $(55.5 \mu\text{A}, 6.40 \text{ V})$
- 4.104** One possibility:  $360 \text{ k}\Omega$ ,  $910 \text{ k}\Omega$ ,  $3 \text{ k}\Omega$ ,  $15 \text{ k}\Omega$ ,  $5/1$
- 4.106**  $(350 \mu\text{A}, 1.7 \text{ V})$ ; triode region
- 4.109**  $(390 \mu\text{A}, 4.1 \text{ V})$ ; saturation region
- 4.110**  $(361 \mu\text{A}, 9.59 \text{ V})$
- 4.112**  $430 \text{ k}\Omega$ ,  $1 \text{ M}\Omega$ ,  $1.5 \text{ k}\Omega$ ,  $3 \text{ k}\Omega$
- 4.114**  $(109 \mu\text{A}, 1.08 \text{ V})$ ;  $(33.5 \mu\text{A}, 0.933 \text{ V})$
- 4.117**  $3.0040 \times 10^{-5} \text{ A}$ ;  $2.8217 \times 10^{-5} \text{ A}$
- 4.120**  $(73.1 \mu\text{A}, 9.37 \text{ V})$
- 4.121**  $(69.7 \mu\text{A}, 9.49 \text{ V})$ ;  $(73.1 \mu\text{A}, 8.49 \text{ V})$
- 4.124**  $(8.22 \mu\text{A}, 7.04 \text{ V})$ ,  $(6.78 \mu\text{A}, 7.56 \text{ V})$ ;  $(8.40 \mu\text{A}, 6.98 \text{ V})$ ,  $(6.92 \mu\text{A}, 7.51 \text{ V})$
- 4.126**  $(93.1 \mu\text{A}, 8.65 \text{ V})$ ,  $(78.2 \mu\text{A}, 9.18 \text{ V})$ ;  $(98.9 \mu\text{A}, 8.44 \text{ V})$ ,  $(82.9 \mu\text{A}, 9.02 \text{ V})$
- 4.127**  $2.25 \text{ mA}$ ;  $16.0 \text{ mA}$ ;  $1.61 \text{ mA}$
- 4.128**  $(322 \mu\text{A}, 0.340 \text{ V})$ ,
- 4.131**  $18.1 \text{ mA}$ ;  $45.2 \text{ mA}$ ;  $13.0 \text{ mA}$
- 4.133**  $1/3.84$
- 4.134**  $(153 \mu\text{A}, -3.53 \text{ V})$ ;  $(195 \mu\text{A}, -0.347 \text{ V})$
- 4.136**  $14.4 \text{ mA}$ ;  $27.1 \text{ mA}$ ;  $10.4 \text{ mA}$
- 4.137**  $4.04 \text{ V}$ ,  $10.8 \text{ mA}$ ;  $43.2 \text{ mA}$ ;  $24.5 \text{ mA}$ ;  $98.0 \text{ mA}$
- 4.139**  $(1.13 \text{ mA}, 1.75 \text{ V})$
- 4.140**  $(63.5 \mu\text{A}, -5.48 \text{ V})$ ,  $R \leq 130 \text{ k}\Omega$
- 4.144**  $(125 \mu\text{A}, -1.54 \text{ V})$ ,  $(115 \mu\text{A}, -2.49 \text{ V})$
- 4.145**  $22.3 \text{ k}\Omega \rightarrow (127 \mu\text{A}, -5.50 \text{ V})$

**4.148** (a) One possible design:  $220\text{ k}\Omega$ ,  $200\text{ k}\Omega$ ,  $10\text{ k}\Omega$ ,  $10\text{ k}\Omega$

**4.149** (b)  $(260\text{ }\mu\text{A}, -12.4\text{ V})$

**4.150**  $(32.1\text{ }\mu\text{A}, -1.41\text{ V})$

**4.151**  $(36.1\text{ }\mu\text{A}, 80.6\text{ mV})$ ;  $(32.4\text{ }\mu\text{A}, -1.32\text{ V})$ ;  $(28.8\text{ }\mu\text{A}, -2.49\text{ V})$

**4.153**  $(431\text{ }\mu\text{A}, 6.47\text{ V})$

**4.154**  $2.5\text{ k}\Omega$ ,  $10\text{ k}\Omega$

**4.155** (b)  $I_D = 1.38\text{ mA}$ ,  $I_G = 0.62\text{ mA}$ ,  $V_S = -0.7\text{ V}$

**4.158**  $(76.4\text{ }\mu\text{A}, 7.69\text{ V})$ ,  $(76.4\text{ }\mu\text{A}, 6.55\text{ V})$ ,  $5.18\text{ V}$

**4.160** (a)  $(69.5\text{ }\mu\text{A}, 3.52\text{ V})$

**4.163**  $10.0\text{ V}$ ;  $10.0\text{ mA}$ ,  $501\text{ mA}$ ;  $13.8\text{ V}$

**4.165**  $15.0\text{ V}$ ;  $15.0\text{ mA}$ ,  $1.00\text{ A}$ ;  $12.2\text{ V}$

## Chapter 5

- 5.4** 0.167, 0.667, 3.00, 0.909, 49.0, 0.995, 0.999, 5000
- 5.5** 200 aA; 0.101 fA, -0.115 V
- 5.6** (d)  $V_{BE} = V_{BC}$  (e)  $I_E/I_C = -\beta_R/\beta_F$  (f) 0.374  $\mu$ A, -149.6  $\mu$ A, +150  $\mu$ A, 0.626 V
- 5.9** 4.04 fA
- 5.11** 1.45 mA; -1.45 mA
- 5.14** -25  $\mu$ A, -100  $\mu$ A, +75  $\mu$ A, 65.7, 1/3, 0, 0.611 V
- 5.17** 1.77  $\mu$ A, -33.2  $\mu$ A, +35  $\mu$ A, 0.663 V
- 5.20** (a) 868  $\mu$ A
- 5.24** 0.990, 0.333, 4.04 fA, 12.0 fA
- 5.26** 83.3, 87.5, 100
- 5.31** 39.6 mV/dec, 49.5 mV/dec, 59.4 mV/dec, 69.3 mV/dec
- 5.32** 5 V, 40 V, 5 V
- 5.33** 2.31 mA; 388  $\mu$ A; 0
- 5.34** 60.7 V
- 5.38** Cutoff
- 5.40** saturation, forward-active region, reverse-active region, cutoff
- 5.44** 50.0 aA, 2.67 aA, 52.7 aA
- 5.45**  $I_C = 81.4 \text{ pA}$ ,  $I_E = 81.4 \text{ pA}$ ,  $I_B = 4.28 \text{ pA}$ , forward-active region; although  $I_C$ ,  $I_E$ ,  $I_B$  are all very small, the Transport model still yields  $I_C \cong \beta_F I_B$
- 5.46** 79.0, 6.83 fA
- 5.47** 83.3, 1.73 fA
- 5.48** 55.3  $\mu$ A, 0.683  $\mu$ A, 54.6  $\mu$ A
- 5.49** 6.67 MHz; 500 MHz
- 5.51** 1.5, 31.1 aA
- 5.53** -19.9  $\mu$ A, 26.5  $\mu$ A, -46.4  $\mu$ A
- 5.56** 17.3 mV, 0.251 mV
- 5.58** 1.46 A, 9.57 A
- 5.60** 0.771 V, 0.683 V, 27.5 mV
- 5.63** 24.2  $\mu$ A
- 5.64** 4.0 fF; 0.4 pF; 40 pF

- 5.66** 0.388 pF at 1 mA
- 5.68** 750 MHz, 4.17 MHz
- 5.69** 0.149  $\mu\text{m}$
- 5.71** 61.7, 23.1 V
- 5.73** 73.5, 37.5 V
- 5.74** Fig. 5.14(a) 100  $\mu\text{A}$ , 4.52  $\mu\text{A}$ , 95.5  $\mu\text{A}$ , 0.647 V, 0.651 V
- 5.76** 26.3  $\mu\text{A}$
- 5.77** (c) 33.1 mS
- 5.80** (b) 38% reduction
- 5.82** (86.2  $\mu\text{A}$ , 2.92 V); (431  $\mu\text{A}$ , 2.92 V); (17.3  $\mu\text{A}$ , 2.92 V); (83.2  $\mu\text{A}$ , 3.13 V);
- 5.87** (23.4  $\mu\text{A}$ , 4.13 V)
- 5.90** 36 k $\Omega$ , 75 k $\Omega$ , 3.9 k $\Omega$ , 3 k $\Omega$ ; (0.975 mA, 5.24 V)
- 5.91** 12 k $\Omega$ , 20 k $\Omega$ , 2.4 k $\Omega$ , 1.2 k $\Omega$ ; (0.870 mA, 1.85 V)
- 5.94** (7.5 mA, 4.3 V)
- 5.97** 30 k $\Omega$ , 620 k $\Omega$ ; (24.2  $\mu\text{A}$ , 0.770 V)
- 5.98** 5.28 V
- 5.100** 3.21  $\Omega$
- 5.101** 10 V, 100 mA, 98.5 mA, 10.7 V
- 5.102** 10 V, 109 mA, 109 mA, 14.3 V

## Chapter 6

- 6.1** 10  $\mu\text{W}/\text{gate}$ , 8  $\mu\text{A}/\text{gate}$
- 6.3** 2.5 V, 0 V, 0 W, 62.5  $\mu\text{W}$ ; 3.3 V, 0 V, 0 V, 109  $\mu\text{W}$
- 6.5**  $V_{OL} = 0 \text{ V}$ ,  $V_{OH} = 2.5 \text{ V}$ ,  $V_{REF} = 0.8 \text{ V}$ ;  $Z = A$
- 6.7** 3 V, 0 V, 2 V, 1 V, -3
- 6.9** 2 V, 0 V, 2 V, 3.3 V, 1.3 V, 2 V
- 6.11** 3.3 V, 0 V, 3.0 V, 0.25 V, 1.8 V, 1.5 V, 1.2 V, 1.25 V
- 6.13** -0.80 V, -1.35 V
- 6.15** 1 ns
- 6.17** 0.250  $\mu\text{W}/\text{gate}$ , 37.5 aJ
- 6.19** 2.5  $\mu\text{W}/\text{gate}$ , 1.39  $\mu\text{A}/\text{gate}$ , 2.5 fJ
- 6.20** 2.20  $RC$ ; 2.20  $RC$
- 6.22** -0.78 V, -1.36 V; 9.5 ns, 9.5 ns; 4 ns, 4 ns; 4 ns
- 6.25**  $Z = 0\ 0\ 0\ 1\ 0\ 0\ 1\ 1$
- 6.27**  $Z = 0\ 1\ 0\ 1\ 0\ 1\ 0\ 1$
- 6.30** 2 ; 1
- 6.32** 80 A
- 6.33** 0.583 pF
- 6.36** 57.6 k $\Omega$ , 1.26/1
- 6.37** (b) 2.5 V, 5.48 mV, 15.6  $\mu\text{W}$
- 6.41** (a) 0.450 V, 1.57 V
- 6.44** (a) 0.521 V, 1.81 V
- 6.47** NM<sub>L</sub>: 0.242 V, 0.134 V, 0.351 V; NM<sub>H</sub>: 0.941 V, 0.508 V, 1.25 V
- 6.49** 34.1 k $\Omega$ ; 1.82/1; 1.49 V, 0.266 V
- 6.51** 81.8 k $\Omega$ , 1/1.15
- 6.52** 250  $\Omega$ ; 625  $\Omega$ ; a resistive channel exists connecting the source and drain; 20/1
- 6.53** 2.17 V
- 6.55** 1.44 V
- 6.58** 2.7 V, 0.20 V, 0.363 mW, 0.673 mW
- 6.59** (a) 2.5 V, 0.206 V, 0.434 mW

- 6.62** 1.75/1, 8.33/1
- 6.64** (b) 14.3/1, 1.70
- 6.66** 0.106 V
- 6.67** (b) 1.55 V, 0.20 V, 0.150 mW
- 6.69** -2.40 at  $v_O = 0.883$  V; -2.44 at  $v_O = 1.08$  V
- 6.71** 3.79 V
- 6.73** 3.3 V, 0.296 V, 1.25 mW
- 6.76** 1.75/1, 1/8.79
- 6.78** 2.5 V, 0.2 V, 0.12 mW
- 6.79** 1.014
- 6.80** 1.46/1, 1.72/1
- 6.83** -5.98 at  $v_O = 1.24$  V
- 6.85** (a) 0.165 V, 80  $\mu$ A (b) 0.860 V, 0.445 V
- 6.86** (a) 0.254 V, 100  $\mu$ A (b) 0.600 V, 0.481 V
- 6.87** 1.65/1, 1/2.32, 0.300 V, 0.426 V
- 6.89** 2.22/1, 1/3.30, 1.43/1
- 6.91** (b) 14.3/1, 1/1.33
- 6.93** 0.103 V, 84.8  $\mu$ A
- 6.94** 0.196 V
- 6.98** 4.71/1, 1/1.68, 50 mV
- 6.99** 6.66/1, 1.11/1, 0.203 V, 6.43/1, 6.74/1, 7.09/1
- 6.102**  $Y = \overline{(A+B)(C+D)E}$ , 6.66/1, 1.11/1
- 6.106**  $Y = \overline{ACE + ACDF + BF + BDE}$ , 3.33/1, 26.6/1, 17.8/1
- 6.110** 1/1.80, 3.33/1
- 6.112**  $Y = \overline{(C+E)[A(B+D)+G]+F}$ ; 5.43/1, 20.0/1, 6.66/1, 9.99/1
- 6.116** 64.9 mV
- 6.117** 1.81/1, 6.43/1, 7.09/1, 6.74/1
- 6.121** 5.43/1, 9.99/1, 6.66./1, 20.0/1
- 6.122** (a) 7.24/1, 26.6/1, 13.3/1
- 6.126**  $I_D^* = 2I_D$  |  $P_D^* = 2P_D$

**6.127** 1 ns

**6.128** 80 mW, 139 mW

**6.131** 60.2 ns, 16.6 MHz, a potentially stable state exists with no oscillation

**6.133** 31.7 ns, 4.39 ns, 5.86 ns

**6.135** 6.10 k $\Omega$ , 10.5/1

**6.138** (a) 68.4 ns, 3.55 ns, 9.18 ns

**6.140** 47.1 ns, 6.14 ns, 5.39 ns

**6.142** 2.11/1, 16.7/1, 12.8 ns, 0.923 ns

**6.143** 2.28/1, 2.80/1, 924  $\mu$ W

**6.144** (a) 1/1.68 (d) 1/5.89 (f) 1/1.60

**6.146** 0.33 ns, 1.7 ns, 0.69 ns, 13.6 ns

**6.149** -1.90 V, -0.156 V

**6.150** 1/3.30, 1.75/1

**6.151** 2.30 V, 1.07 V

**6.153**  $Y = \overline{A + B}$

## Chapter 7

- 7.1** 10 nm:  $173 \mu\text{A}/\text{V}^2$ ;  $69.1 \mu\text{A}/\text{V}^2$
- 7.3** 250 pA; 450 pA; 450 pA
- 7.6** 3.3 V, 0 V
- 7.8** cutoff, triode; triode, cutoff; saturation, cutoff
- 7.11** 1.25 V, 42.3  $\mu\text{A}$ ; 1.104 V, 25.3  $\mu\text{A}$
- 7.12** 0.90 V, 20.3  $\mu\text{A}$ ; 0.80 V, 12.3  $\mu\text{A}$
- 7.13** 1.104 V
- 7.14** (b) 2.5 V, 92.8 mV
- 7.16** 0.799 V
- 7.17** 1.16 V, 0.728 V
- 7.22** 0.984 V, 2.77 mA
- 7.23** 6.10/1, 1/5.37
- 7.24** (a) 1.90 ns, 1.90 ns, 0.947 ns
- 7.27** 7.90 ns, 3.16 ns, 2.77 ns
- 7.31** 2.11/1, 5.26/1
- 7.33** (a) 63.2/1, 158/1
- 7.36** 5.52/1
- 7.37** 5.76/1, 14.4/1
- 7.41** +0.25, +0.31
- 7.42** 2.1 ns, 2.48 ns, 1.3 ns, 1.0 ns,  $\langle C \rangle = 138 \text{ fF}$
- 7.44** 0.75 V: 1.09 ns, 1.96 ns, 1.96 ns; (b) 2.20/1, 5.49/1; 3.07/1, 7.68/1
- 7.48** 2.51/1, 6.27/1; 2.51/1, 12.5/1
- 7.50** 11.3/1, 84.6/1
- 7.51** 0.200  $\mu\text{W}/\text{gate}$ ; 55.6 A
- 7.52** 0.5  $\mu\text{W}/\text{gate}$ ; 0.46 fF; 0.80 fF; 1.54 fF
- 7.54** 5.00 W; 8.71 W
- 7.55** 211,000/1; 0.0106  $\text{cm}^2$
- 7.56** 2.00  $\mu\text{W}$ , 25.0 ns
- 7.59** 72.3  $\mu\text{A}$ ; 25.0  $\mu\text{A}$

- 7.61** 545 fJ, 340 MHz, 926  $\mu$ W
- 7.65**  $\alpha\Delta T$ ,  $\alpha^2 P$ ,  $\alpha^3 PDP$
- 7.68** SPICE: 47.2 ns, 30.3 ns, 30.3 ns, 26.5 ns; Propagation delay formulas: 7.5 ns, 17.3 ns
- 7.69** 1/3.75
- 7.70** 2/1, 20/1; 4/1, 40/1
- 7.74** 1.25/1
- 7.80** 3.95 ns, 3.95 ns, 11.8 ns
- 7.81** 4.67/1; 7.5/1
- 7.82** 5 transistors; The CMOS design requires 47% less area.
- 7.84**  $Y = \overline{(A+B)(C+D)E} = \overline{ACE + ADE + BDE + BCE}$ ; 12/1, 20/1, 10/1; 6/1; 30/1
- 7.86**  $Y = \overline{(A+B)}(\overline{C}+\overline{D})(\overline{E}+\overline{F}) = \overline{AB + CD + EF}$ ; 4/1, 15/1; 6/1; 10/1
- 7.88** 2/1, 4/1, 6/1, 15/1
- 7.91** (a) Path through NMOS A-D-E (c) Paths through PMOS A-C and B-E
- 7.93** 24/1, 20/1, 40/1
- 7.94** 6/1, 4/1, 10/1
- 7.101** 5.37 ns, 1.26 ns
- 7.103** 1.26 ns, 0.421 ns, 4.74 ns, 2.38 ns
- 7.105** 4.74 ns, 2.37 ns
- 7.107** 8; 2.90; 23.2  $A_o$
- 7.110**  $A_o \frac{\beta^N - 1}{\beta - 1}$
- 7.111** 263  $\Omega$ ; 658  $\Omega$
- 7.114** 240/1, 96.2/1
- 7.115** 1.41 V, 2.50 V
- 7.117** **1.16/1**
- 7.121** Latchup does not occur.

## Chapter 8

- 8.1** 1,048,576 bits, 4,294,967,296 bits; 2048 blocks
- 8.2** 3.73 pA/cell , 233 fA/cell
- 8.5** 3 V, 0.667  $\mu$ V
- 8.9** 1.55 V, 0 V, 3.59 V
- 8.11** “1” level is discharged by junction leakage current
- 8.13** 1.47 V, 1.43 V
- 8.14** –16.6 mV; 2.48 V
- 8.15** 0 V, 1.90; Junction leakage will destroy the “1” level
- 8.18** 3.30 V, 1.60 V; –1.58 V
- 8.22** 135  $\mu$ A, 346 mW
- 8.24** 0.266 V
- 8.25** 0.945 V (The sense amplifier provides a gain of 10.5.)
- 8.31** 0 V, 1.43 V, 3.00 V
- 8.32** 0.8 V, 1.2 V; 0.95 V, 0.95 V
- 8.34** 53,296
- 8.38**  $W_1 = 01000110_2$  ,  $W_3 = 00101011_2$

## Chapter 9

- 9.1** 0 V, -1.50 V; 6 k $\Omega$
- 9.2** 0 V, -0.700 V
- 9.3** (a) -1.38 V, -1.12
- 9.6** 0 V, -0.40 V; 3.39 k $\Omega$ ; Saturation, cutoff; Cutoff, saturation
- 9.8** -0.70 V, -1.30 V, -1.00 V, 0.60 V
- 9.11** -0.70 V, -1.50 V, -1.10 V, 2.67 k $\Omega$ , 41 k $\Omega$ ; 0.289 V; -0.10 V, +0.30 V
- 9.13** -1.70 V, -2.30 V, 0.60 V, Yes
- 9.15** Fig. P9.6: 1; In contrast, Fig. 9.6: 11
- 9.16** (a) 370  $\Omega$ , 400 k $\Omega$ , 2.34 k $\Omega$ , 8.40 k $\Omega$
- 9.18** -1.10 V, -1.50 V, -1.30 V, 0.400 V, 0.107 V, 1.10 mW
- 9.19** 0.383 V
- 9.21** -0.70 V, -1.50 V, -1.10 V, 11.3 k $\Omega$ , 2.67 k $\Omega$ , 2.38 k $\Omega$ ; 0.289 V
- 9.22** 0.413 V
- 9.25** 50.0  $\mu$ A, -2.30 V
- 9.26** Standard values: 11 k $\Omega$ , 150 k $\Omega$ , 136 k $\Omega$
- 9.29** +0.300 V, -0.535 V, 334  $\Omega$
- 9.31** 3.7 mA
- 9.33** (b) 0.135 mA
- 9.35** 10.7 mA
- 9.37** 400  $\Omega$ , 75.0 mA
- 9.39** (c) 0 V, -0.7 V, 3.93 mA (d) -3.7 V, 0.982 mA (e) 2920  $\Omega$
- 9.42** (b)  $Z = \overline{A} + \overline{B} = \overline{AB}$
- 9.44** -0.850 V; 3.59 pJ
- 9.46** 359 ns
- 9.47** 0 V, -0.600 V, 5.67 mW, 505  $\Omega$ , 600  $\Omega$ ;  $Y = A + B + C$ , 5 vs. 6
- 9.50** 5.00 k $\Omega$ , 5.40 k $\Omega$ , 31.6 k $\Omega$ , 113 k $\Omega$
- 9.51** 1 k $\Omega$ , 1 k $\Omega$ , 1.30 mW
- 9.53** 2.23 k $\Omega$ , 4.84 k $\Omega$ , 60.1 k $\Omega$
- 9.56** 1.45 V for  $V_{CB2} \geq 0$  V; 1.25 V for  $V_{CB2} \geq -0.2$  V

- 9.57** +0.60, - 0.56,  $314 \Omega$
- 9.60** 1.446 mA, 1.476 mA,  $29.66 \mu\text{A}$ ; 1.446 mA, 1.476 mA,  $29.52 \mu\text{A}$
- 9.62** -0.9 V, -1.1 V, -1.8 V, -2.0 V, -2.7 V, -2.9 V, -4.2 V
- 9.63**  $Y = AB + \overline{AC}$
- 9.68** 0, -0.8. 0, -0.8, 3.8 V
- 9.70** 2.98 pA, 70.5 fA
- 9.72** 160; 0.976; 0.976; 0.773 V
- 9.73** 0.691 V, 0.710 V
- 9.77**  $63.3 \mu\text{A}$ ,  $265 \mu\text{A}$
- 9.79** 40.2 mV, 0.617 mV
- 9.81** 234 mA; 34.9 mA
- 9.85** ( $I_B, I_C$ ): (a) (135  $\mu\text{A}$ , -169  $\mu\text{A}$ ); (515  $\mu\text{A}$ , 0); (169  $\mu\text{A}$ , 506  $\mu\text{A}$ ); (0, 0)  
(b) all 0 except  $I_{B1} = I_{E1} = 203 \mu\text{A}$
- 9.86** 13.5 mW, 7.60 mW
- 9.88** 1.85 V, 0.15 V;  $62.5 \mu\text{A}$ , - $650 \mu\text{A}$ ; 13
- 9.89** 2.5 V, 0.15 V, 0.66 V, 0.80 V, 0.51 V, 1.7 V
- 9.92** 180
- 9.93** 22
- 9.96**  $Y = \overline{ABC}$ ; 1.9 V; 0.15 V; 0, - $408 \mu\text{A}$
- 9.98** 1.5 V, 0.25 V; 0, -1.00 mA; 16
- 9.99** 0.7 V, 191  $\mu\text{A}$ , 59  $\mu\text{A}$ , 1.18 mA
- 9.100** -1.13 mA, 0, 4.50 mA, 0, 0; 0, 0, 0, 0, 1.23 mA, 0
- 9.102**  $Y = A + B + C$ ; 0 V, -0.8 V; -0.40 V
- 9.103** 1.05 mA,  $26.9 \mu\text{A}$
- 9.104** 2 fJ; 10 fJ
- 9.106** 1.67 ns; 0.5 mW
- 9.107** 2.8 ns; 140 mW

## Chapter 10

**10.2** (a) 41.6 dB, 35.6 dB, 94.0 dB, 100 dB, -0.915 dB

**10.4** 29.35

**10.5** Using MATLAB:

```
t = linspace(0,.004);
vs = sin(1000*pi*t)+0.333*sin(3000*pi*t)+0.200*sin(5000*pi*t);
vo= 2*sin(1000*pi*t+pi/6)+sin(3000*pi*t+pi/6)+sin(5000*pi*t+pi/6); plot(t,vs,t,vo)par
500 Hz: 1 0°, 1500 Hz: 0.333 0°, 2500 Hz: 0.200 0°; 2 30°, 1 30°, 1 30° 2 30°, 3 30°, 5
30°; yes
```

**10.7** 36.8 dB, 113 dB, 75.0 dB

**10.9** 22.0 dB, 90.0 dB, 56.0 dB;  $V_o = 12.7$  V, recommend  $\pm 15$ -V supplies

**10.11**  $3.01 \times 10^{-8}$  S,  $-6.62 \times 10^{-3}$ , 1.00, 66.2  $\Omega$

**10.13** 0.167 mS, -0.333, -2000, 4.08 M $\Omega$

**10.15** 1.000 mS, -1.000, 6001, 30.00 k $\Omega$

**10.16** 53.7 dB, 150 dB, 102 dB; 11.7 mV; 31.3 mW

**10.17** 45.3 mV, 1.00 W

**10.21** -5420

**10.23** 0,  $\infty$ , 80 mW,  $\infty$

**10.24** 196

**10.30** -10 (20 dB), 0.1 V; 0, 0 V

**10.32**  $v_o = [8 - 4 \sin(1000t)]$  volts; there are only two components; dc: 8 V, 159 Hz: -4 V

**10.33** 24.1 dB, 2nd and 3rd, 22.4%

**10.35** 2.4588 0.0038 5.3105 0.0066 1.3341 0.0026 0.4427 0.0028 0.0883  
0.0012 0.1863 0.0023

**10.38** 59.6 dB, 124 dB, 91.8 dB; 10.1 mV

**10.41**  $R_{id} \geq 4.95$  M $\Omega$

**10.43** 50.1  $\mu$ V, 140 dB

**10.45** (a) -46.8, 4.7 k $\Omega$ , 0, 33.4 dB

**10.47** (d)  $(-2.20 + 1.50 \sin 2500\pi t)$  V

**10.48** (a)  $v_o = (4.00 - 20V_i \sin 2000\pi t)$  V (b) 0.4 V

**10.53** 15.0 k $\Omega$ , 374 k $\Omega$ ,  $A_v = -24.9$ ,  $R_{in} = 15.0$  k $\Omega$

**10.56** -80.0, 15 kΩ, 0

**10.59** 2 MΩ

**10.60** 92.5, ∞, 0, 39.3 dB

**10.63** (d)  $(5.74 - 3.13 \sin 3250\pi t)$  V

**10.67** 1 kΩ, 200 kΩ,  $A_v = 201$

**10.69**  $-(1.88 \sin 10000t + 0.235 \sin 3770t)$  V, 0 V

**10.70**  $-0.750 \sin 4000\pi t$  V;  $-1.375 \sin 4000\pi t$  V; 0 to  $-1.875$  V in -125-mV steps

**10.71** 455/1, 50/1

**10.72** -10, 110 kΩ, 10 kΩ, ,  $(-30 + 15\cos 8300\pi t)$  V,  $(-30 + 30\cos 8300\pi t)$  V

**10.73** 3.1 V, 3.2 V, 2.91 V, 2.91 V, 1.00 V, 0 V; 1.91 μA; 1.91 μA, 2.90 μA

**10.76** 60 dB, 10 kHz, 10 Hz, 9.99 kHz, band-pass amplifier

**10.78** 80 dB, ∞, 100 Hz, ∞, high-pass amplifier

**10.81** 60 dB, 100 kHz, 28.3 Hz, 100 kHz, band-pass amplifier

**10.83** Using MATLAB:  $n = [1e4 \ 0]$ ;  $d = [1 \ 200*pi]$ ;  $bode(n,d)$

**10.84** (a) Using MATLAB:  $n = [-20 \ 0 \ -2e13]$ ;  $d = [1 \ 1e4 \ 1e12]$ ;  $bode(n,d)$

**10.86**  $0.030 \sin(2\pi t + 89.4^\circ)$  V,  $1.34 \sin(100\pi t + 63.4^\circ)$  V,  $3.00 \sin(10^4\pi t + 1.15^\circ)$  V

**10.89**  $0.956 \sin(3.18 \times 10^5 \pi t + 101^\circ)$  V,  $5.00 \sin(10^5 \pi t + 180^\circ)$  V,  $5.00 \sin(4 \times 10^5 \pi t - 179^\circ)$  V

$$\mathbf{10.91} \quad A_v(s) = \frac{2x10^8\pi}{s+10^7\pi} \quad | \quad A_v(s) = -\frac{2x10^8\pi}{s+10^7\pi}$$

**10.93** 12.8 kHz, -60 dB/decade

**10.94**  $3.16 \sin(1000\pi t + 10^\circ) + 1.05 \sin(3000\pi t + 30^\circ) + 0.632 \sin(5000\pi t + 50^\circ)$  V

Using MATLAB:

```
t = linspace(0,.004);
A=10^(10/20);
vs = sin(1000*pi*t)+0.333*sin(3000*pi*t)+0.200*sin(5000*pi*t);
vo = A*sin(1000*pi*t+pi/18)+3.33*sin(3000*pi*t+3*pi/18)+2.00*sin(5000*pi*t+5*pi/18);
plot(t, A*vs, t, vo)
```

**10.96** -4.44 dB, 26.5 kHz

**10.97** 11 kΩ, 0.015 μF

**10.100** 60 dB, 100 Hz

**10.101** -1.00 dB, 173 Hz

**10.104** (b) -20.7, 29.5 kHz

**10.105** 20 kΩ, 200 kΩ, 8200 πF

**10.107**  $0.265 \cos(2000\pi t)$  V

**10.109**  $A_v(s) = \frac{V_o}{V_i} = +\frac{1+K}{sRC}$

**10.110**  $T(s) = -sRC$

**10.113**  $-6.00, 20.0 \text{ k}\Omega, 0; +9.00, 91.0 \text{ k}\Omega, 0; 0, 160 \text{ k}\Omega, 0$

**10.114**  $0.5 \text{ A}, 2.00 \text{ V}, > 5 \text{ W}$  (choose 7.5 W)

**10.115**  $0.968 \text{ A}; 0.748 \text{ V}; 0.748 \text{ V}; \geq 14.5 \text{ W}$  (choose 20 W), 14.5 W

## Chapter 11

**11.1** (c) 2.50, 8.00, 5.71, 28.6 %

**11.3** 124 dB

**11.4**  $1/(1+A\beta)$ ;  $9.99 \times 10^{-3}$  percent

**11.5** (a) 13.49,  $9.11 \times 10^{-3}$ , 0.0675%

**11.7** 120 dB

**11.9** (a) -19.98,  $2.10 \times 10^{-2}$ , 0.105%

**11.13** 106 dB

**11.15** 100  $\mu$ A, 100  $\mu$ A, -48.0 pA, +48.0 pA

**11.17** (a) 13.5, 296 M $\Omega$ , 135 m $\Omega$

**11.20** (a) -19.6, 2.40 k $\Omega$ , 82.1 m $\Omega$

**11.22** If the gain specification is met with a non-inverting amplifier, the input and output specifications cannot be met.

**11.24** 157V<sub>s</sub>, 1.95  $\Omega$

**11.26**  $\leq 0.75$  %

**11.27** (b) shunt-series feedback (d) series-shunt feedback

**11.29** (a) Series-shunt (a) and and series-series (c) feedback

**11.32** 110 dB, 6.32 S

**11.34** 9.97, 10.3 M $\Omega$ , 2.43  $\Omega$

**11.35** 9110, 3.00, 3.00, 368 M $\Omega$ , 0.400  $\Omega$

**11.37** (a)  $+T/(1+T) \approx +1$  (c)  $-T/(1+T) \approx -1$

**11.39** -9.997 k $\Omega$ , 2.333  $\Omega$ , 0.2999  $\Omega$

**11.41** -23.99 k $\Omega$ , 5.957  $\Omega$ , 0.4398  $\Omega$

**11.44**  $20000s/(s+4170)$ ,  $20000/(4.80s+1)$

**11.48** -3.33 mS, 26.8 M $\Omega$ , 8.74 M $\Omega$

**11.54** 1.097, 28.12  $\Omega$ , 4.775 M $\Omega$

**11.56** 10.98, 15.17  $\Omega$ , 33.11 M $\Omega$

**11.57** 680.4, 0.334

**11.59** 6330, 0.0260

**11.61** 6.25 %, 16.7 %

**11.62** 0.00372 %, 0.0183 %

**11.63** 0 V, -26 mV, 90.9 k $\Omega$

**11.65** +7500, -0.667 mV

**11.67** The nearest 5% values are 1 M $\Omega$  and 5.1 k $\Omega$

**11.69** +6.8 V, 0 V; -10 V, +0.462 V

**11.71** -5.00 V, 0 V; -10.0 V, +0.182 V

**11.73** 12 V, 0 V; 15 V, 0.225 V

**11.76** 110  $\Omega$  and 22 k $\Omega$  represent the smallest acceptable resistor pair.

**11.78** 32.8  $\Omega$

**11.80** 0 V, 3 V; 0.105 V; 0 V; 49.0 dB

**11.82** (d) [0.357 sin(120 $\pi$ t) - 4.91 sin(5000 $\pi$ t)] V

**11.84** The middle resistor in Fig. P11.84 should be 20 k $\Omega$ , and part (b) should refer to the 20 k $\Omega$  resistor. (b) 124 dB

**11.85** 66 dB

**11.86** 20.0 k $\Omega$ , 56.0 k $\Omega$

**11.87** (a) 20 Hz (c) 104 dB

**11.89** 50 Hz; 5 MHz; 2.5 MHz

**11.91** 200; 199

**11.93** 80 dB, 1 kHz, 1 MHz; 101 MHz, 9.90 Hz; 251 MHz, 3.98 Hz

**11.95** 100 dB, 1 kHz, 1 MHz; 8.4 Hz, 119 MHz; 5.3 Hz, 188 MHz

**11.96** (a)  $R_o(s + \omega_B)/(s + \omega_B(1 + A_o\beta))$

**11.99** (a)  $R_{id}[s + \omega_B(1 + A_o\beta)]/(s + \omega_B)$

**11.103**  $A_v(s) = -\frac{3.285 \times 10^{12}}{s^2 + 1.284 \times 10^7 s + 1.675 \times 10^{11}}$ ; (2 poles: 2.08 kHz and 2.04 MHz)

**11.105**  $A_v(s) = -\frac{6.283 \times 10^{10}}{s^2 + 3.142 \times 10^7 s + 6.283 \times 10^5}$ ; (2 poles: 3.18 mHz and 5.00 MHz)

**11.107** 6.91, 7.53, 6.35; 145 kHz, 157 kHz, 133 kHz

**11.109** 3.14 V/ $\mu$ s; 3.14 V/ms

**11.111** 10 V/ $\mu$ s

**11.115**  $10^{10} \Omega$ , 7.96 pF,  $4 \times 10^6$ ,  $R_o$  not specified

**11.117**  $90.6^\circ$ ;  $90.2^\circ$

**11.118**  $8.1^\circ$ ;  $5.1^\circ$

**11.120** 110 kHz;  $A \leq 2048$ ; larger

**11.121** Yes, but almost no phase margin;  $0.4^\circ$

**11.123**  $88^\circ$  versus  $90^\circ$ ;  $90^\circ$  versus  $90^\circ$

**11.126** 10 MHz,  $90.0^\circ$ ; 5 MHz,  $90.0^\circ$

$$\mathbf{11.128} \quad A_v(s) = -\frac{3.770 \times 10^{10}}{s^2 + 1.885 \times 10^7 s + 3.770 \times 10^5}; \quad 90^\circ$$

**11.130** Yes, but almost no phase margin;  $1.83^\circ$

**11.132**  $90.0^\circ$

**11.134**  $12^\circ$ ; Yes, 796 pF  $\rightarrow 50^\circ$

**11.139** Yes,  $24.4^\circ$ , 50 %

**11.141**  $1.8^\circ$

**11.142**  $38.4^\circ$ , 31 %

**11.145** 133 pF

**11.147**  $90.1^\circ$

**11.150** (a)  $72.2^\circ$

**11.151** (a) 44.4 MHz,  $8.09^\circ$ , 80.0%

**11.153** (a) 34.4, 23.4%

**11.155** (a) 12.5 MHz

## Chapter 12

- 12.1** *A* and *B* taken together, *B* and *C* taken together
- 12.3** -6500, 3 k $\Omega$ , 0
- 12.5** 72, 556 M $\Omega$ , 4.50 m $\Omega$
- 12.7** 76.3 dB, 3.00 k $\Omega$ , 98.3 m $\Omega$
- 12.8** (c) 2.00 mV, -37.3 mV, 3.73  $\mu$ V, 0.696 V, 69.6  $\mu$ V, 0 V, -12.0 V, 50.4 mV, 0V (ground node)
- 12.11** -2960, 3.9 k $\Omega$ , 0
- 12.12** “2-k $\Omega$ ” should be 3-k $\Omega$ ; 12.1 k $\Omega$ , 12.1 k $\Omega$
- 12.16** 3050, 3440, 2704, 1 M $\Omega$ , 1.02 M $\Omega$ , 980 k $\Omega$ , 0
- 12.17** -2970, 120 k $\Omega$ , 0; 4.00 mV, 4.00 mV, 54.0 mV, 0 V, -1.08 V, -1.08 V, -11.9 V, 0V (ground node)
- 12.19** (a) -15.0, 188 kHz; -4.70, 526 kHz; +70.4, 169 kHz
- 12.21** 14.5, 345 kHz, 69.7 dB, 176 kHz
- 12.23** -2648, 662 M $\Omega$ , 75.5 m $\Omega$ , 26.0 kHz; 0 V, 10.0 mV, 49.2 mV, 215  $\mu$ V, -4.30 V, -3.06 V, -15.0 V, +15.0 V, -15.0 V, 0 V
- 12.25** 3
- 12.27** 20 k $\Omega$ , 62 k $\Omega$ , 394 kHz
- 12.30** 103 dB, 98.5 dB, 65 kHz, 38 kHz
- 12.33** (a) In a simulation of 5000 cases, 33.5% of the amplifiers failed to meet one of the specifications. (b) 1.5% tolerance.
- 12.36** -12, (-6.00 + 2.40 sin 4000 $\pi$ t) V
- 12.38** 6.00 V, 5.02 V, 4.98 V, 4.00 V, 1.998 V, 1.998 V, 2.012 V, -600  $\mu$ A, 0  $\mu$ A, +400  $\mu$ A, 0.002, -50.0, 88 dB
- 12.40** (b) 0.005  $\mu$ F, 0.0025  $\mu$ F, 900  $\Omega$
- 12.44** 
$$\frac{V_o}{V_s} = \frac{K}{s^2 R_1 R_2 C_1 C_2 + s[R_1 C_1(1-K) + C_2(R_1 + R_2)] + 1} \quad | \quad S_K^Q = \frac{K}{3-K}$$
- 12.46** -1
- 12.48** 270 pF, 270 pF, 19.1 k $\Omega$
- 12.49** (a) 51.2 kHz, 7.07, 7.24 kHz

**12.52** (a) 1 rad/s, 4.65, 0.215 rad/s;  $A_{BP}(s) = \left( \frac{-6s}{s^2 + \frac{s}{3} + 1} \right)^2$

**12.54** 5.48 kHz, 4.09, 1.34 kHz

**12.56**  $T = +K \frac{\frac{s}{R_2 C_2}}{s^2 + s \left[ \frac{1}{R_2 C_2} + \frac{1}{(R_l \| R_2) C_1} \right] + \frac{1}{R_l R_2 C_l C_2}}$

**12.62** -5.5 V, -5.5, 10 %; -5.0 V, -5.0, 0

**12.64** 12.6 kHz, 1.58, 7.97 kHz

**12.67** (a) -0.960 V (b) -1.440 V

**12.68** 10.6 mV, 5 %

**12.71** 379/1, 41.7/1

**12.73** 0.66 LSB, 0.33 LSB

**12.74** 1.43%, 2.5%, 5%, 10%

**12.75** 12 resistors, 4096:1

**12.77** (a) 1.0742 k $\Omega$ , 0.188 LSB, 0.094 LSB

**12.79** (a)  $(2^{n+1}-1)C$

**12.82** (b) 1.01 inches

**12.83**  $3.49546875 \leq V_X \leq 3.49578125$  V

**12.84** 1.90735  $\mu$ V, 11010000101101000100<sub>2</sub>, 01111111001111010111<sub>2</sub>

**12.87** 0001011101<sub>2</sub>, 93  $\mu$ s

**12.89** 800 kHz, 125 ns

**12.91**  $v_o(t) = 2 \times 10^5 \left( 1 - \exp \frac{-t}{4 \times 10^4 RC} \right)$  for  $t \geq 0$  |  $RC \geq 0.050$  s

**12.92** 19.1 ns

**12.95** 0.5774/RC, 1.83

**12.96** 1/RC, 2R

**12.98** 60 kHz, 6.8 V

**12.100** 17.5 kHz, 11.5 V

**12.104** 0.759 V

**12.105** 2.40 Hz

**12.110**  $V_o = -\frac{V_1 V_2}{10^4 I_s}$

**12.111** 3.11 V, 2.83 V, 0.28 V

**12.113** 0.445 V, -0.445 V, 0.89 V

**12.115** 9.86 kHz

**12.116**  $V_O = 0$  is a stable state, so the circuit does not oscillate.  $f = 0$ .

**12.118** 0, 0.298 V, 69.0 mV

**12.120** 42 k $\Omega$ , 2 k $\Omega$ , 51 k $\Omega$ , 120 pF

## Chapter 13

- 13.1**  $(0.700 + 0.005 \sin 2000\pi t)$  V,  $-1.03 \sin 2000\pi t$  V,  $(5.00 - 1.03 \sin 2000\pi t)$  V.  $2.82$  mA
- 13.3** (a)  $C_1$  is a coupling capacitor that couples the ac component of  $v_i$  into the amplifier.  $C_2$  is a coupling capacitor that couples the ac component of the signal at the collector to the output  $v_o$ .  $C_3$  is a bypass capacitor. (b) The signal voltage at the top of resistor  $R_4$  will be zero.
- 13.5** (a)  $C_1$  is a coupling capacitor that couples the ac component of  $v_i$  into the amplifier.  $C_2$  is a bypass capacitor.  $C_3$  is a coupling capacitor that couples the ac component of the signal at the drain to output  $v_o$ . (b) The signal voltage at the source of  $M_1$  will be  $v_s = 0$ .
- 13.7** (a)  $C_1$  is a coupling capacitor that couples the ac component of  $v_i$  into the amplifier.  $C_2$  is a bypass capacitor.  $C_3$  is a coupling capacitor that couples the ac component of the signal at the collector to output  $v_o$ . (b) The signal voltage at the emitter terminal will be  $v_e = 0$ .
- 13.9** (a)  $C_1$  is a coupling capacitor that couples the ac component of  $v_i$  into the amplifier.  $C_2$  is a coupling capacitor that couples the ac component of the signal at the drain to output  $v_o$ .
- 13.12** (a)  $C_1$  is a coupling capacitor that couples the ac component of  $v_i$  into the amplifier.  $C_2$  is a bypass capacitor.  $C_3$  is a coupling capacitor that couples the ac component of the signal at the drain to the output  $v_o$ . (b) The signal voltage at the top of  $R_4$  will be zero.
- 13.16** (1.91 mA, 2.78 V)
- 13.18** (a) (18.3  $\mu$ A, 6.50 V)
- 13.20** (56.4  $\mu$ A, 3.67 V)
- 13.24** (99.7  $\mu$ A, 9.74 V)
- 13.28** (184  $\mu$ A, 15.5 V)
- 13.32** (943  $\mu$ A, -7.89 V)
- 13.34** (1.01 mA, 9.20 V)
- 13.43** Thévenin equivalent source resistance, gate-bias voltage divider, gate-bias voltage divider, source-bias resistor—sets source current, drain-bias resistor—sets drain-source voltage, load resistor
- 13.45**  $118 \Omega$ ,  $3.13 \text{ T}\Omega$ ,  $\leq -28.5$  mV
- 13.46** (c)  $8.65 \Omega$
- 13.47** Errors: +10.7%, -9.37%; +23.0%, -17.5%

**13.48** (c) 1.00  $\mu\text{A}$

**13.49** (188  $\mu\text{A}$ ,  $\geq 0.7 \text{ V}$ ), 7.50 mS, 533  $\text{k}\Omega$

**13.54** (b) +16.7%, -13.6%

**13.55** 90, 120; 95, 75

**13.60** [-59.0, -58.3]

**13.62** -48.1

**13.66** -90

**13.68** Yes, using  $I_C R_C = \frac{V_{CC} + V_{EE}}{2}$

**13.70** 3

**13.71** 25 mA; 30.7 V

**13.72** 1.00 V

**13.73** No, there will be significant distortion

**13.74** -345

**13.79** 40/1, 0.500 V

**13.80** 0.960 A

**13.81** 10%, 20%

**13.84** (66  $\mu\text{A}$ , 7.5 V)

**13.85** Virtually any desired Q-point (set by the choice of  $R_G$ )

**13.86**  $400 = 133,000i_P + v_{PK}$ ; (1.4 mA, 215 V); 1.6 mS, 55.6  $\text{k}\Omega$ , 89.0; -62.7

**13.87** FET

**13.88** BJT

**13.89** 35.3  $\mu\text{A}$ , 2800

**13.90** 2000, 200, 8.00 mS, 0.800 mS

**13.93** 23.5 dB

**13.95** (180  $\mu\text{A}$ , 9.0 V)

**13.96** 0.360 V

**13.97** 1.0 V, 45 V

**13.99** 3

**13.101** -10.3

**13.104** -6.66

- 13.109**  $25.0 \text{ k}\Omega, 91.9 \text{ k}\Omega$
- 13.112**  $455 \text{ k}\Omega, 1.42 \text{ M}\Omega$
- 13.114**  $243 \text{ k}\Omega, 40.1 \text{ k}\Omega$
- 13.116**  $6.8 \text{ M}\Omega, 45.8 \text{ k}\Omega$ , independent of  $K_n$
- 13.118**  $1 \text{ M}\Omega, 3.53 \text{ k}\Omega$
- 13.119**  $-150v_i, 95.5 \text{ k}\Omega$
- 13.121**  $-23.6v_i, 508 \text{ k}\Omega$
- 13.123** (a)  $38.9 \text{ dB}, 6.29 \text{ k}\Omega, 9.57 \text{ k}\Omega$
- 13.125**  $36.4 \text{ dB}, 62.9 \text{ k}\Omega, 95.7 \text{ k}\Omega$
- 13.129**  $92.6 \mu\text{W}, 221 \mu\text{W}, 1.26 \text{ mW}, 0.761 \text{ mW}, 0.865 \text{ mW}, 3.19 \text{ mW}$
- 13.133**  $528 \mu\text{W}, 765 \mu\text{W}, 252 \mu\text{W}, 51.6 \mu\text{W}, 132 \mu\text{W}, 1.73 \text{ mW}$
- 13.136**  $V_{CC}/15$
- 13.137**  $2.35 \text{ V}, 9.72 \text{ V}$
- 13.138**  $V_{CC}/2, (V_{CC})^2/8R_L, (V_{CC})^2/2R_L, 25\%$
- 13.139**  $0.955 \text{ V}$
- 13.141**  $2.35 \text{ V}$
- 13.142**  $1.86 \text{ V}$
- 13.143**  $3.19 \text{ V}$
- 13.147**  $694 \mu\text{A}$
- 13.148**  $-4.60, 1 \text{ M}\Omega, 6.82 \text{ k}\Omega$

## Chapter 14

- 14.1** (a) C-C or emitter-follower (c) C-E (e) not useful, signal is being injected into the drain (h) C-B (k) C-G (o) C-D or source-follower
- 14.16** (a) -38.5, 8.99 k $\Omega$ , 552 k $\Omega$ , -30.1, 34.7 mV
- 14.17** Assume (V<sub>GS</sub>-V<sub>TN</sub>) = 0.5 V (a) -5.82, 2 M $\Omega$ , 29.8 k $\Omega$ , -4030
- 14.18** (a) -6.52 (e) -240
- 14.19** 3.29 k $\Omega$ , 50.0 k $\Omega$
- 14.22** -215, -9.85, 22.4 k $\Omega$ , 56 k $\Omega$ , 5.11 mV
- 14.23** -145, -5.54, 3.49 k $\Omega$ , 10.0 k $\Omega$ , 6.76 mV, -120
- 14.24** -12.9, -10.1, 368 k $\Omega$ , 82 k $\Omega$ , 149 mV
- 14.26** -2.40, -667, 10 M $\Omega$ , 1.80 k $\Omega$ , 0.700 V
- 14.27** -3330, -3.65, 848  $\Omega$ , 50.1 k $\Omega$ , 6.41 mV
- 14.29** 0.779, 35.6 k $\Omega$ , 105  $\Omega$ , 29.6, 6.40 mV
- 14.30** Assume (V<sub>GS</sub>-V<sub>TN</sub>) = 0.5 V: 0.914, 2 M $\Omega$ , 125  $\Omega$ , 16,000, 2.50 V
- 14.31** 0.986, 44.6 k $\Omega$ , 13.7  $\Omega$ , 1.62 V
- 14.32** 0.961, 1 M $\Omega$ , 542  $\Omega$ , 7.02 V
- 14.33** 0.992, 12.6 M $\Omega$ , 1.18 k $\Omega$ , 0.664 V
- 14.34** 0.874, 7.94 M $\Omega$ , 247  $\Omega$ ,  $\infty$
- 14.35**  $v_i \leq (0.005 + 0.2V_{R_E})$  V
- 14.35** 0.9992, 30.1 V
- 14.39** (b) 77.7, 702  $\Omega$ , 6.88 M $\Omega$ , 0.969, 20.7 mV
- 14.40** 49.8, 1.25 k $\Omega$ ,  $\infty$ , 0.750, 1.13 V (Assume (V<sub>GS</sub>-V<sub>TN</sub>) = 1 V)
- 14.42** 43.6, 146  $\Omega$ , 39.0 k $\Omega$ , 22.1 mV
- 14.44** 4.11, 1.32 k $\Omega$ , 20.0 k $\Omega$ , 354 mV
- 14.46** 4.75, 3.19 k $\Omega$ , 24.0 k $\Omega$ , 326 mV
- 14.48** 44.4  $\Omega$ ; 260  $\Omega$
- 14.49** 633  $\Omega$ ; 408  $\Omega$
- 14.51**  $(\beta_o + 1)r_o = 198 M\Omega$

**14.52** Low  $R_{in}$ , high gain: Either a common-base amplifier operating at a current of 50.0  $\mu A$  or a common-emitter amplifier operating at a current of approximately 5.00 mA can meet the specifications with  $V_{CC} \approx 14$  V.

**14.56** Large  $R_{in}$ , moderate gain: Common-source amplifier.

**14.57** Common-drain amplifier.

**14.58** Cannot be achieved with what we know at this stage in the text.

**14.59** Low  $R_{in}$ , high gain: Common-emitter amplifier with 5- $\Omega$  input "swamping" resistor.

**14.61** Part (b) should be  $I_C = 1$  mA: (a) 4.13  $\Omega$

#### 14.64

$v_i$	1 kHz	2 kHz	3 kHz	THD
5 mV	621 mV	26.4 mV (4.2%)	0.71 mV (0.11%)	4.2%
10 mV	1.23 V	0.104 V (8.5%)	5.5 mV (0.45%)	8.5%
15 mV	1.81 V	0.228 V (12.6%)	18.2 mV (1.0%)	12.7%

**14.66** (b)  $1230v_i$ ,  $583$  k $\Omega$

**14.67**  $v_i$ ,  $297$   $\Omega$

**14.70**  $g_m$ , 0;  $-500$   $\mu S$ , 0

$$14.71 \text{ (a)} -g_m \left( 1 + \frac{1}{\mu_f} \right) + -g_o + \mu_f + 1$$

$$14.74 \text{ (a)} -\frac{g_m}{1 + g_m R_E} + -\frac{g_o}{(1 + g_m R_E)} \left( \frac{R_E}{R_E + r_\pi} \right) + \frac{G_m}{G_r} = \mu_f \left( 1 + \frac{r_\pi}{R_E} \right) \gg 1$$

**14.76** -0.984, 0.993, 0.703 V

**14.80** SPICE: (115  $\mu A$ , 6.30 V), -20.5, 368 k $\Omega$ , 65.1 k $\Omega$

**14.81** SPICE: (116  $\mu A$ , 7.53 V), -150, 19.6 k $\Omega$ , 37.0 k $\Omega$

**14.83** SPICE: (66.7  $\mu A$ , 4.47 V), -16.8, 1.10 M $\Omega$ , 81.0 k $\Omega$

**14.85** SPICE: (5.59 mA, -5.93 V), -3.27, 10.0 M $\Omega$ , 1.52 k $\Omega$

**14.87** SPICE: (6.20 mA, 12.0 V), 0.953, 2.00 M $\Omega$ , 388  $\Omega$

**14.88** SPICE: (175  $\mu A$ , 4.29 V), -4.49, 500 k $\Omega$ , 17.0 k $\Omega$

**14.89** (430  $\mu A$ , 1.93 V), (430  $\mu A$ , 3.07 V), -2.89, 193 k $\Omega$ , 3.22 k $\Omega$ , (Note  $A_{tr} = 743$  k $\Omega$ )

**14.90** (4.50 mA, 2.50 V), (4.50 mA, 2.50 V), -83.9, 8.94 k $\Omega$ , 10.5 k $\Omega$

**14.91** 0.486, 182 k $\Omega$ , 348  $\Omega$

**14.95** 1.00  $\mu F$ , 0.039  $\mu F$ , 68  $\mu F$ ; 2.7  $\mu F$

- 14.96** 2000 pF, 33 pF; 10  $\mu$ F, 150 pF
- 14.99** 0.68  $\mu$ F, 0.015  $\mu$ F
- 14.101** 8200 pF, 1500 pF
- 14.105** 33.3 mA
- 14.106**  $R_1 = 120 \text{ k}\Omega$ ,  $R_2 = 110 \text{ k}\Omega$
- 14.109**  $45.1 \leq A_v \leq 55.3$  - Only slightly beyond the limits in the Monte Carlo results.
- 14.111** The second MOSFET
- 14.114** The supply voltage is not sufficient - transistor will be saturated.
- 14.116** 4.08, 1.00 M $\Omega$ , 64.3  $\Omega$
- 14.119** 2.17, 1.00 M $\Omega$ , 64.3  $\Omega$
- 14.124** 468, 73.6 k $\Omega$ , 18.8 k $\Omega$
- 14.125** 0.670, 107 k $\Omega$ , 20.0 k $\Omega$
- 14.127** 7920, 10.0 k $\Omega$ , 18.8 k $\Omega$
- 14.128** 140, 94.7  $\Omega$ , 113  $\Omega$
- 14.132** 1.56 Hz; 1.22 Hz
- 14.133** 19.2 Hz; 18.0 Hz
- 14.134** 6.40 Hz; 5.72 Hz
- 14.136** 0.497 Hz, 0.427 Hz
- 14.137** 1.70 kHz; 1.68 kHz

## Chapter 15

- 15.1** (20.7  $\mu$ A, 5.86 V); -273, 242 k $\Omega$ , 484 k $\Omega$ ; -0.604, 47.0 dB, 27.3 M $\Omega$
- 15.2** (5.25  $\mu$ A, 1.68 V); -21.0, -0.636, 24.4 dB, 572 k $\Omega$ , 4.72 M $\Omega$ , 200 k $\Omega$ , 50.0 k $\Omega$
- 15.4** (70.8  $\mu$ A, 8.62 V); -283, -0.494, 47.1 dB, 58.4 k $\Omega$ , 10.1 M $\Omega$ , 200 k $\Omega$ , 50.0 k $\Omega$
- 15.7**  $R_{EE} = 1.1 \text{ M}\Omega$ ,  $R_C = 1.0 \text{ M}\Omega$
- 15.8** (a) (198  $\mu$ A, 3.39 V); differential output: -372, 0,  $\infty$  (b) single-ended output: -186, -0.0862, 66.7 dB; 25.2 k $\Omega$ , 27.3 M $\Omega$ , 94.0 k $\Omega$ , 23.5 k $\Omega$
- 15.10** 3.478 V, 6.258 V, -2.78 V, 4.64 V
- 15.12**  $V_O = 5.72 \text{ V}$ ,  $v_o = 0$ ;  $V_O = 5.79 \text{ V}$ ;  $v_i \leq 27 \text{ mV}$ , the small-signal limit.
- 15.15** (27.5  $\mu$ A, 4.20 V); Differential output: -220, 0,  $\infty$ ; single-ended output: -110, -0.661, 44.4 dB; 272 k $\Omega$ , 22.7 M $\Omega$
- 15.16** -6.815 V, -3.905 V, -2.91 V
- 15.20** (4.94  $\mu$ A, 1.77 V); differential output: -77.2, 0,  $\infty$ ; single-ended output: -38.6, -0.0385, 60.0 dB; 810 k $\Omega$ , 405 M $\Omega$ , [-1.07 V, 1.60 V]
- 15.21** -283, -0.00494, 95.2 dB
- 15.22** -273.6, -0.004942, 94.9 dB
- 15.24** (330  $\mu$ A, 6.83 V); differential output: -11.3, 0,  $\infty$ ; single-ended output: -5.65, -0.689, 18.3 dB;  $\infty$ ,  $\infty$
- 15.26** (329  $\mu$ A, 6.87 V); differential output: -8.8, 0,  $\infty$ ; single-ended output: -4.40, -0.677, 16.3 dB;  $\infty$ ,  $\infty$
- 15.29** 5.1 k $\Omega$ , 27 k $\Omega$
- 15.30** (70.2  $\mu$ A, 10.9 V); differential output: -14.7, 0,  $\infty$ ; single-ended output: -7.35, -0.484, 23.6 dB;  $\infty$ ,  $\infty$ ; (83.5  $\mu$ A, 8.47 V)
- 15.33** (750  $\mu$ A, 3.50 V); differential output: -11.3, 0,  $\infty$ ; single-ended output: -5.65, -0.223, 28.1 dB;  $\infty$ ,  $\infty$
- 15.34** (750  $\mu$ A, 4.25 V); differential output: -5.63, 0,  $\infty$ ; single-ended output: -2.81, -0.218, 22.2 dB;  $\infty$ ,  $\infty$
- 15.35** (20.0  $\mu$ A, 10.3 V); differential output: -38.1, 0,  $\infty$ ; single-ended output: -19.0, -0.120, 44.0 dB;  $\infty$ ,  $\infty$
- 15.38** 312  $\mu$ A, 27 k $\Omega$
- 15.41** -20.26, -0.7812, 22.3 dB,  $\infty$ ,  $\infty$
- 15.44** -3.80 V, -2.64 V, 40 mV
- 15.47** -79.85, -0.4936, 751.4 k $\Omega$

- 15.48** (99.0  $\mu\text{A}$ , 6.80 V), -30.4, -0.167, 550 k $\Omega$
- 15.50** (49.5  $\mu\text{A}$ , 3.29 V), (49.5  $\mu\text{A}$ , 11.7 V); -149, -0.0625, 101 k $\Omega$
- 15.51** (100  $\mu\text{A}$ , 1.38 V), (100  $\mu\text{A}$ , 4.68 V); -13.4, 0,  $\infty$
- 15.54** (24.8  $\mu\text{A}$ , 18.0 V), (750  $\mu\text{A}$ , 18.0 V); 8980, 202 k $\Omega$ ; 19.5 k $\Omega$ ; 160 M $\Omega$ ;  $v_2$
- 15.56** 6.33 mV, 106 dB, PSRR<sub>+</sub> = 105 dB, PSRR<sub>-</sub> = 60.3 dB
- 15.58** [-16.6 V, 17.3 V]
- 15.63** 4550, 21.98 nA, 0.879  $\mu\text{A}$ , 99.1  $\mu\text{A}$ , 72.8 M $\Omega$ , 653 k $\Omega$
- 15.66** (24.8  $\mu\text{A}$ , 17.3 V), (7.35  $\mu\text{A}$ , 17.3 V), (743  $\mu\text{A}$ , 18.0 V); 6760, 202 k $\Omega$ ; 17.9 k $\Omega$ ; 158 M $\Omega$ ;  $v_2$
- 15.67** (98.8  $\mu\text{A}$ , 20.9 V), (440  $\mu\text{A}$ , 20.9 V); 699, 40.5 k $\Omega$ ; 48.6 k $\Omega$
- 15.68** (98.8  $\mu\text{A}$ , 18.0 V), (8.8  $\mu\text{A}$ , 18.0 V), (360  $\mu\text{A}$ , 18.0 V); 3740, 40.4 k $\Omega$ ; 36.1 M $\Omega$
- 15.70** 390  $\Omega$ , 1.1 k  $\Omega$ , 3.74 mA
- 15.75** (250  $\mu\text{A}$ , 15.6 V), (500  $\mu\text{A}$ , 15.0 V); 3300,  $\infty$ ; 165 k $\Omega$
- 15.78** 5770
- 15.79** [-5.32 V, 2.93 V]
- 15.80** (250  $\mu\text{A}$ , 7.42 V), (6.10  $\mu\text{A}$ , 4.30 V), (494  $\mu\text{A}$ , 5.00 V); 4230,  $\infty$ ; 97.5 k $\Omega$
- 15.84** (49.5  $\mu\text{A}$ , 22.0 V), (360  $\mu\text{A}$ , 21.3 V), (990  $\mu\text{A}$ , 22.0 V); 13500, 101 k $\Omega$ ; 1.98 k $\Omega$ ; 73.5 M $\Omega$ ;  $v_2$
- 15.86** (300  $\mu\text{A}$ , 6.10 V), (500  $\mu\text{A}$ , 3.89 V), (2.00 mA, 6.00 V); 541,  $\infty$ , 339  $\Omega$
- 15.88** (300  $\mu\text{A}$ , 6.55 V), (500  $\mu\text{A}$ , 3.89 V), (2.00 mA, 6.00 V), 3000,  $\infty$ , 336  $\Omega$
- 15.90** Error in Problem Statement:  $K_n = 5 \text{ mS}$   
(375  $\mu\text{A}$ , 11.0 V), (2.00 mA, 9.84 V), (5.00 mA, 12.0 V); 708,  $\infty$ ; 127  $\Omega$
- 15.91** Error in Problem Statement:  $K_n = 5 \text{ mS}$   
(375  $\mu\text{A}$ , 11.7 V), (2.00 mA, 9.75 V), (5.00 mA, 12.0 V); 1270,  $\infty$ ; 159  $\Omega$
- 15.92** 15.32 mV, 77.5 dB, PSRR<sub>+</sub> = 77.5 dB, PSRR<sub>-</sub> is limited by numerical noise
- 15.93** (99.0  $\mu\text{A}$ , 4.96 V), (99.0  $\mu\text{A}$ , 5.00 V), (500  $\mu\text{A}$ , 3.41V), (2.00 mA, 5.00 V); 11400, 50.5 k $\Omega$ , 224  $\Omega$
- 15.95** (49.5  $\mu\text{A}$ , 10.0 V), (98.0  $\mu\text{A}$ , 9.30 V), (735  $\mu\text{A}$ , 15.0 V); 2680, 101 k $\Omega$ , 3.05 k $\Omega$ ; [undefined for an ideal current source, +9.3 V]; 1.81 mV
- 15.97** No,  $R_{id}$  must be reduced or  $R_{out}$  must be increased.

- 15.108** 30.6  $\mu\text{A}$
- 15.111** 438  $\mu\text{A}$
- 15.114** 32.2  $\mu\text{A}$
- 15.116** 4 mA, 0 mA, 8 mA, 10.0 percent
- 15.117** 66.7 percent
- 15.120** 46.7 mA, 13.5 V
- 15.122** 23.5  $\mu\text{A}$
- 15.123** 6.98 mA, 0 mA
- 15.124** 25.0  $\text{m}\Omega$
- 15.126** (a) 18.7  $\mu\text{A}$ , 61.5  $\text{M}\Omega$
- 15.129** (a) 134  $\mu\text{A}$ , 8.19  $\text{M}\Omega$
- 15.130** Two of many: 75  $\text{k}\Omega$ , 6.2  $\text{k}\Omega$ , 150  $\Omega$ ; 68  $\text{k}\Omega$ , 12  $\text{k}\Omega$ , 1  $\text{k}\Omega$
- 15.131** 570  $\mu\text{A}$ , 655  $\text{k}\Omega$
- 15.132** 543  $\mu\text{A}$ , 674  $\text{k}\Omega$
- 15.135** 0,  $\infty$
- 15.136** 68.0  $\mu\text{A}$ , 22.4  $\text{M}\Omega$
- 15.139** 19.6  $\mu\text{A}$ , 123  $\text{M}\Omega$
- 15.142** 390  $\text{k}\Omega$ , 210  $\text{k}\Omega$ , 33  $\text{k}\Omega$
- 15.144** 157.4  $\mu\text{A}$ , 16.61  $\text{M}\Omega$ , 31.89  $\mu\text{A}$ , 112.2  $\text{M}\Omega$
- 15.145** 139  $\mu\text{A}$ , 3.15  $\text{M}\Omega$ , 486  $\mu\text{A}$ , 432  $\text{k}\Omega$
- 15.149** 100  $\mu\text{A}$ ,  $6.57 \times 10^{11} \Omega$
- 15.150** (4.64  $\mu\text{A}$ , 7.13 V), (9.38  $\mu\text{A}$ , 9.02 V); 40.9 dB, 96.5 dB
- 15.153**  $\beta_{o1}\mu_{f1}/2$ , For typical numbers:  $(100)(40)(70)/2 = 140,000$  or 103 dB
- 15.141**  $3\sigma$  limits:  $I_O = 200 \mu\text{A} \pm 31.9 \mu\text{A}$ ,  $R_{\text{OUT}} = 11.7 \text{ M}\Omega \pm 2.1 \text{ M}\Omega$   
 $3\sigma$  limits:  $I_O = 197 \mu\text{A} \pm 33.8 \mu\text{A}$ ,  $R_{\text{OUT}} = 11.5 \text{ M}\Omega \pm 1.7 \text{ M}\Omega$

## Chapter 16

- 16.1** [4.39 k $\Omega$ , 4.62 k $\Omega$ ]
- 16.2** 2.00 mV; 3.76 mV; 2%
- 16.4** 7.7%, 0.678  $\mu$ A, 0.712  $\mu$ A, ( $I_{OS} = -34.7$  nA)
- 16.7** 25.0 mV; 1.2%; 0.4%
- 16.8** (a) 122  $\mu$ A, 239  $\mu$ A, 496  $\mu$ A, 904 k $\Omega$ , 452 k $\Omega$ , 226 k $\Omega$
- 16.11** 87.5  $\mu$ A, 175  $\mu$ A, 350  $\mu$ A; 0.0834 LSB, 0.126 LSB, 0.411 LSB
- 16.12** 273  $\mu$ A, 385 k $\Omega$ , 574  $\mu$ A, 192 k $\Omega$
- 16.16** (a) 687  $\mu$ A, 94.6 k $\Omega$ , 1.11 mA, 56.8 k $\Omega$
- 16.18** 469 k $\Omega$ , 109  $\mu$ A; 515 k $\Omega$ , 109  $\mu$ A
- 16.21** 202  $\mu$ A, 327  $\mu$ A
- 16.22** Use  $\beta_{FO} = 80$  and  $V_A = 60$  V.  
514  $\mu$ A, 827  $\mu$ A; 522  $\mu$ A, 827  $\mu$ A; 423  $\mu$ A, 681  $\mu$ A
- 16.24 Use transistor parameters from Prob. 16.23**  
581 k $\Omega$ , 13.6  $\mu$ A, 142  $\mu$ A
- 16.26** 10
- 16.28** 15 k $\Omega$ , 2/3
- 16.30** 142  $\mu$ A, 592 M $\Omega$
- 16.32** 4.90 k $\Omega$ ; 4.90 k $\Omega$
- 16.34** 215 k $\Omega$ , 13.9 k $\Omega$ , 0.556
- 16.36** (a) 21.8  $\mu$ A, 18.4 M $\Omega$
- 16.38** (a) 24.8  $\mu$ A, 143 M $\Omega$  (c) 1410 V
- 16.42** (a) 14.0  $\mu$ A, 80/1; 122 M $\Omega$
- 16.44** (a) 2/g<sub>m2</sub>
- 16.46** 9.49/1
- 16.49** 23.1 M $\Omega$ , 0, 6.04, 163 M $\Omega$
- 16.51** n = 4: 643 k $\Omega$ , 0.25, 27.8, 14.8 M $\Omega$
- 16.52** 40.0  $\mu$ A, 335 M $\Omega$ ; 13.4 kV; 2.81 V
- 16.54** 2  $\mu$ A or 5%, 12.5 nA
- 16.57** (b) 50  $\mu$ A, 240 M $\Omega$ ; 12.0 kV; 3.05 V

**16.60** 193  $\mu\text{A}$ , 171  $\text{M}\Omega$ , 3300 V;  $2V_{BE} = 1.40 \text{ V}$

**16.63** 2.50  $\text{k}\Omega$

**16.65**  $\approx \beta_o r_{o4}/2$

**16.66** (a) 102  $\text{G}\Omega$

**16.67** (a) 51.0  $\text{G}\Omega$

**16.73** (a) 66.5  $\mu\text{A}$ , 3.07  $\text{M}\Omega$

**16.75** 5.86  $\text{k}\Omega$

**16.77** 317  $\mu\text{A}$ ; 295  $\mu\text{A}$ ; 43.7  $\mu\text{A}$

**16.80** 13.2  $\text{k}\Omega$ , 332  $\text{k}\Omega$

**16.82** 8.48  $\text{k}\Omega$ , 449  $\text{k}\Omega$

**16.84**  $I_{C1} = 111 \mu\text{A}$ ,  $I_{C2} = 37.9 \mu\text{A}$ ,  $S_{V_{CC}}^{I_{C1}} = 0.147$ ,  $S_{V_{CC}}^{I_{C2}} = 0.0496$

**16.86**  $n > 1/3$

**16.88** 38.9  $\mu\text{A}$

**16.90** (b)  $I_{D1} = 8.19 \mu\text{A}$   $I_{D2} = 7.24 \mu\text{A}$   $S_{V_{DD}}^{I_{D1}} = 7.75 \times 10^{-2}$   $S_{V_{DD}}^{I_{D2}} = 6.31 \times 10^{-2}$

The currents differ considerably from the hand calculations. The currents are quite sensitive to the value of  $\lambda$ . The hand calculations used  $\lambda = 0$ . If the simulations are run with  $\lambda = 0$ , then the results are identical to the hand calculations.

**16.92** 4.57  $\mu\text{A}$ , 11.4  $\mu\text{A}$ , 3.16  $\mu\text{A}$ , 22.9  $\mu\text{A}$ , 2.91  $\mu\text{A}$

**16.94**  $I_{C2} = 18.3 \mu\text{A}$   $I_{C1} = 34.1 \mu\text{A}$  - Similar to hand calculations.

$$S_{V_{CC}}^{I_{C1}} = 9.36 \times 10^{-3} \quad S_{V_{CC}}^{I_{C2}} = 2.64 \times 10^{-3}$$

**16.96** (a) 331  $\mu\text{A}$ , 220  $\mu\text{A}$

**16.98** (a) 199  $\mu\text{A}$ , 166  $\mu\text{A}$

**16.101** 1.20 V, 304.9 K

**16.103** 4.90 V, 327.4 K

**16.104** 5.07 V, +44.0  $\mu\text{V/K}$

**16.106** -472  $\mu\text{V/K}$ , -199  $\mu\text{V/K}$

**16.109** 60.9,  $9.02 \times 10^{-5}$ , 117 dB,  $\pm 8.2 \text{ V}$

**16.111** 90.9,  $7.29 \times 10^{-5}$ , 122 dB

**16.113** 1200,  $4 \times 10^{-3}$ , 110 dB,  $\pm 2.9 \text{ V}$

- 16.117**  $R_{SS} = 25 \text{ M}\Omega$   
 (100  $\mu\text{A}$ , 8.70 V), (100  $\mu\text{A}$ , 8.70 V), (100  $\mu\text{A}$ , -2.50 V), (100  $\mu\text{A}$ , -1.25 V),  
 (100  $\mu\text{A}$ , -1.25 V); 323; 152; 4.18 mV
- 16.119** (125  $\mu\text{A}$ , 1.54 V), (125  $\mu\text{A}$ , -2.79 V), (125  $\mu\text{A}$ , 2.50 V), (125  $\mu\text{A}$ , 1.25 V); 19600
- 16.123** 171  $\mu\text{A}$
- 16.124** (b) 100  $\mu\text{A}$
- 16.125** (250  $\mu\text{A}$ , 5.00 V), (250  $\mu\text{A}$ , 5.00 V), (250  $\mu\text{A}$ , -1.46 V), (250  $\mu\text{A}$ , -1.46 V), (500  $\mu\text{A}$ , -3.63 V), (97.7  $\mu\text{A}$ , 5.00 V), (97.7  $\mu\text{A}$ , -5.00 V), (250  $\mu\text{A}$ , 1.75V), (500  $\mu\text{A}$ , 3.54 V), (500  $\mu\text{A}$ , 3.63 V), (500  $\mu\text{A}$ , 3.54 V); 8340; 4170
- 16.127** (250  $\mu\text{A}$ , 7.50 V), (250  $\mu\text{A}$ , 7.50 V), (250  $\mu\text{A}$ , -1.46 V), (250  $\mu\text{A}$ , -1.46 V), (500  $\mu\text{A}$ , -6.12 V), (99.2  $\mu\text{A}$ , 7.50 V), (99.2  $\mu\text{A}$ , -7.50 V), (500  $\mu\text{A}$ , 2.75 V), (250  $\mu\text{A}$ , 1.75 V), (500  $\mu\text{A}$ , 5.75 V), (500  $\mu\text{A}$ , 6.12 V), 3160. 278  $\mu\text{V}$
- 16.128** 25300
- 16.131** (b) 31.2/1 (c) 39500
- 16.136** 7.81, 703  $\Omega$ ,  $3.02 \times 10^5$ , 75.0 k $\Omega$
- 16.138**  $\pm 1.4 \text{ V}$ ,  $\pm 2.4 \text{ V}$
- 16.139** (a) 9.72  $\mu\text{A}$ , 138  $\mu\text{A}$ , 46.0  $\mu\text{A}$
- 16.140** 271 k $\Omega$ , 255  $\Omega$
- 16.142**  $V_{EE} \geq 2.8 \text{ V}$ ,  $V_{CC} \geq 1.4 \text{ V}$ ; 3.8 V, 2.4 V
- 16.144** 2.84 M $\Omega$ , 356 k $\Omega$ .  $6.11 \times 10^5$
- 16.147** (80  $\mu\text{A}$ , 15.7 V), (80  $\mu\text{A}$ , 15.7 V), (40  $\mu\text{A}$ , -12.9 V), (40  $\mu\text{A}$ , -0.700 V), (40  $\mu\text{A}$ , -0.700 V), (40  $\mu\text{A}$ , -12.9 V), (40  $\mu\text{A}$ , 1.40 V), (40  $\mu\text{A}$ , 1.40 V), (1.60  $\mu\text{A}$ , 29.3 V), (80  $\mu\text{A}$ , 0.700 V), (80  $\mu\text{A}$ , 13.6 V); 0.800 mS, 940 k $\Omega$
- 16.148** (37.5  $\mu\text{A}$ , 15.7 V), (37.5  $\mu\text{A}$ , 15.7 V), (37.5  $\mu\text{A}$ , 12.9 V), (37.5  $\mu\text{A}$ , 12.9 V), (37.5  $\mu\text{A}$ , 1.40 V), (37.5  $\mu\text{A}$ , 1.40 V), (0.75  $\mu\text{A}$ , 29.3 V), (75  $\mu\text{A}$ , 1.40 V), (0.75  $\mu\text{A}$ , 0.700 V), (0.75  $\mu\text{A}$ , 13.6 V); 0.750 mS, 1.15 M $\Omega$
- 16.150** (50  $\mu\text{A}$ , 2.50 V), (25  $\mu\text{A}$ , 3.20 V)
- 16.151** (a) 125  $\mu\text{A}$ , 75  $\mu\text{A}$ , 62.5  $\mu\text{A}$ , 37.5  $\mu\text{A}$ ,
- 16.146**  $(500 - 195 \sin 5000\pi t) \mu\text{A}$ ,  $(500 + 195 \sin 5000\pi t) \mu\text{A}$ ; 0.488 mS

## Chapter 17

**17.1**  $A_{mid} = 50, F_L(s) = \frac{s^2}{(s+3)(s+40)}$ , yes,  $A_v(s) \approx 50 \frac{s}{(s+40)}$ , 6.37 Hz, 6.40 Hz

**17.4** 200,  $\frac{1}{\left(\frac{s}{10^4} + 1\right)\left(\frac{s}{10^5} + 1\right)}$ , yes, 1.59 kHz, 1.58 kHz

**17.7** 400,  $\frac{s^2}{(s+1)(s+2)}$ ,  $\frac{1}{\left(1 + \frac{s}{500}\right)\left(1 + \frac{s}{1000}\right)}$ , 0.356 Hz, 71.2 Hz; 0.380 Hz, 66.7 Hz

**17.9** (b) -20.4 (26.2 dB), 13.3 Hz

**17.10** (b) -22.3, 10.7 Hz (c) 16.2 V

**17.11** 2.06  $\mu\text{F}$ ; 2.20  $\mu\text{F}$ , 47.1 Hz

**17.13** 0.194  $\mu\text{F}$ ; 0.20  $\mu\text{F}$ ; 1940 Hz

**17.14**

$$A_v(s) = A_{mid} \frac{s^2}{(s + \omega_1)(s + \omega_2)} \quad | \quad \omega_1 = \frac{1}{C_1 \left( R_S + R_E \left\| \frac{1}{g_m} \right. \right)} \quad | \quad \omega_2 = \frac{1}{C_2 (R_C + R_3)} \quad | \quad 2 \text{ zeros at } \omega = 0$$

27.2 dB, 369 Hz; -7.15 V, 7.60 V

**17.16** 123 Hz; 91 Hz; (144  $\mu\text{A}$ , 3.67 V)

**17.18** -131, 49.9 Hz, 12.0 V

**17.19** 53.4 Hz

**17.21** 7.23 dB, 12.7 Hz

**17.23** +0.739, 11.9 Hz, 7.5 V

**17.24** 0.15  $\mu\text{F}$

**17.25** 3.9  $\mu\text{F}$

**17.27** 0.82  $\mu\text{F}$

**17.29** 0.33  $\mu\text{F}$

**17.30** 308 ps

**17.33** (a) 22.5 GHz

**17.35** 750  $\Omega$

**17.36** -96.7; -110

- 17.37** 0.976; 0.977
- 17.39**  $8.00\angle -90^\circ$ ;  $272\Omega\angle -23.0^\circ$
- 17.41** (a) -5000, -100.0, -4989, -122, 2% error (b) -250, -60.0, -150, -100, 60% error
- 17.43** Real roots: -100, -20, -15, -5
- 17.45** (0.924 mA, 2.16 V); -89.6, 1.45 MHz; 130 MHz
- 17.47** -20.4, 429 kHz;  $4900\Omega\angle -90^\circ$ ,  $2.80\angle -90^\circ$
- 17.49** (0.834 mA, 2.41 V); -8.70, 3.22 MHz; 28.0 MHz
- 17.53** 61.0 pF, 303 MHz
- 17.56**  $1/(4\times 10^4 RC)$ ;  $1/(4\times 10^5 RC)$ ;  $-1/sRC$
- 17.58** 39.2 dB, 6.85 MHz
- 17.64** -120, 1.40 MHz; 168 MHz, 979 MHz
- 17.63**  $1.90\text{ k}\Omega$ , -51.2, 204 MHz
- 17.64** -29.3, 7.41 MHz, 227 MHz
- 17.66**  $220\text{ }\Omega$ ,  $1.1\text{ k}\Omega$ , -15.9, 201 MHz
- 17.67** -1300; -92.3; -100, -1200
- 17.68** +8.44, 64.4 MHz
- 17.70** 88.0, 1.72 MHz
- 17.73** 2.96, 14.0 MHz
- 17.74** 0.957, 13.6 MHz, 7.64 Hz
- 17.77** 0.964, 114 MHz
- 17.80** -1.43 dB, 76.0 MHz
- 17.81**  $C_{GD} + C_{GS}/(1 + g_m R_L)$  for  $\omega \ll \omega_T$
- 17.83** Using a factor of 5 margin: 20 GHz, 7.96 ps
- 17.87** 672 mA - not a realistic design. A different FET is needed.
- 17.89** (a) 393 kHz (b) 640 kHz
- 17.93** 434 kHz
- 17.95** 36.2 kHz
- 17.96** 42.2 kHz
- 17.98** (a) 543 kHz
- 17.100** (a) 2.12 MHz
- 17.102** 53.4 dB, 833 Hz, 526 kHz

- 17.103** 1.63 MHz; 300  $\mu$ H, 2.80 MHz
- 17.105** -45 $^{\circ}$ ; -118 $^{\circ}$ ; -105 $^{\circ}$
- 17.107** 22.5 MHz, -41.1, 2.91
- 17.108** 20.4 pF; 12.6;  $n = 2.81$ ; 21.9 pF
- 17.109** 15.9 MHz; 28.9 MHz
- 17.110** 13.0 MHz, 7.18, 116/ $-90^{\circ}$ ; 4.36 MHz, 5.59, 51.3/ $-90^{\circ}$
- 17.111** 10.1 MHz, 3.52, -33.3; 10.94 MHz, 6.86, -70.8
- 17.114** 65 pF; 240, -4.41x10<sup>4</sup>, 25.1 kHz
- 17.116** 67.3 pF; 152 kHz, 40
- 17.118** (b) 497  $\Omega$ , 108 pF
- 17.119** 100  $\Omega$ , 104 fF; 52.2  $\Omega$ , 144 fF
- 17.125** (a) 100 MHz, 1900 MHz
- 17.126** 61.1 dB
- 17.129** -19.5 dB; -23.9 dB
- 17.131** 0.6 A
- 17.133** -13.5 dB; -17.9 dB
- 17.135** 0.1 A
- 17.137** 1, 0.5, 0.5
- 17.139** 0.567 V
- 17.142**  $0.2I_1R_C$

## Chapter 18

**18.1** (b) 250, 3.984, 0.398%

**18.3** 1/40, 396.2, -38.90

**18.5** 97.5 dB

**18.7** 1/(1+T); 0.0995 %

**18.9** (a) Series-series feedback (b) Shunt-shunt feedback

**18.13** (a)  $857 \Omega$ , 33.3, 57.1, 506  $\Omega$

**18.15**  $25.9 \Omega$ , 0, 0.952, 13.3  $\Omega$

**18.17**  $2.13 \times 10^6$ , 24.8 S

**18.19** 2.53 mV

**18.21** 13.0,  $8.76 M\Omega$ ,  $1.54 \Omega$

**18.23**  $31.1 \Omega$ , 2.01, 17.9, 195  $\Omega$

**18.25** 10.1,  $252 k\Omega$ , 358  $\Omega$

**18.27**  $2.66 \Omega$ ; ( $32.2 \Omega$ , 0, 11.1)

**18.29**  $132 \Omega$ ; ( $13.0 k\Omega$ , 0, 97.6)

**18.31** 0.9989,  $106.4 M\Omega$ ,  $3.301 \Omega$  vs. 0.999,  $131 M\Omega$ ,  $4.53 \Omega$

**18.33**  $-36.0 k\Omega$ ,  $7.60 \Omega$ ,  $0.262 \Omega$

**18.35**  $37.0 \Omega$ ,  $50.4 \Omega$ ,  $-43.1 k\Omega$

**18.37**  $34.1 k\Omega$ ,  $1.72 k\Omega$ ,  $-625 k\Omega$

**18.39** 0.133 mS,  $60.4 M\Omega$ ,  $26.8 M\Omega$

**18.41**

SPICE Results :  $A_{tc} = 9.92 \times 10^{-5} S$     $R_{in} = 144.1 M\Omega$     $R_{out} = 11.91 M\Omega$

Hand Calculations  $A_{tc} = 9.92 \times 10^{-5} S$     $R_{in} = 148 M\Omega$     $R_{out} = 11.1 M\Omega$

**18.43** 0.468 mS,  $95.1 M\Omega$

**18.44** 10.1,  $17.9 \Omega$ ,  $3.34 M\Omega$

**18.46**  $50.0 \Omega$ ,  $5.63 M\Omega$ , 0.993

**18.47**  $14.92 M\Omega$ ,  $399.8 M\Omega$ ,  $540.1 M\Omega$

**18.49**  $2.97$ ,  $14.5 \Omega$ ,  $24.3 M\Omega$ ;  $2.99$ ,  $14.6 \Omega$ ,  $18.1 M\Omega$

**18.51**  $30.39 G\Omega$ ;  $33.3 G\Omega$

**18.53**  $47.32 M\Omega$ ;  $37.5 M\Omega$

**18.55**  $T_v = 106.3$ ,  $T_i = 15.93$ ,  $T = 13.62$ ,  $R_2/R_1 = 6.34$

**18.57**  $T_v = 1472$ ,  $T_i = 168$ ,  $T = 150.6$ ,  $R_2/R_1 = 8.716$

**18.59** 110 kHz, 2048,  $\leq 2048$

**18.61** 285 pF

**18.63** 76.6°

**18.65** 107°

**18.69** 6.63 MHz, 20.8 V/μS

**18.72** (b) 95 MHz, 30 V/μS

**18.74** ±8.57 V/μS, SPICE +8.1 V/μS, -8.8 V/μS

**18.76** 71.5 MHz, 11.3 kHz, 236 MHz, 326 MHz, 300 MHz; 84.4 dB;  $< 0$ ; 16.8 pF

**18.78** 11.9 kΩ; 9.04 MHz, 101 MHz, 66.8 MHz, 286 MHz; 10.0 MHz, 11.3 pF

**18.79** (a) 37°

**18.82** 6.32 pF; 315 MHz, 91.4 MHz; 89.4°

**18.85** 15.9 MHz; [18.4 MHz, 33.1 MHz]; 0.211 mS, 5.28 μA

**18.86** 5.45 MHz, 4.78 MHz

**18.88** 10.3 MHz, 1.18

**18.90** 7.96 MHz, 8.11 MHz, 1.05

**18.92** 7.5 MHz, 80 V<sub>p-p</sub>

**18.93** 7.96 MHz

**18.94** 11.1 MHz, 18.1 MHz, 1.00

**18.95**  $L_{EQ} = L_1 + L_2$  |  $R_{EQ} = -\omega^2 g_m L_1 L_2$

$$\mathbf{18.97} \quad \omega_o = \frac{1}{\sqrt{(L_1 + L_2 + 2M)C}}$$

$$\mathbf{18.99} \quad \omega_o^2 = \frac{1}{L(C + C_{GS} + 4C_{GD})} \quad | \quad \mu_f \geq 1 + \frac{r_o}{R_P}$$

**18.101** 5.13 pF; 1 GHz can't be achieved.

**18.102** 4.33 pF; 2.81 mA; 3.08 mA; 1.32 V

**18.104** 15.915 mH, 15.915 fF; 10.008 MHz, 10.003 MHz

**18.106** 9.281 MHz, 9.192 MHz

**18.111** 16.3 MHz